

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE- SEMESTER-I & II EXAMINATION – WINTER 2024****Subject Code:3110005****Date:13-01-2025****Subject Name:Basic Electrical Engineering****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

**MARKS**

- |            |  |           |
|------------|--|-----------|
| <b>Q.1</b> | (a) State and explain Kirchhoff's current Law.   | <b>03</b> |
|            | (b) Prepare a list of parts of a Single-phase AC Motor.  | <b>04</b> |
|            | (c) State & Explain the Thevenin's theorem with suitable example.  | <b>07</b> |
| <b>Q.2</b> | (a) Write short note on autotransformer.   | <b>03</b> |
|            | (b) Derive the EMF equation of single-phase transformer.   | <b>04</b> |
|            | (c) When three resistances of $10\Omega$ , $20\Omega$ , and $30\Omega$ are connected in series across 230 V supply. Find (1) equivalent resistance (2) current flowing through each resistance, (3) voltage drop across each and (4) power loss in each resistor | <b>07</b> |
|            | <b>OR</b>  |           |
|            | (c) Derive the relationship between line and phase values of current in a three phase, balanced, delta connected system.   | <b>07</b> |
| <b>Q.3</b> | (a) Define following terms in connection with A.C wave forms: (i) Frequency (ii) Time period (iii) Amplitude.  | <b>03</b> |
|            | (b) If the waveform of a voltage has a form factor of 1.11 and peak factor of 1.51 and if the maximum value of a voltage is 4500 volts. Calculate the average and r.m.s. values of the voltage.  | <b>04</b> |
|            | (c) Describe the open circuit & short circuit test on single-phase transformer.  | <b>07</b> |
|            | <b>OR</b>  |           |
| <b>Q.3</b> | (a) List out the merits of two-watt meter method.  | <b>03</b> |
|            | (b) Compare series and parallel RLC circuit resonance.   | <b>04</b> |
|            | (c) Derive an expression for the voltage across the capacitor during charging through the resistor at any instant $V_c = V (1 - e^{-t/RC})$ . Assume that RC series circuit is connected across a DC supply of voltage V.  | <b>07</b> |
| <b>Q.4</b> | (a) Mention Merits and Demerits of Single-Phase Induction Motor.   | <b>03</b> |
|            | (b) Compare Squirrel cage induction motor and Slip ring Induction Motor.   | <b>04</b> |
|            | (c) Describe construction of a DC machine.   | <b>07</b> |
|            | <b>OR</b>  |           |
| <b>Q.4</b> | (a) Write applications of Auto Transformer.  | <b>03</b> |
|            | (b) Explain Working of capacitor start Single phase induction motor  | <b>04</b> |
|            | (c) Explain construction of synchronous generator with diagram.  | <b>07</b> |
| <b>Q.5</b> | (a) Write advantages and disadvantages of ELCB.  | <b>03</b> |
|            | (b) Draw the structure of underground cable with name of all sections.   | <b>04</b> |
|            | (c) Explain different methods of Power factor Improvement  | <b>07</b> |

**OR**

- Q.5**
- |     |   |           |
|-----|---|-----------|
| (a) | Write safety precautions for electrical Applications  | <b>03</b> |
| (b) | Compute the monthly energy charges for an air conditioner having Power consumption of 3 kW and daily uses 10 hours. Energy charges Rs. 5 per unit | <b>04</b> |
| (c) | Classify different types Earthing and explain any one in detail.  | <b>07</b> |

\*\*\*\*\*