

Enrollment No./Seat No.:

## GUJARAT TECHNOLOGICAL UNIVERSITY

Bachelor of Engineering - SEMESTER - III EXAMINATION - WINTER 2025

Subject Code: BE03009011

Date: 15-12-2025

Subject Name: Analog and Digital Electronics

Time: 10:30 AM TO 01:00 PM

Total Marks: 70

### Instructions

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

|  | Marks     |
|--|-----------|
| <b>Q.1</b> (a) Draw the symbol and write truth table of NAND, NOR, EX-NOR gate   | <b>03</b> |
| (b) Define slew rate, CMRR, output offset voltage and input bias current   | <b>04</b> |
| (c) Draw and explain block diagram of an OPAMP.  | <b>07</b> |
| <b>Q.2</b> (a) Define the term inverting, non-inverting and differential amplifier.  | <b>03</b> |
| (b) Discuss the application of OPAMP as a zero-crossing detector.  | <b>04</b> |
| (c) The OPAMP is a 741C with the following specifications: $A = 200000$ , $R_i = 2M\Omega$ , $R_o = 75\Omega$ , $f_o = 5\text{Hz}$ , Supply voltage = +15V, and output voltage swing = $\pm 13\text{V}$ . It is connected as a close loop noninverting amplifier with $R_1 = 1k\Omega$ and $R_F = 10\text{ k}\Omega$ . Calculate the values of $A_F$ , $R_{iF}$ , $R_{oF}$ and $f_F$ . | <b>07</b> |

### OR

|   |           |
|---|-----------|
| (c) Derive the voltage gain equation of single OPAMP close loop differential amplifier. | 07        |
| <b>Q.3</b> (a) Draw the circuit diagram of triangular wave generator using OPAMP.       | <b>03</b> |
| (b) Draw the transfer characteristic of OPAMP comparator and explain in brief.          | <b>04</b> |
| (c) Draw and explain working of adjustable voltage regulator using IC LM 317.           | <b>07</b> |

### OR

|  |           |
|--|-----------|
| (a) Draw the circuit diagram of peak detector using OPAMP  | 03        |
| (b) Draw the circuit of non-inverting negative half wave precision rectifier using OPAMP and explain in brief. | 04        |
| (c) Explain with diagram the working of Wien bridge oscillator using an OPAMP.                                 | 07        |
| <b>Q.4</b> (a) Compare the performance of SR flipflop using NAND gates and NOR gates.                          | <b>03</b> |
| (b) Classify the register based on data shifting and circuit technology with brief description.                | <b>04</b> |
| (c) Explain the working of decade counter with logic diagram and timing diagram.                               | <b>07</b> |

### OR

(a) Write excitation table of T flipflop and also write it's characteristic equation from 2 variable k-map. **03**

(b) Analyze the synchronous operation of a 4-bit shift left register by logic diagram and timing diagram. **04**

(c) Explain the working of 4-bit synchronous counter with look ahead carry. Also draw logic diagram and timing diagram. **07**

**Q.5** (a) State applications of Digital to Analog converter. **03**

(b) Explain 2-bit digital comparator with logic diagram and truth table. **04**

(c) Explain the voltage to time conversion type ADC with circuit diagram and waveforms. **07**

**OR**

(a) Write analog output voltage equation of weighted resistor D/A converter and explain in brief. **03**

(b) Draw and explain the 4-variable k-map with assuming suitable data. **04**

(c) Explain in detail the process of sampling, quantization and encoding used for A/D converter. **07**

\*\*\*