

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE- SEMESTER-VII EXAMINATION – WINTER 2025****Subject Code:3170906****Date:20-11-2025****Subject Name:Advanced Power Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

			<b>MARKS</b>
<b>Q.1</b>	(a)	Compare switching voltage regulator with linear voltage regulator.	<b>03</b>
	(b)	Explain fly back converter.	<b>04</b>
	(c)	Describe Cuk converter with circuit diagram.	<b>07</b>
<b>Q.2</b>	(a)	Classify the Resonant converter.	<b>03</b>
	(b)	Compare ZVS-ZCS converter.	<b>04</b>
	(c)	Explain operation of ZVS converter with diagram and wave forms.	<b>07</b>
<b>OR</b>			
	(c)	Derive the expression for duty ratio in discontinuous mode of operation with constant $V_o$ for Buck converter with circuit diagram and waveform.	<b>07</b>
<b>Q.3</b>	(a)	Explain concept of multilevel inverter.	<b>03</b>
	(b)	State important advantages, disadvantages and applications of SMPS	<b>04</b>
	(c)	Draw the circuit diagram and waveform of five levels cascaded H – Bridge Multilevel Inverter and explain its working	<b>07</b>
<b>OR</b>			
<b>Q.3</b>	(a)	Explain half bridge converter.	<b>03</b>
	(b)	Compare the three topologies of multilevel inverter	<b>04</b>
	(c)	Explain working of Diode Clamped three level inverter.	<b>07</b>
<b>Q.4</b>	(a)	Discuss Equipment required for HVDC System and their significance	<b>03</b>
	(b)	Give Comparison of HVAC and HVDC transmission.	<b>04</b>
	(c)	Draw the transformer connections for 18 pulse converter. Explain Y-Z2 transformer connection used for multipulse converter.	<b>07</b>
<b>OR</b>			
<b>Q.4</b>	(a)	Explain different type of HVDC link.	<b>03</b>
	(b)	Explain the all equipments required for HVDC system.	<b>04</b>
	(c)	Draw and explain bipolar HVDC power transmission system based on 12 pulse converters for each pole	<b>07</b>
<b>Q.5</b>	(a)	Explain operating principle of Unified power flow controller (UPFC).	<b>03</b>
	(b)	Give comparison of SVC and STATCOM.	<b>04</b>

- (c) Discuss principle of series compensation. Explain operation of static synchronous series compensator (SSSC). **07**

**OR**

- Q.5** (a) What is phase angle compensation in transmission line? **03**  
(b) Define FACTS. Give detail classification of FACTS controller. **04**  
(c) Discuss principle of shunt compensation. Explain operation of fixed capacitor- thyristors controlled reactor (FC-TCR) **07**

\*\*\*\*\*