

Enrollment No./Seat No.:

GUJARAT TECHNOLOGICAL UNIVERSITY

Bachelor of Engineering - SEMESTER - III EXAMINATION - WINTER 2025

Subject Code: BE03000161

Date: 15-12-2025

Subject Name: Network Theory


Time: 10:30 AM TO 01:00 PM

Total Marks: 70

Instructions


1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

	Marks
Q.1 (a) List out independent and dependent electrical sources with their symbols.	03
(b) Determine the current through load resistor using source transformation techniques.	04

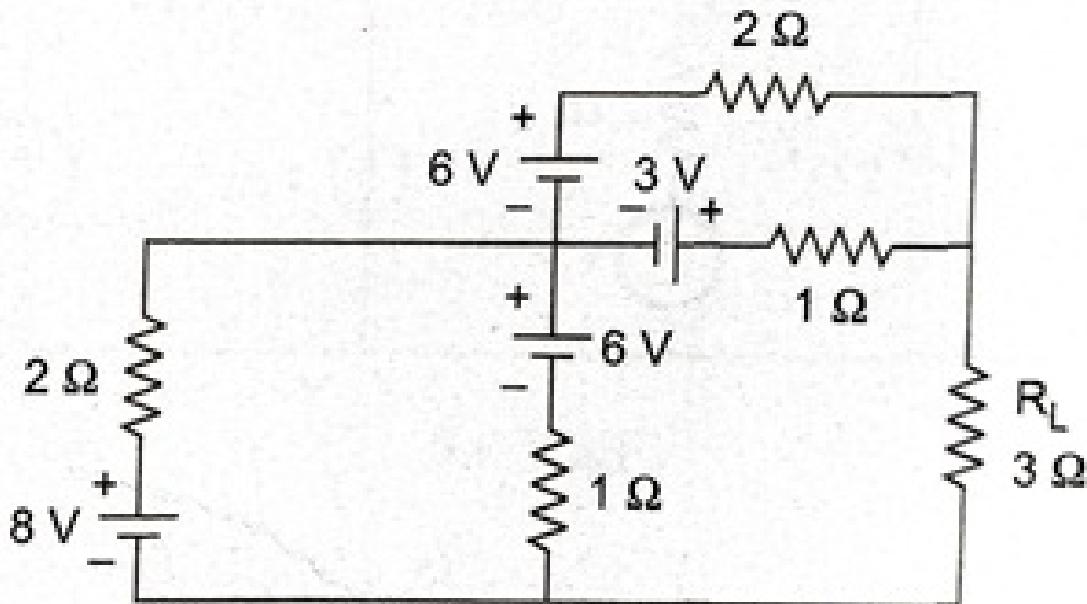

(c) For the given network, determine the current in 4Ω resistors using Mesh Analysis.

07

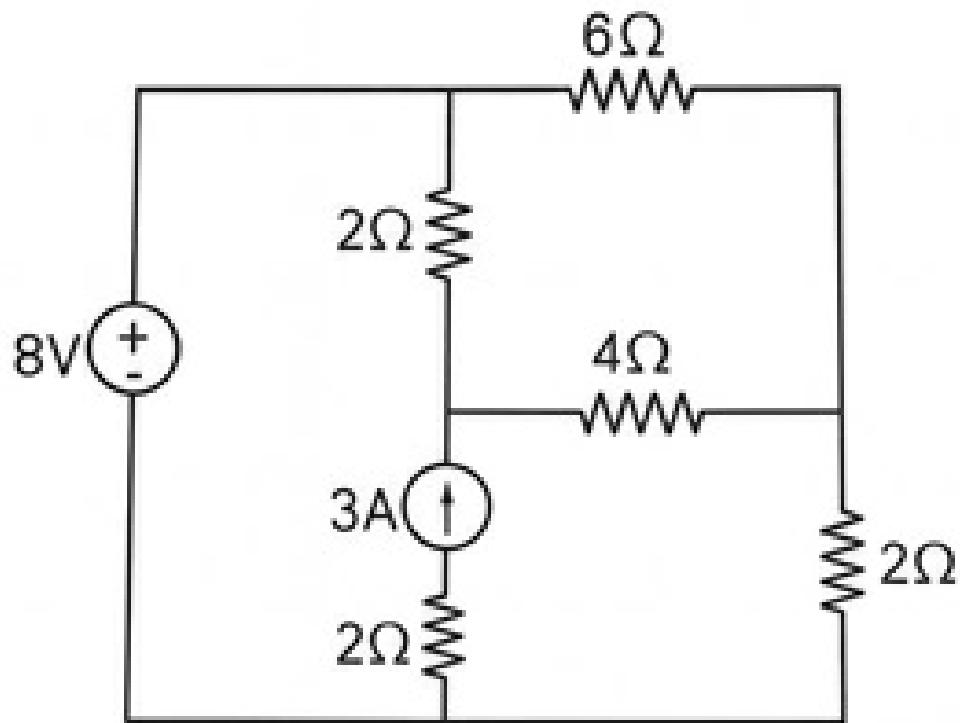


Q.2 (a) State the Superposition Theorem. List its limitations.

03


(b) For the transformer shown in the figure with 3 winding with their winding directions over the limbs, mark the dots on the terminals according Dot convention theorem.

04

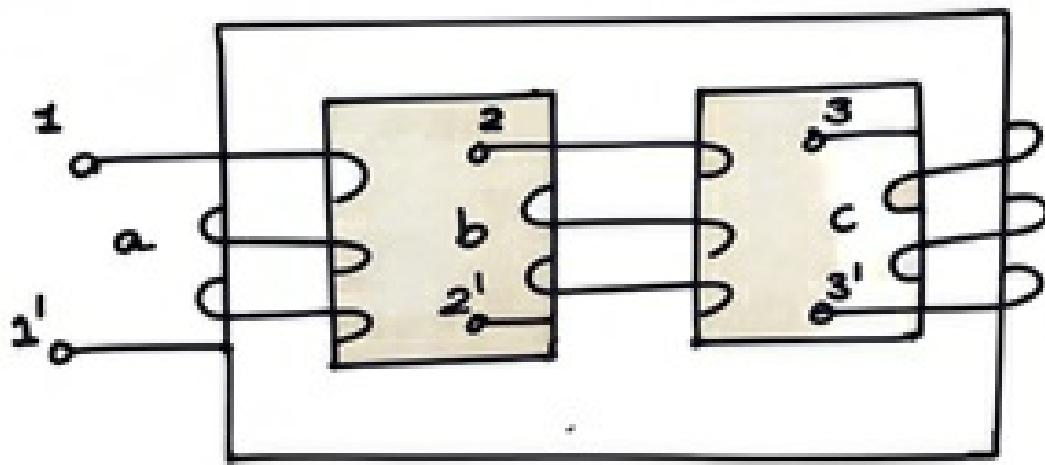

(c) Draw Thevenin's equivalent circuit across terminal AB of the given network.


07

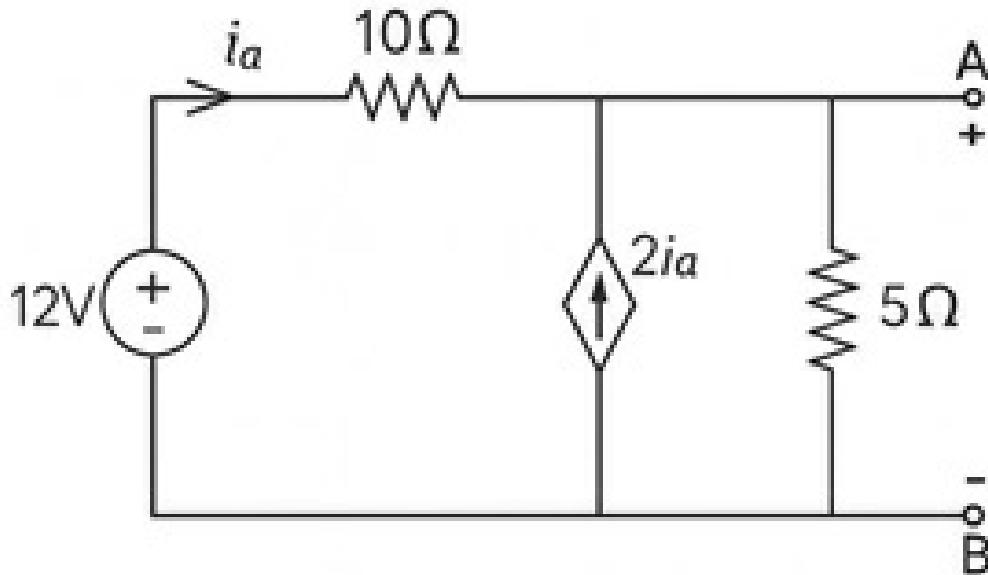

OR


(c) Determine the current i in the circuit shown in figure using Nodal analysis.

07

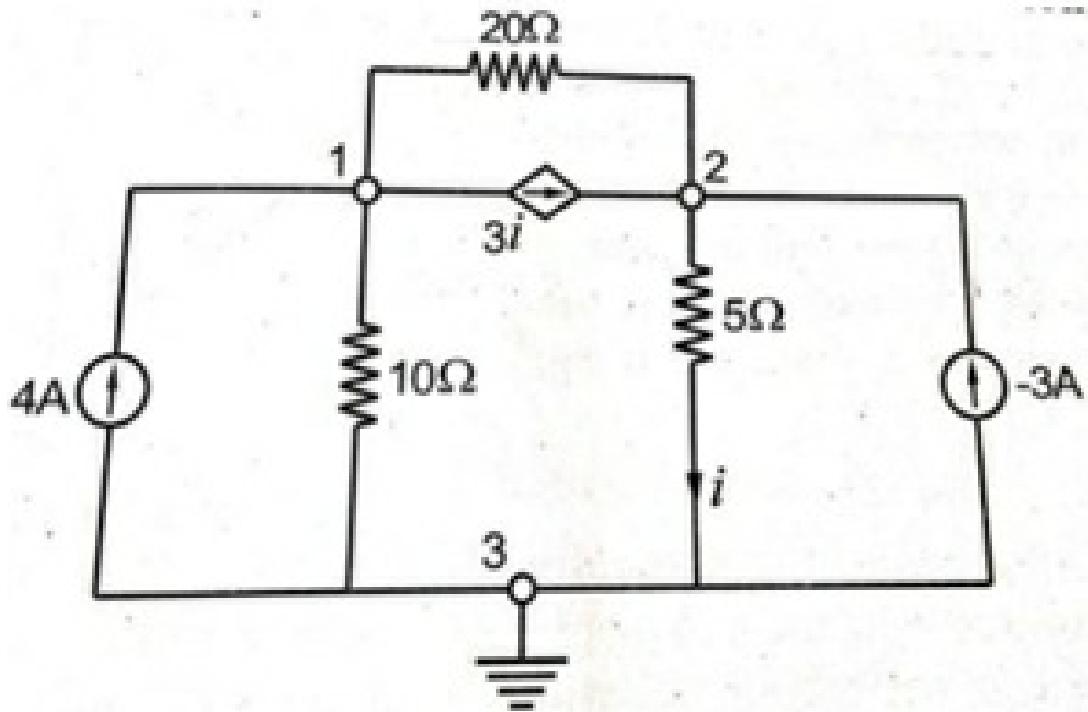

Q.3 (a) Draw dual of the given network.

03

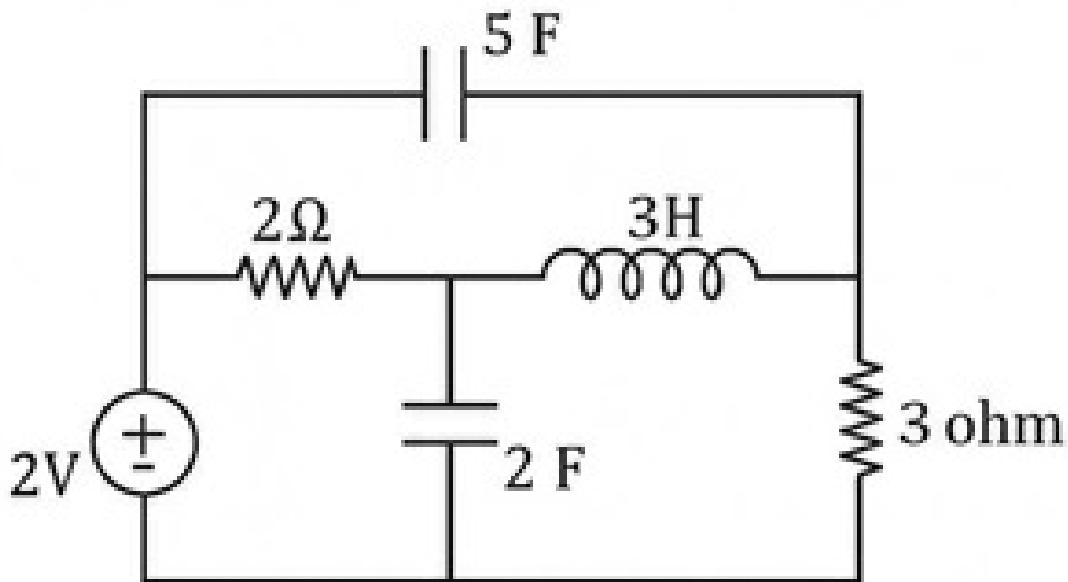

(b) Draw and explain briefly the equivalent circuit of the charged and uncharged inductor and capacitor at $t=0+$ and $t=\infty$ (infinity). 04

(c) State Maximum Power Transfer theorem and explain in brief. Derive the condition for maximum power transfer to the load for DC and AC circuits. 07


OR

(a) Define the time-constant. Explain the significance of the time-constant. 03

(b) State and Explain Millman's theorem. 04

(c) Find the value of I_x using Superposition theorem in the circuit shown below.

07

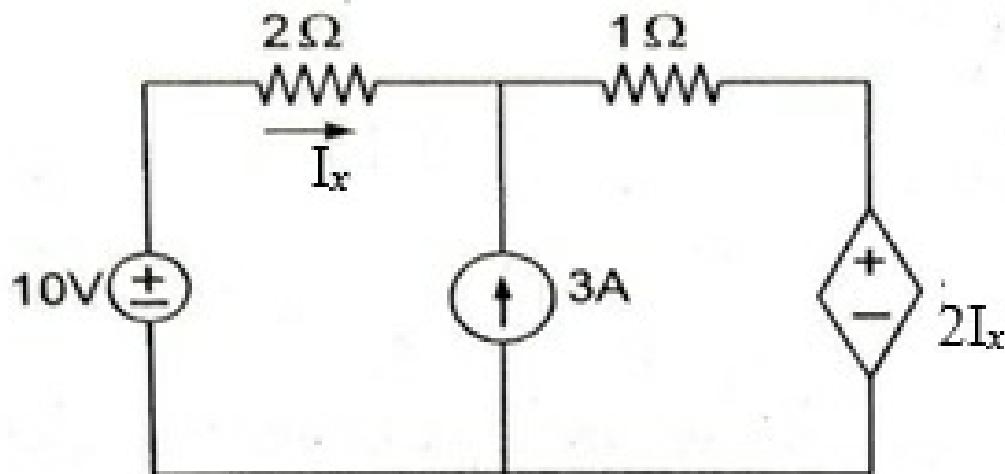

Q.4 (a) Find the Laplace Transform of $e^{-at} \cos wt$.

03

(b) The reduced incidence matrix of an oriented graph is as shown below.

04

$$A = \begin{pmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{pmatrix}$$

a) Draw the graph b) How many trees are possible? c) Write the tie set matrix d) Write the cut set matrix

(c) Obtain the transient response of a first order system using a suitable example.


07

OR


(a) State initial and final value theorem with appropriate equation in term of Laplace Transformation.

03

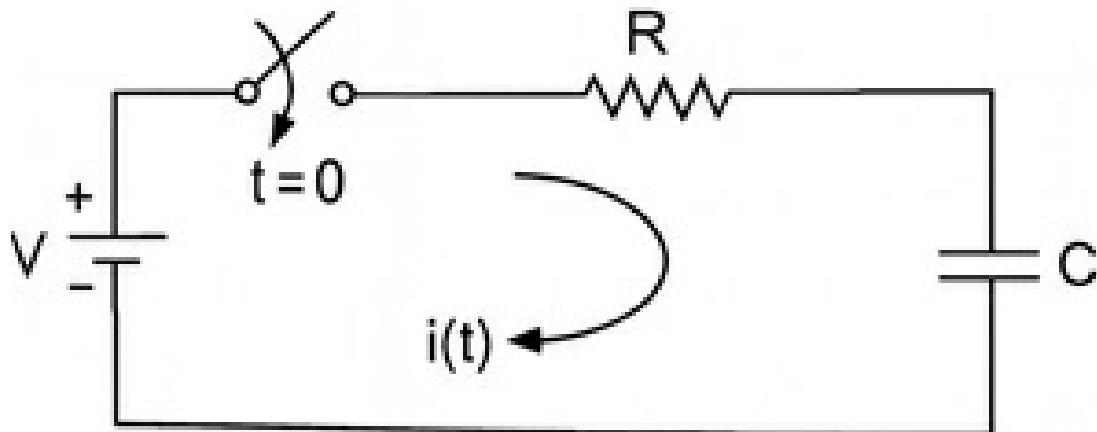(b) A series R-C circuit is connected to a constant d.c. voltage source V through switch K , as shown in figure. Initially the switch is kept open for very long time. Obtain the expression for the current $i_c(t)$ through capacitor for $t > 0$.



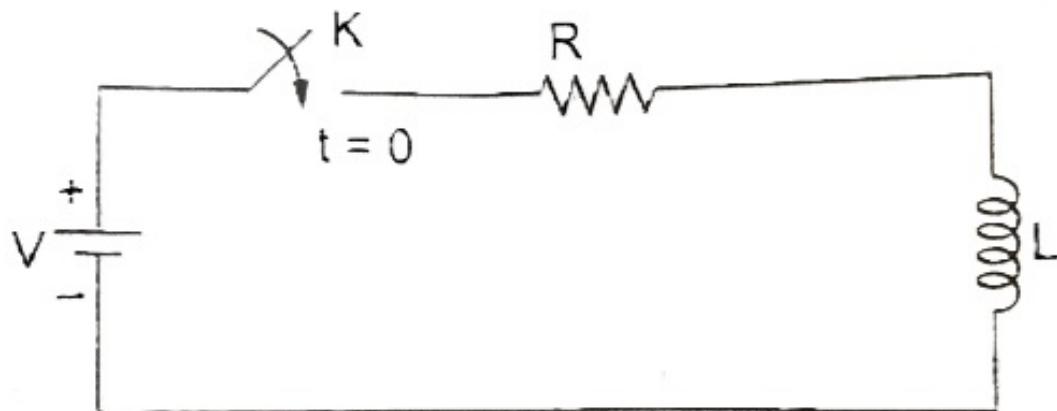(c) The switch is closed at $t = 0$. Find out value of $i, \frac{di}{dt}, \frac{d^2i}{dt^2}$ at $t = 0+$. The value of R is 10Ω , L is $1H$ and $100V$ is applied. Assume initial current of inductor to be zero.



Q.5 (a) List out and write the equation of h-parameters and ABCD-parameters. **03**
(b) Derive z-parameters in terms of y-parameters. **04**
(c) Explain condition of reciprocity and symmetry of two port network in terms of z-parameter. **07**

OR

(a) Define (1) Oriented Graph (2) Incidence matrix (3) Tree **03**
(b) Write down the necessary and sufficient conditions for positive real function (PRF). **04**
(c) Derive the relation between incidence matrix, fundamental tie-set matrix and fundamental cut-set matrix. **07**
