

GUJARAT TECHNOLOGICAL UNIVERSITY**BE- SEMESTER-III EXAMINATION – WINTER 2025****Subject Code:3131103****Date:22-12-2025****Subject Name: Network Theory****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

Marks

| | | |
|------------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------|
| Q.1 | (a) State and explain superposition's theorem. | 03 |
| | (b) Derive the condition for network to be reciprocal for y-parameters. | 04 |
| | (c) Determine the power delivered by the voltage source for the circuit shown in fig.1 | 07 |
| Q.2 | (a) Determine the Laplace transform of $f(t) = e^{5t} \sin 8t$. | 03 |
| | (b) Write a short note on Dot Convention. | 04 |
| | (c) Derive relationship between incidence matrix and fundamental cut-set matrix. | 07 |
| | OR | |
| | (c) Find the current in 10ohm resistor in the network of Fig.2 using Thevenin's theorem. Resistances are in ohms. | 07 |
| Q.3 | (a) Explain initial value theorem of Laplace transform. | 03 |
| | (b) Explain and derive the step response to R-L series circuit using Laplace Transformation method. | 04 |
| | (c) In the network of Fig.3, a steady state is reached with the switch k open. At $t=0$, the switch is closed. For the elements given, determine values of $V_a(0-)$ and $V_a(0+)$. | 07 |
| | OR | |
| Q.3 | (a) Explain final value theorem of Laplace transform. | 03 |
| | (b) Explain and derive the step response to R-C series circuit using Laplace Transformation method. | 04 |
| | (c) In the network of Fig.4, the switch k is closed at $t=0$. Find the particular solution for the current. | 07 |
| Q.4 | (a) Explain characteristic of an ideal current source. | 03 |
| | (b) Briefly explain Positive Real Function (PRF). | 04 |
| | (c) In the circuit shown in Fig.5, switch k is closed on position 1 at $t=0$, and then moved to position 2 after 0.5ms. Obtain the equations for the current in both intervals. | 07 |
| | OR | |
| Q.4 | (a) Explain characteristic of an ideal voltage source. | 03 |
| | (b) Explain following terms: (a) Tree (b) Mesh (c) Subgraph d) Planar Graph. | 04 |
| | (c) Obtain required condition for ABCD parameters to be reciprocal and symmetrical. | 07 |
| Q.5 | (a) Write a short note on Source Transformation. | 03 |
| | (b) Write a short note on Inverse Hybrid Parameters. | 04 |
| | (c) Obtain Z parameters for the network shown in Fig.6 | 07 |
| | OR | |
| Q.5 | (a) What is network synthesis? | 03 |
| | (b) Derive formulae to convert given y – parameters into z - parameters. | 04 |
| | (c) Find Norton's equivalent network across terminals AB of the network shown in Fig. 7 | 07 |

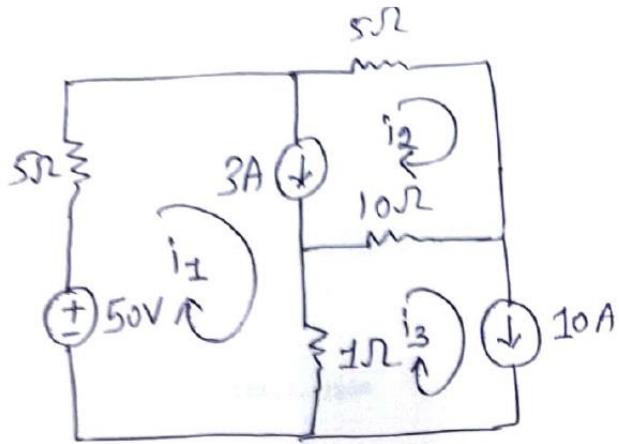


Fig 1.

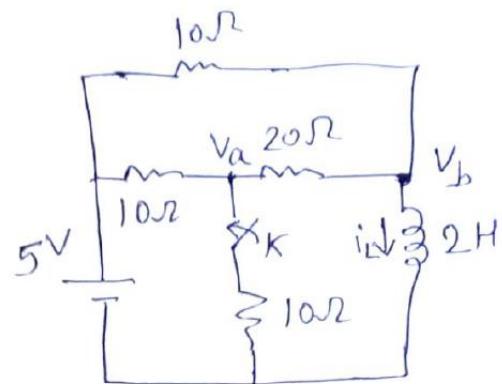


Fig 3

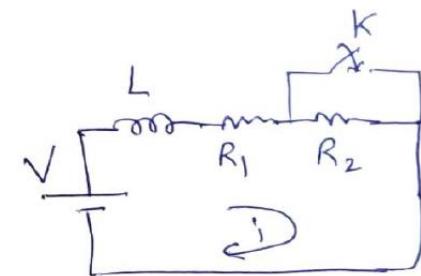
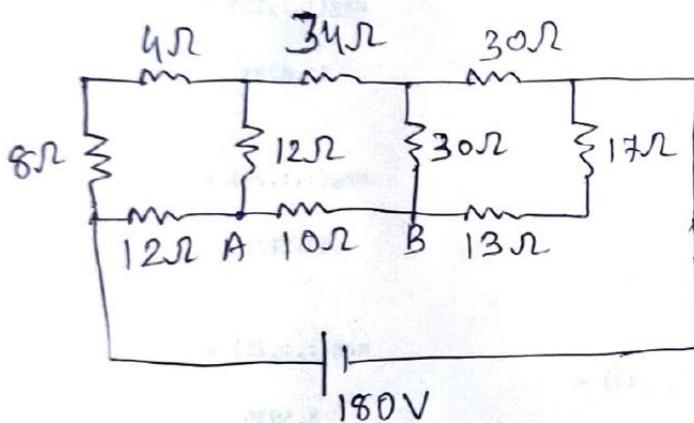


Fig 4

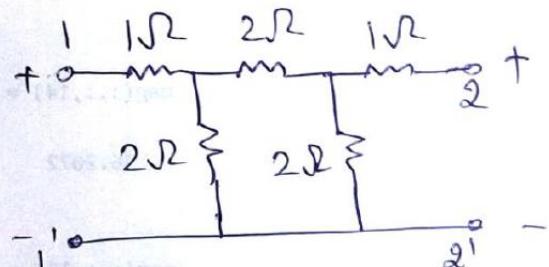
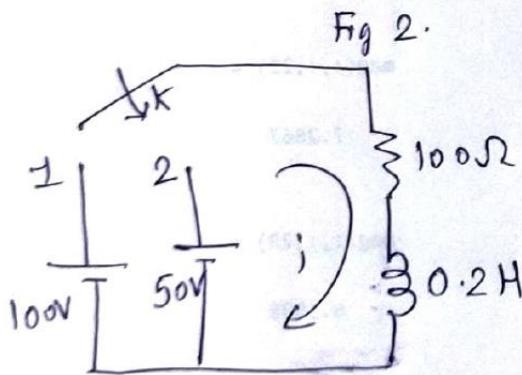


Fig 6

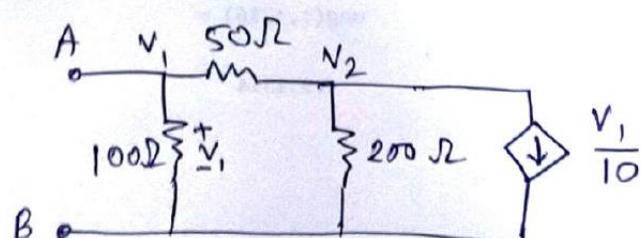


Fig 7
