

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE- SEMESTER-V EXAMINATION – WINTER 2025

Subject Code:3151106

Date:19-11-2025

Subject Name:Power Electronics

Time:10:30 AM TO 01:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) Design VI characteristic of SCR. Show and explain the difference between holding current and latching current.	03
	(b) Make the comparison between SCR and TRIAC.	04
	(c) A single phase half wave controlled rectifier is operated from a 240 V, 50 Hz. Load resistance $R = 20 \Omega$. If the average output voltage is 25% of the maximum possible average output voltage, determine: (1) the firing angle (2) rms and average output and SCR currents.	07
Q.2	(a) Explain the effect of freewheeling diodes in power electronics circuits.	03
	(b) Explain the SCR resistance-capacitance triggering circuit.	04
	(c) Explain the operation of single phase semi controlled bridge converter with resistive and inductive load. Draw the associated waveforms.	07
OR		
	(c) A dc chopper circuit connected to 100 V dc source supplies an inductive load having 50 mH in series with resistance of 5Ω . Freewheeling diodes is placed across the load. The load current varies between the limits of 10-12 A. Determine the time ratio of the chopper.	07
Q.3	(a) What is the function of Chopper? Explain the working of step-up chopper.	03
	(b) With help of waveform explain the current limit control strategy of chopper.	04
	(c) With help of neat circuit diagram and waveforms, explain the operation of PWM half bridge inverter with resistive load.	07
OR		
Q.3	(a) What are the applications of chopper? Explain the working of class D chopper.	03
	(b) Compare the step up and step down chopper.	04
	(c) With help of neat circuit diagram and waveforms, explain the operation of single phase current source inverter.	07
Q.4	(a) What is commutation? Explain self commutation.	03
	(b) Explain the snubber circuits for thyristor.	04
	(c) Explain the basic structure and VI characteristic of IGBT.	07
OR		
Q.4	(a) What is the function of an inverter? List out various applications of an inverter.	03
	(b) Explain two transistor analogy of SCR.	04
	(c) Draw and explain the structure of power MOSFET. Explain principle and operation and V-I characteristics of power MOSFET.	07

- Q.5** (a) Compare Power supply and SMPS. **03**
(b) Explain the working of Fly back SMPS. **04**
(c) Write short note on UPS. **07**

OR

- Q.5** (a) Compare EMI and EMC. **03**
(b) Explain the working of DC chopper drive. **04**
(c) Write short note on P M Stepper Motor drives. **07**