

Enrollment No./Seat No.:

GUJARAT TECHNOLOGICAL UNIVERSITY

Bachelor of Engineering - SEMESTER - 1/2 EXAMINATION - WINTER 2025

Subject Code: BE01000111/BE01R00111

Date: 30-12-2025

Subject Name: Basic Electronics Engineering

Time: 02:30 PM TO 05:00 PM

Total Marks: 70

Instructions

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

	Marks
Q.1 (a) A BJT has emitter current and collector current of the value 10 mA and 9.8 mA respectively, determine current gains for CB and CE configurations.	03
(b) Explain forward and reverse bias operation of a P-N junction diode with depletion region.	04
(c) Draw CB configuration using NPN transistor and discuss its input and output characteristics with I_{CBO} , r_i , r_o , and current gain α .	07
Q.2 (a) Define knee voltage, bulk resistance and PIV for a P-N junction.	03
(b) Draw Bridge rectifier circuit and input and output waveforms. Also derive output voltages V_{dc} & V_{rms} .	04
(c) Draw circuit for voltage Doubler, Tripler & Quadrupler and explain their operation.	07
OR	
(c) Differentiate between Avalanche and Zener breakdown and discuss circuit of Zener as a voltage regulator.	07
Q.3 (a) Explain biased negative clipper with necessary waveforms.	03
(b) Discuss Choke input filter with its limitations.	04
(c) Discuss load line, operating point, DC & AC load lines for BJT.	07
OR	
(a) Describe positive clamper circuit with necessary waveforms.	03
(b) Describe RC filter and state ripple voltage formula.	04
(c) Discuss thermal stability of BJT with stability factors S , S' , S'' .	07
Q.4 (a) Explain FET as a switch.	03
(b) Draw Hybrid equivalent model of transistor for CB, CE, CC configurations.	04
(c) Explain CE amplifier with derivation of input impedance, output impedance and voltage gain in terms of h parameters.	07

OR

- (a) Explain FET as an amplifier. **03**
- (b) Compare CB, CE, CC amplifiers. **04**
- (c) Explain voltage divider bias circuit for BJT in detail. **07**

Q.5 (a) Discuss Solar cell in detail. **03**

(b) Explain Varactor diode with applications. **04**

(c) Explain Drain characteristics and Transfer characteristics of JFET in detail with all related terms as Transconductance g_m , drain resistance r_d , and amplification factor μ . **07**

OR

- (a) Describe LED with applications. **03**
- (b) Discuss Tunnel diode with its V/I characteristics and applications **04**
- (c) Explain MOSFET and draw the structure for D-MOSFET & E-MOSFET. **07**
