

GUJARAT TECHNOLOGICAL UNIVERSITY**BE- SEMESTER-I&II EXAMINATION – SUMMER 2025****Subject Code:3110016****Date:17-06-2025****Subject Name:Basic Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

MARKS

Q.1	(a) Draw and explain constructional details and symbols for BJT.	03
	(b) Draw and explain the V/I characteristics of a practical diode.	04
	(c) Draw Common Base configuration and discuss its input and output characteristics with I_{CBO} , r_i , r_o , and current gain α .	07
Q.2	(a) Define: clipper, Clamper, PIV of a Diode.	03
	(b) Compare different rectifier circuits.	04
	(c) Discuss diode approximations.	07
	OR	
	(c) Explain full wave center-tape rectifier in detail with waveforms and derivation of average output voltage.	07
Q.3	(a) Draw circuit diagram of positive clamper and explain the operation.	03
	(b) Draw and explain circuit of AND gate using diodes.	04
	(c) Explain thermal stability of BJT with stability factors S , S' , S'' .	07
	OR	
Q.3	(a) Draw Hybrid equivalent model of transistor for CB, CE, CC configurations.	03
	(b) Describe LED with its applications.	04
	(c) Discuss operation and applications of PIN Photo diode and Solar cell.	07
Q.4	(a) State the difference between Avalanche breakdown and Zener breakdown.	03
	(b) Discuss seven segment display with its types.	04
	(c) Explain biased positive and negative clipper circuits in detail.	07
	OR	
Q.4	(a) For a BJT, α_{dc} is 0.98 and base current is $50 \mu A$, then find β_{dc} , I_C & I_E .	03
	(b) Compare CB, CE, CC configurations.	04
	(c) Draw Emitter follower circuit and discuss its input and output characteristics.	07
Q.5	(a) Compare BJT & FET.	03
	(b) Explain OR gate using diodes.	04
	(c) Describe MOSFET operation and draw the structures for D-MOSFET & E-MOSFET.	07
	OR	
Q.5	(a) Discuss FET as an amplifier.	03
	(b) Compare different logic families.	04
	(c) Explain Drain characteristics and Transfer characteristics of JFET in detail with all related terms as Transconductance, drain resistance and amplification factor.	07
