

GUJARAT TECHNOLOGICAL UNIVERSITY**BE- SEMESTER-I & II EXAMINATION – WINTER 2025****Subject Code:3110016****Date:19-01-2026****Subject Name:Basic Electronics****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) Draw the vi characteristics for ideal diode and real diode. (b) Explain the forward and reverse bias of PN junction. (c) Discuss the operation of full bridge rectifier circuits with voltage and current waveforms.	03 04 07
Q.2	(a) Draw the circuits for clipping the voltage waveforms. (b) Explain the characteristics of Zener diode. (c) Write short note on bipolar junction transistor (BJT).	03 04 07
	OR	
	(c) Explain the operation of transistor as amplifier in Common Emitter(CE) configuration.	07
Q.3	(a) Write key factors to achieve faithful amplifications. (b) Discuss the importances of operating points in transistor. (c) Discuss the load line analysis of transistor.	03 04 07
	OR	
Q.3	(a) What is a stability factor? (b) Explain the voltage divider biasing. (c) Discuss the construction and operation of Schottky diode.	03 04 07
Q.4	(a) What are the roles of coupling capacitor and bypass capacitor in amplifier circuits? (b) Discuss the operation of common collector circuits analysis. (c) Shows parametric comparisons between of CE, CB and CC.	03 04 07
	OR	
Q.4	(a) Draw the circuits of seven segment LED display. (b) What are the differences between FET and BJT? (c) Write short note on MOSFET.	03 04 07
Q.5	(a) Prepare the truth table for three basic logic gates. (b) Explain the working principle of a field effect transistor (FET). (c) Discuss the resistor transistor logic (RTL)circuits for basic gates.	03 04 07
	OR	
Q.5	(a) Draw the circuit diagram of OR gate with diodes. (b) Show the implementation of OR gate logic with use of NAND gate. (c) Discuss the applications of EX-OR and EX-NOR gate with truth tables.	03 04 07