

Subject Name & Code:**BASIC ELECTRICAL ENGINEERING- BE01R00051**

PBL Assignment – 2**Q-1: Derive the current and voltage relation in a purely resistive AC circuit.**

Answer:

In a purely resistive AC circuit, the voltage $v(t)$ and current $i(t)$ are in phase. Let the supply voltage be:

$$v(t) = V_m \sin(\omega t)$$

By Ohm's law,

$$i(t) = \frac{v(t)}{R} = \frac{V_m}{R} \sin(\omega t)$$

Let $I_m = \frac{V_m}{R}$. Then:

$$i(t) = I_m \sin(\omega t)$$

Both waveforms reach their maximum, minimum, and zero points at the same instant. The phasor representation shows **V** and **I** aligned along the same direction, with a phase difference of 0° .

Q-2: Explain AC circuit containing pure capacitance with phasor diagram.

Answer:

In a pure capacitive circuit, current leads voltage by 90° .


Capacitive reactance:

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

If $v(t) = V_m \sin(\omega t)$, then:

$$i(t) = C \frac{dv}{dt} = \omega C V_m \cos(\omega t) = I_m \sin\left(\omega t + \frac{\pi}{2}\right)$$

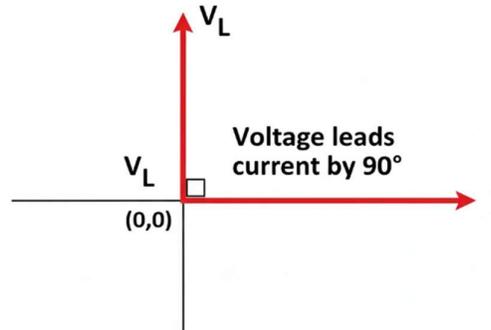Phasor Diagram: (Diagram is AI generated and only for reference)



Q-3: Analyze series RC circuit with phasor diagram.

Answer:

Impedance of series RC:

$$Z = R - jX_C \text{ where } X_C = \frac{1}{\omega C}$$

Magnitude:

$$|Z| = \sqrt{R^2 + X_C^2}$$


Phase angle:

$$\phi = -\tan^{-1}\left(\frac{X_C}{R}\right) \text{ (current leads voltage)}$$

Current:

$$I = \frac{V}{|Z|}$$

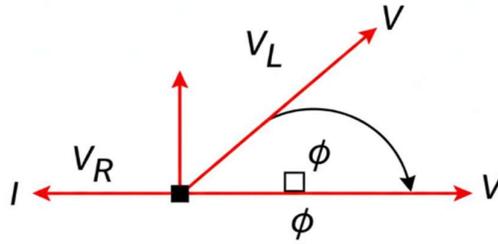Phasor Diagram: (Diagram is AI generated and only for reference)



Q-4: Explain parallel RLC circuit with phasor diagram.

Answer:

For parallel R, L, C across same AC voltage V :

- $I_R = \frac{V}{R}$ (in phase with V)
- $I_L = \frac{V}{X_L}$ (lags V by 90°)
- $I_C = \frac{V}{X_C}$ (leads V by 90°)

Net reactive current:

$$I_X = I_C - I_L$$

Resultant current:

$$I = \sqrt{I_R^2 + (I_C - I_L)^2}$$

Phase angle:

$$\phi = \tan^{-1} \left(\frac{I_C - I_L}{I_R} \right)$$

Q-5: Explain series resonance and derive resonant frequency.

Answer:

In series RLC, impedance is:

$$Z = R + j \left(\omega L - \frac{1}{\omega C} \right)$$

Resonance occurs when imaginary part = 0:

$$\omega L = \frac{1}{\omega C}$$
$$\omega_r = \frac{1}{\sqrt{LC}}$$
$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

At resonance:

- Impedance is minimum ($Z = R$).
- Current is maximum ($I = V/R$).
- Voltage across L and C can be higher than supply voltage (Q-factor effect).
- Power factor = 1.

Q-6: Explain advantages of three-phase system over single-phase system.

Answer:

1. **Power Delivery:** Constant instantaneous power in balanced 3-phase, leading to smoother motor operation.
2. **Efficiency:** Higher power-to-weight ratio for generators, motors, and transformers.
3. **Economy:** Less conductor material for same power transmission compared to single-phase.
4. **Flexibility:** Can supply both single-phase and three-phase loads.
5. **Self-starting:** Three-phase induction motors are self-starting without extra starting devices.

Q-7: Explain power measurement in three-phase balanced circuits.

Answer:

For balanced three-phase systems:

- **Two-wattmeter method** is commonly used (for 3-wire systems).
- Total power:

$$P_T = W_1 + W_2$$

- Power factor:

$$\tan \phi = \sqrt{3} \frac{W_1 - W_2}{W_1 + W_2}$$

- Each wattmeter reads:

$$W = V_L I_L \cos (\phi \mp 30^\circ)$$

Q-8: Derive expression for total power in a three-phase balanced system.

Answer:

Let phase voltage = V_{ph} , phase current = I_{ph} , power factor angle = ϕ .

Power per phase:

$$P_{ph} = V_{ph} I_{ph} \cos \phi$$

For star: $V_L = \sqrt{3} V_{ph}$, $I_L = I_{ph}$

For delta: $V_L = V_{ph}$, $I_L = \sqrt{3} I_{ph}$

In both cases:

$$P_T = 3V_{ph} I_{ph} \cos \phi = \sqrt{3} V_L I_L \cos \phi$$

Q-9: A sinusoidal current has peak value of 15 A. Find: (a) RMS value (b) Average value (c) Form factor (d) Peak factor

Answer:

Given: $I_m = 15$ A

(a) RMS value:

$$I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{15}{\sqrt{2}} \approx 10.61 \text{ A}$$

(b) Average value (full cycle):

$$I_{avg} = \frac{2I_m}{\pi} = \frac{30}{\pi} \approx 9.55 \text{ A}$$

(c) Form factor:

$$FF = \frac{I_{rms}}{I_{avg}} = \frac{10.61}{9.55} \approx 1.111$$

(d) Peak factor:

$$PF = \frac{I_m}{I_{rms}} = \sqrt{2} \approx 1.414$$

Final Answer:

$$I_{rms} = 10.61 \text{ A}, I_{avg} = 9.55 \text{ A}, FF = 1.111, PF = 1.414$$

Q-10: A current of 10 A leads the voltage by 30°, Represent the voltage and current phasors.

Answer:

Given: $I = 10 \text{ A}, \phi = 30^\circ$ (I leads V).

Phasor Diagram Description:

- Draw horizontal reference axis.
- Draw voltage phasor **V** along reference.
- Draw current phasor **I** rotated 30° counterclockwise from **V**.
- Label lengths proportional to magnitudes, indicate angle.

Q-11: A load absorbs 4 kW at a power factor of 0.6 lagging. Find the apparent power and reactive power.

Answer:

Given: $P = 4 \text{ kW}, \text{pf} = 0.6$ lagging

Apparent power:

$$S = \frac{P}{\text{pf}} = \frac{4}{0.6} \approx 6.667 \text{ kVA}$$

Reactive power:

$$Q = \sqrt{S^2 - P^2} = \sqrt{(6.667)^2 - (4)^2} \approx 5.333 \text{ kVAR}$$

Final Answer:

$$S \approx 6.67 \text{ kVA}, Q \approx 5.33 \text{ kVAR (lagging)}$$

Q-12: A pure inductance of 0.2 H and a capacitor of 50 μF is connected to 230 V, 50 Hz supply. Calculate reactance of the circuit and current.

Answer:

Given: $L = 0.2 \text{ H}, C = 50 \mu\text{F}, V = 230 \text{ V}, f = 50 \text{ Hz}$

Inductive reactance:

$$X_L = 2\pi fL = 2\pi(50)(0.2) = 62.83 \Omega$$

Capacitive reactance:

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(50)(50 \times 10^{-6})} \approx 63.66 \Omega$$

Since L and C are in series:

$$X = X_L - X_C = 62.83 - 63.66 = -0.83 \Omega$$

(Net capacitive reactance)

Impedance magnitude:

$$|Z| = \sqrt{0^2 + (0.83)^2} \approx 0.83 \Omega$$

Current:

$$I = \frac{V}{|Z|} = \frac{230}{0.83} \approx 277.11 \text{ A}$$

Final Answer:

$$X \approx 0.83 \Omega \text{ (capacitive)}, I \approx 277.1 \text{ A}$$

Q-13: In a series RC circuit, $R = 20 \Omega$ and $C = 100 \mu\text{F}$. Find impedance, current and phase angle.

Answer:

Given: $R = 20 \Omega$, $C = 100 \times 10^{-6} \text{ F}$

Assume frequency $f = 50 \text{ Hz}$ (typical for such problems unless specified).

Capacitive reactance:

$$X_C = \frac{1}{2\pi(50)(100 \times 10^{-6})} \approx 31.83 \Omega$$

Impedance:

$$Z = R - jX_C = 20 - j31.83$$

Magnitude:

$$|Z| = \sqrt{20^2 + 31.83^2} \approx 37.59 \Omega$$

Phase angle:

$$\phi = -\tan^{-1}\left(\frac{31.83}{20}\right) \approx -57.87^\circ$$

Assuming voltage V given, if not, current in terms of V is:

$$I = \frac{V}{|Z|}, \text{ leads voltage by } 57.87^\circ.$$

Final Answer:

$$|Z| \approx 37.59 \Omega, \phi \approx -57.87^\circ$$

Q-14: A resistor of 40Ω and an inductor of 0.2 H and capacitor of $120 \mu\text{F}$ are connected in parallel across 230 V , 50 Hz supply. Find (1) the current of each branch (2) the resultant current (3) Power factor of the circuit

Answer:

Given: $R = 40 \Omega$, $L = 0.2 \text{ H}$, $C = 120 \mu\text{F}$, $V = 230 \text{ V}$, $f = 50 \text{ Hz}$

Branch currents:

$$I_R = \frac{V}{R} = \frac{230}{40} = 5.75 \text{ A (in phase)}$$

$$X_L = 2\pi(50)(0.2) = 62.83 \Omega, I_L = \frac{230}{62.83} \approx 3.66 \text{ A (lags } 90^\circ)$$

$$X_C = \frac{1}{2\pi(50)(120 \times 10^{-6})} \approx 26.53 \Omega, I_C = \frac{230}{26.53} \approx 8.67 \text{ A (leads } 90^\circ)$$

Net reactive current:

$$I_X = I_C - I_L = 8.67 - 3.66 = 5.01 \text{ A (leading)}$$

Resultant current:

$$I = \sqrt{I_R^2 + I_X^2} = \sqrt{(5.75)^2 + (5.01)^2} \approx 7.63 \text{ A}$$

Power factor:

$$pf = \frac{I_R}{I} = \frac{5.75}{7.63} \approx 0.754 \text{ leading}$$

Final Answer:

$$I_R = 5.75 \text{ A}, I_L = 3.66 \text{ A}, I_C = 8.67 \text{ A}, I = 7.63 \text{ A}, pf \approx 0.754 \text{ leading}$$

Q-15: A circuit consumes a power of 1000 W at 0.6 leading power factor, when connected to 200 V, 50 Hz ac supply. Calculate (a) Current (b) Apparent power (c) Reactive power.

Answer:

Given: $P = 1000 \text{ W}$, $pf = 0.6 \text{ leading}$, $V = 200 \text{ V}$

(a) Current:

$$P = VI \cos \phi \Rightarrow I = \frac{P}{V \cos \phi} = \frac{1000}{200 \times 0.6} \approx 8.333 \text{ A}$$

(b) Apparent power:

$$S = VI = 200 \times 8.333 \approx 1666.67 \text{ VA}$$

(c) Reactive power:

$$Q = \sqrt{S^2 - P^2} = \sqrt{1666.67^2 - 1000^2} \approx 1333.33 \text{ VAR (leading)}$$

Final Answer:

$$I = 8.33 \text{ A}, S = 1666.67 \text{ VA}, Q \approx 1333.33 \text{ VAR (leading)}$$

Q-16: Two impedances are connected in parallel across a 100 volt, 50 Hz a.c. supply. Impedance no. 1 has resistance of 8Ω and capacitive reactance of 7Ω . While impedance no. 2 has resistance of 5Ω and inductive reactance of 6Ω . Calculate: (i) Current through each circuit & p.f. of each circuit. (ii) Total current and p.f. of combined circuit. (iii) Power taken by the whole circuit.

Answer:

Given:

$$Z_1 = 8 - j7 \Omega, Z_2 = 5 + j6 \Omega, V = 100 \text{ V}$$

(i) Current through each circuit & pf:

$$I_1 = \frac{V}{|Z_1|} = \frac{100}{\sqrt{8^2 + 7^2}} = \frac{100}{\sqrt{113}} \approx 9.41 \text{ A}$$

$$\text{pf}_1 = \cos \phi_1 = \frac{8}{\sqrt{113}} \approx 0.754 \text{ leading (since capacitive).}$$

$$I_2 = \frac{V}{|Z_2|} = \frac{100}{\sqrt{5^2 + 6^2}} = \frac{100}{\sqrt{61}} \approx 12.81 \text{ A}$$

$$\text{pf}_2 = \frac{5}{\sqrt{61}} \approx 0.64 \text{ lagging (inductive).}$$

(ii) Total current & pf:

Admittances:

$$Y_1 = \frac{1}{Z_1} = \frac{1}{8 - j7} = \frac{8 + j7}{113} \approx 0.0708 + j0.0619 \text{ S}$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{5 + j6} = \frac{5 - j6}{61} \approx 0.0820 - j0.0984 \text{ S}$$

$$Y_T = Y_1 + Y_2 \approx 0.1528 - j0.0365 \text{ S}$$

$$|Y_T| \approx 0.1565 \text{ S}$$

$$I_T = V \times |Y_T| = 100 \times 0.1565 \approx 15.65 \text{ A}$$

$$\phi_T = \tan^{-1} \left(\frac{-0.0365}{0.1528} \right) \approx -13.43^\circ$$

$$\text{pf}_T = \cos \phi_T \approx 0.973 \text{ leading.}$$

(iii) Power taken:

$$P = VI_T \cos \phi_T = 100 \times 15.65 \times 0.973 \approx 1522.5 \text{ W}$$

Final Answer:

$$I_1 \approx 9.41 \text{ A (0.754 leading)}, I_2 \approx 12.81 \text{ A (0.64 lagging)}, I_T \approx 15.65 \text{ A, pf}_T \approx 0.973 \text{ leading, } P \approx 1522.5$$

Q-17: A resistance of 1 Ω and inductance of 0.02 H are connected in series with a capacitor across 200 V supply. Find the value of capacitance, so that current drawn by circuit will be maximum at frequency 50 Hz. Find current and voltage across capacitor.

Answer:

Given: $R = 1 \Omega, L = 0.02 \text{ H}, V = 200 \text{ V}, f = 50 \text{ Hz}$

For max current at resonance:

$$\omega_r L = \frac{1}{\omega_r C} \Rightarrow C = \frac{1}{\omega_r^2 L} = \frac{1}{(2\pi \times 50)^2 \times 0.02}$$

$$C = \frac{1}{(314.16)^2 \times 0.02} \approx \frac{1}{1973.9} \approx 5.066 \times 10^{-4} \text{ F} = 506.6 \mu\text{F}$$

At resonance, $Z = R = 1 \Omega$

$$I_{\max} = \frac{V}{R} = \frac{200}{1} = 200 \text{ A}$$

Voltage across capacitor:

$$V_C = I \times X_C = 200 \times \frac{1}{2\pi(50)(506.6 \times 10^{-6})}$$

$$X_C = \frac{1}{314.16 \times 5.066 \times 10^{-4}} \approx 6.28 \Omega$$

$$V_C \approx 200 \times 6.28 = 1256 \text{ V}$$

Final Answer:

$$C \approx 506.6 \mu\text{F}, I_{\max} = 200 \text{ A}, V_C \approx 1256 \text{ V}$$

Q-18: For 3- ϕ star connected load consists of non-inductive resistance of 50 Ω in parallel with a capacitance of 15 μF . Calculate the line current, power absorbed, total kVA and power factor when connected to 415 V, 3 phase, 50 Hz supply.

Answer:

Given: Per phase: $R = 50 \Omega$, $C = 15 \mu\text{F}$, $V_L = 415 \text{ V}$

Phase voltage:

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{415}{\sqrt{3}} \approx 239.6 \text{ V}$$

Admittance per phase:

$$Y = \frac{1}{R} + j\omega C = \frac{1}{50} + j(2\pi \times 50 \times 15 \times 10^{-6})$$

$$Y = 0.02 + j0.004712 \approx 0.02055 \angle 13.24^\circ \text{ S}$$

Phase current:

$$I_{ph} = V_{ph} \times |Y| = 239.6 \times 0.02055 \approx 4.925 \text{ A}$$

Line current = phase current for star:

$$I_L \approx 4.925 \text{ A}$$

Power absorbed per phase:

$$P_{ph} = V_{ph}^2 \times G = (239.6)^2 \times 0.02 \approx 1148.3 \text{ W}$$

Total power:

$$P_T = 3 \times P_{ph} \approx 3444.9 \text{ W}$$

Total kVA:

$$S_T = 3 \times V_{ph} I_{ph} = 3 \times 239.6 \times 4.925 \approx 3539.6 \text{ VA} = 3.54 \text{ kVA}$$

Power factor:

$$pf = \cos(13.24^\circ) \approx 0.973 \text{ leading}$$

Final Answer:

$$I_L \approx 4.925 \text{ A}, P_T \approx 3.445 \text{ kW}, S_T \approx 3.54 \text{ kVA}, pf \approx 0.973 \text{ leading}$$

Q-19: In balanced 3- ϕ , 415 V system, line current is 100 A. When power is measured by two wattmeters, one wattmeter indicates power and other indicates zero. What will be power factor of load & measured power? If the power factor were unity and same load current what would be the reading of each wattmeter?

Answer:

Given: $V_L = 415 \text{ V}$, $I_L = 100 \text{ A}$, $W_1 = \text{some } P$, $W_2 = 0$

When one wattmeter reads zero:

$$W_2 = 0 \Rightarrow \cos(\phi - 30^\circ) = 0 \Rightarrow \phi - 30^\circ = 90^\circ \Rightarrow \phi = 120^\circ$$

But pf angle $\leq 90^\circ$ for loads. Actually, for $W_2 = 0$,

$$\phi = 60^\circ \text{ (since } W = V_L I_L \cos(\phi \pm 30^\circ)\text{)}$$

Check:

$$W_2 = V_L I_L \cos(\phi + 30^\circ) = 0 \Rightarrow \phi + 30^\circ = 90^\circ \Rightarrow \phi = 60^\circ$$

Power factor:

$$pf = \cos 60^\circ = 0.5 \text{ lagging}$$

Measured power:

$$P_T = W_1 + W_2 = W_1 + 0 = V_L I_L \cos(\phi - 30^\circ) \times 2?$$

Better: $P_T = \sqrt{3} V_L I_L \cos \phi$

$$P_T = \sqrt{3} \times 415 \times 100 \times 0.5 \approx 35938.5 \text{ W} = 35.94 \text{ kW}$$

If pf were unity ($\phi = 0$):

Each wattmeter reading:

$$W = V_L I_L \cos(30^\circ) = 415 \times 100 \times \frac{\sqrt{3}}{2} \approx 35938.5/2?$$

Actually:

$$W_1 = V_L I_L \cos(30^\circ) \approx 35938.5 \text{ W}/\sqrt{3}?$$

Let's compute:

$$W = 415 \times 100 \times \cos(30^\circ) \approx 415 \times 100 \times 0.866 \approx 35939 \text{ W? That's too high.}$$

Wait: For unity pf, total power $P_T = \sqrt{3} \times 415 \times 100 \times 1 \approx 71877 \text{ W}$.
Each wattmeter reads:

$$W = V_L I_L \cos(30^\circ) = 415 \times 100 \times 0.866 \approx 35938.5 \text{ W}$$

Thus $W_1 = W_2 \approx 35.94 \text{ kW}$.

Final Answer:

$\text{pf} = 0.5 \text{ lagging, } P_T \approx 35.94 \text{ kW, At unity pf: each wattmeter reads } \approx 35.94 \text{ kW}$
