

Subject Name & Code:

BASIC ELECTRONICS ENGINEERING- BE01R0111

(Disclaimer: The purpose of these AI-generated responses is just education and reference. Utilise them to grasp topics and structure, but always rewrite in your own words and double-check the content before submitting.)

ASSIGNMENT SOLUTION

Assignment – 1

Q-1: Explain the working principle of a p-n junction diode with neat diagrams.


Answer:

A p-n junction diode is formed by joining a p-type semiconductor (with holes as majority carriers) and an n-type semiconductor (with electrons as majority carriers). Its operation is governed by the behavior of the depletion region at the junction.

- **Unbiased Condition (Equilibrium):** At the instant of junction formation, electrons and holes diffuse across the junction, recombining with each other. This creates a region near the junction devoid of free charge carriers, known as the **Depletion Region**. This region contains immobile positive donor ions on the n-side and immobile negative acceptor ions on the p-side, creating an internal electric field and an associated **Barrier Potential** (~0.7 V for Si, ~0.3 V for Ge). This potential prevents further diffusion, establishing equilibrium.
- **Forward Bias:** When the positive terminal of a battery is connected to the p-side and the negative to the n-side, the applied external voltage opposes the internal barrier potential.
 - This reduces the width of the depletion region and the height of the barrier potential.
 - When the external voltage exceeds the barrier potential, a large current flows due to the uninhibited diffusion of majority carriers (holes from p-side and electrons from n-side).
- **Reverse Bias:** When the positive terminal is connected to the n-side and the negative to the p-side, the applied voltage supports the internal barrier potential.
 - This increases the width of the depletion region and the height of the barrier potential.

- The majority carriers are pulled away from the junction, preventing current flow. Only a very small, saturation current (I_S), due to minority carriers, flows. This current is temperature-dependent.

P-N Junction Diode Biasing

 


Q-2: Derive and explain the DC load line for a diode circuit.

Answer:

The DC load line is a graphical tool used to find the operating point (Q-point) of a nonlinear device (like a diode) in a linear circuit.

- **Circuit:** Consider a simple circuit with a DC voltage source V_S , a series resistor R , and a diode.
- **Derivation:** Applying Kirchhoff's Voltage Law (KVL) to the loop gives the equation: $V_S = I_D R + V_D$.
 - This equation has two variables, I_D and V_D . It is a linear equation.

- **Plotting the Load Line:** The load line is the graph of this KVL equation on the diode's I-V characteristic curve.
 - **X-intercept:** When $I_D = 0$, the equation becomes $V_S = V_D$. This point $(V_S, 0)$ is on the X-axis.
 - **Y-intercept:** When $V_D = 0$, the equation becomes $I_D = V_S/R$. This point $(0, V_S/R)$ is on the Y-axis.
- **The Q-Point:** The point where this straight load line intersects the nonlinear diode characteristic curve is the **Quiescent Point or Q-Point**. This point gives the exact current I_D and voltage V_D at which the diode operates for the given V_S and R .

 

Q-3: Compare ideal, practical, and real diode models.

Answer:

Feature	Ideal Diode Model	Practical Diode Model	Real Diode Model
Forward Voltage (V_F)	$V_F = 0\text{ V}$	$V_F = \text{Constant}$ (e.g., 0.7 V for Si)	$V_F = V_{constant} + (I_F \times R_S)$, where R_S is bulk resistance
Reverse Current (I_R)	$I_R = 0\text{ A}$	$I_R = 0\text{ A}$	I_R is a small, finite value (μA to nA)
Reverse Breakdown	Does not occur	Not considered	Considered; has a specific breakdown voltage V_{BR}
Analysis Complexity	Simplest; for quick estimations	Most commonly used; good balance of accuracy/simplicity	Most accurate; used for high-frequency/precision analysis

Q-4: Describe the temperature effect on a diode's characteristics.

Answer:

- **On Forward Voltage (V_F):** For a constant forward current, the forward voltage drop **decreases** with an increase in temperature. The temperature coefficient is approximately **-2.2 mV/°C** for a silicon diode.
- **On Reverse Saturation Current (I_S):** The reverse saturation current **increases** significantly with temperature. It approximately **doubles for every 10°C rise** in temperature.
- **On Breakdown Voltage (V_{BR}/V_Z):** The effect depends on the breakdown mechanism.
 - For **Zener diodes (low voltage, <5V)**, the breakdown voltage **decreases** with temperature (negative TC).
 - For **Avalanche diodes (high voltage, >7V)**, the breakdown voltage **increases** with temperature (positive TC).

Q-5: Write a short note on Zener diodes and their applications.

Answer:

A Zener diode is a specially fabricated p-n junction designed to operate reliably in the reverse breakdown region. The key feature is that the voltage across it (V_Z) remains nearly constant for a wide range of reverse currents.

Applications:

1. **Voltage Regulation:** Used as a shunt regulator to provide a stable DC output voltage from an unregulated power supply, despite variations in input voltage or load current.
2. **Voltage Reference:** Provides a precise and stable reference voltage in circuits like power supplies, analog-to-digital converters (ADCs), and voltage comparators.
3. **Overvoltage Protection:** Placed across a sensitive component, it clamps any transient voltage spikes to a safe level (V_Z), protecting the component.
4. **Waveform Clipping:** Used in wave-shaping circuits to limit the peak amplitude of a signal to the Zener voltage level.

Q-6: A silicon diode has a forward voltage drop of 0.7 V. Calculate the current through a series circuit with a 10 V source and a 1 k Ω resistor.

Answer:

- **Step 1:** Apply Kirchhoff's Voltage Law (KVL) to the series loop.
 - $V_{Source} - V_{Resistor} - V_{Diode} = 0$
- **Step 2:** Substitute the known values into the KVL equation.
 - $10\text{ V} - V_R - 0.7\text{ V} = 0$
- **Step 3:** Solve for the voltage across the resistor (V_R).
 - $V_R = 10\text{ V} - 0.7\text{ V}$
 - $V_R = 9.3\text{ V}$
- **Step 4:** Apply Ohm's Law to find the current (I) through the circuit.
 - $I = \frac{V_R}{R}$

- **Step 5:** Substitute the values to calculate the current.

- $I = \frac{9.3 \text{ V}}{1000 \Omega}$

- $I = 0.0093 \text{ A}$

- **Step 6:** Convert the current to milliamperes (mA).

- $I = 0.0093 \times 1000 = 9.3 \text{ mA}$

Final Answer: The current through the circuit is **9.3 mA**.

Q-7: For a Zener diode with $V_Z = 5.1 \text{ V}$ and load resistance $1 \text{ k}\Omega$, calculate the minimum series resistor required for a 12 V input to ensure regulation.

Answer:

- **Step 1:** State the standard assumption for minimum Zener current ($I_{Z(min)}$).

- Let $I_{Z(min)} = 5 \text{ mA}$.

- **Step 2:** Calculate the load current (I_L) using Ohm's Law.

- $I_L = \frac{V_Z}{R_L} = \frac{5.1 \text{ V}}{1000 \Omega}$

- $I_L = 0.0051 \text{ A} = 5.1 \text{ mA}$

- **Step 3:** Calculate the total current (I_S) that must flow through the series resistor (R_S).

- $I_S = I_L + I_{Z(min)}$

- $I_S = 5.1 \text{ mA} + 5 \text{ mA} = 10.1 \text{ mA}$

- **Step 4:** Calculate the voltage drop across the series resistor (V_{R_S}).

- $V_{R_S} = V_{in} - V_Z$

- $V_{R_S} = 12 \text{ V} - 5.1 \text{ V} = 6.9 \text{ V}$

- **Step 5:** Apply Ohm's Law to find the *maximum* allowable value of R_S .

- $R_{S(max)} = \frac{V_{R_S}}{I_S} = \frac{6.9 \text{ V}}{0.0101 \text{ A}}$

- $R_{S(max)} \approx 683.17 \Omega$

- **Step 6:** Select the nearest standard resistor value that is less than this calculated maximum to ensure the Zener current is always sufficient.

- A standard 680Ω resistor is suitable.

Final Answer: The minimum series resistor required (using standard value) is 680Ω .

Q-8: Compare half-wave and full-wave rectifiers. Derive efficiency and ripple factor.

Answer:


Parameter	Half-Wave Rectifier	Full-Wave Rectifier (Center-Tapped)
No. of Diodes	1	2
Transformer Requirement	Simple	Center-tapped
Average DC Voltage (V_{dc})	$V_{dc} = \frac{V_m}{\pi}$	$V_{dc} = \frac{2V_m}{\pi}$
RMS Voltage (V_{rms})	$V_{rms} = \frac{V_m}{2}$	$V_{rms} = \frac{V_m}{\sqrt{2}}$
Efficiency (η)	$\eta = \frac{P_{dc}}{P_{ac}} = \frac{(V_m/\pi)^2/R_L}{(V_m/2)^2/R_L} = \frac{4}{\pi^2} \approx 40.6\%$	$\eta = \frac{(2V_m/\pi)^2/R_L}{(V_m/\sqrt{2})^2/R_L} = \frac{8}{\pi^2} \approx 81.2\%$
Ripple Factor (γ)	$\gamma = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1} = \sqrt{\left(\frac{\pi}{2}\right)^2 - 1} \approx 1.21$	$\gamma = \sqrt{\left(\frac{\pi}{2\sqrt{2}}\right)^2 - 1} \approx 0.48$
Ripple Frequency	f (same as input)	$2f$ (twice the input)


Q-9: Explain the operation of Zener diode voltage regulator.**Answer:**

A Zener diode voltage regulator maintains a constant output voltage across a load, despite variations in the input voltage or the load current. It operates in the reverse breakdown region.

- **Circuit:** It consists of an unregulated DC input voltage (V_{in}), a current-limiting series resistor (R_S), and a Zener diode connected in parallel with the load resistor (R_L).
- **Principle of Operation:**
 1. **Constant Load, Varying Input Voltage:** If V_{in} increases, it tends to increase V_{out} . However, an increase in V_{out} (which is V_Z) causes a large increase in the Zener current (I_Z). The voltage drop across R_S ($I_S R_S$) increases, compensating for the rise in V_{in} , thus keeping V_{out} constant. The reverse happens if V_{in} decreases.
 2. **Constant Input, Varying Load:** If R_L decreases (load current I_L increases), I_S tends to increase, increasing the drop across R_S , which would tend to decrease V_{out} . However, a slight decrease in V_{out} causes a significant decrease in I_Z . This keeps the total current $I_S = I_Z + I_L$ relatively constant, and hence V_{out} remains stable.

Zener Shunt Regulator

 

 

Q-10: Describe RC and LC filters in power supply circuits.

Answer:

- **RC Filter:**

- **Construction:** A resistor (R) in series with the load, and a capacitor (C) in parallel with the load.
- **Operation:** The resistor limits the current flow, while the capacitor offers a very low impedance path (shunt) to the AC ripple component to ground. The smoothed DC appears across the capacitor and the load.
- **Advantages:** Simple, small size, low cost.
- **Disadvantages:** Poor voltage regulation due to voltage drop across R, low efficiency, suitable only for light load currents.

- **LC Filter (Choke Input Filter):**


- **Construction:** An inductor (L) in series with the load, and a capacitor (C) in parallel with the load.
- **Operation:** The inductor (choke) offers high impedance to the AC ripple and low resistance to DC. The capacitor further shunts the remaining AC ripple to ground.
- **Advantages:** Excellent ripple reduction, better voltage regulation than RC filter, high efficiency, suitable for heavy load currents.
- **Disadvantages:** Bulky, heavy, and more expensive.

Q-11: Draw and explain clipper and clamper circuits.


Answer:

- **Clipper (Limiter):** A clipper circuit removes or "clips off" a portion of the input waveform that exceeds a specific voltage level. It is used for waveform shaping and protection.
 - **Explanation:** A simple series clipper uses a diode. If the diode is in series with the input and a reference bias voltage, it will conduct only when the input voltage exceeds a certain level ($\text{bias} + V_F$), thereby clipping the peaks.
- **Clamper (DC Restorer):** A clamper circuit shifts the entire input waveform vertically, either up or down, to a desired DC level without distorting its shape. It is used in television receivers and test equipment.
 - **Explanation:** A clamper typically consists of a capacitor, a diode, and sometimes a DC bias source. The capacitor charges to the peak value of the input during one half-cycle and then acts as a battery, adding or subtracting this DC level to the input waveform in subsequent cycles.

Series Positive Clipper

 

Positive Clamper

 

Q-12: Design a Zener diode shunt regulator to maintain 5 V across a load of 1k ohm.

Answer:

Design Steps:

- **Step 1:** Define Parameters.
 - $V_{out} = V_Z = 5 \text{ V}$
 - $R_L = 1 \text{ k}\Omega$
 - Assume a nominal input voltage $V_{in} = 9 \text{ V}$
- **Step 2:** Assume a minimum Zener current for regulation.
 - $I_{Z(min)} = 5 \text{ mA}$
- **Step 3:** Calculate the load current (I_L).
 - $I_L = \frac{V_{out}}{R_L} = \frac{5 \text{ V}}{1000 \Omega} = 5 \text{ mA}$
- **Step 4:** Calculate the total current through R_S (I_S).
 - $I_S = I_L + I_{Z(min)} = 5 \text{ mA} + 5 \text{ mA} = 10 \text{ mA}$
- **Step 5:** Calculate the voltage drop across R_S (V_{R_S}).
 - $V_{R_S} = V_{in} - V_{out} = 9 \text{ V} - 5 \text{ V} = 4 \text{ V}$
- **Step 6:** Calculate the value of R_S .
 - $R_S = \frac{V_{R_S}}{I_S} = \frac{4 \text{ V}}{0.010 \text{ A}} = 400 \Omega$
- **Step 7:** Calculate the power rating for R_S .
 - $P_{R_S} = I_S^2 \times R_S = (0.01)^2 \times 400 = 0.04 \text{ W}$
 - Select a **400 Ω , 1/4 W (or 0.25 W)** resistor.
- **Step 8:** Select a Zener diode.
 - Choose a **5.1V Zener diode** (standard value).
 - Estimate maximum Zener current ($I_{Z(max)}$) when load is disconnected ($I_L = 0$) and V_{in} is maximum (assume $V_{in(max)} = 10\text{V}$).
 - $I_{S(max)} = \frac{V_{in(max)} - V_Z}{R_S} = \frac{10 - 5.1}{400} \approx 12.25 \text{ mA}$
 - With no load, all this current flows through the Zener: $I_{Z(max)} \approx 12.25 \text{ mA}$

- $P_Z = V_Z \times I_{Z(max)} = 5.1 \text{ V} \times 0.01225 \text{ A} \approx 0.0625 \text{ W}$
- Select a **5.1V, 1W** Zener diode for a good safety margin.

Final Design Summary:

- **Input Voltage (V_{in}):** 9 V
- **Series Resistor (R_S):** 400 Ω , 1/4 W
- **Zener Diode (D_Z):** 5.1 V, 1 W
- **Load Resistor (R_L):** 1 k Ω

Q-13: Write short note on Voltage Multiplier circuits.**Answer:**

Voltage multipliers are circuits that generate a high DC output voltage from a lower voltage AC source using a network of diodes and capacitors. They function by switching capacitors between parallel (charging) and series (discharging) connections with the voltage source.

- **Principle:** On one half-cycle of the AC input, capacitors are charged in parallel to the peak input voltage (V_m). On the opposite half-cycle, these charged capacitors are connected in series with each other and with the input source, effectively adding their voltages to produce an output that is a multiple of V_m .
- **Types:**
 - **Voltage Doubler:** Produces an output of $2V_m$. (e.g., Half-Wave Voltage Doubler).
 - **Voltage Tripler:** Produces an output of $3V_m$.
 - **Voltage Quadrupler:** Produces an output of $4V_m$.
- **Applications:** Used in applications requiring high voltage and low current, such as Cathode Ray Tubes (CRTs), photomultiplier tubes, X-ray systems, and laser equipment.

Assignment – 2

Q-1: What is a transistor? Explain different configurations of a transistor and their uses.

Answer:

A transistor is a three-terminal, semiconductor device used to amplify or switch electronic signals and electrical power. It is the fundamental building block of modern electronic devices.

Different Configurations and their Uses:

- **Common Emitter (CE):**
 - **Description:** The emitter terminal is common to both input and output.
 - **Characteristics:** High current gain, high voltage gain, high power gain, medium input impedance, medium output impedance, phase inversion between input and output.
 - **Uses:** Most widely used configuration for audio frequency amplifiers.
- **Common Base (CB):**
 - **Description:** The base terminal is common to both input and output.
 - **Characteristics:** Low current gain (<1), high voltage gain, high power gain, very low input impedance, very high output impedance, no phase inversion.
 - **Uses:** High-frequency applications, impedance matching, microphone preamplifiers.
- **Common Collector (CC) / Emitter Follower:**
 - **Description:** The collector terminal is common to both input and output.
 - **Characteristics:** High current gain, voltage gain ≈ 1 (slightly less), high power gain, very high input impedance, very low output impedance, no phase inversion.
 - **Uses:** Used as a buffer for impedance matching, in driver stages, and as a voltage regulator.

Q-2: What is bipolar junction transistor?**Answer:**

A Bipolar Junction Transistor (BJT) is a three-layer, three-terminal semiconductor device. It consists of two p-n junctions and is available in two types: NPN and PNP. The three terminals are the Emitter (E), Base (B), and Collector (C). It is called "bipolar" because both electrons and holes are involved in the current conduction process. Current flow is controlled by the injection of minority carriers across the base-emitter junction.

Q-3: What is power dissipated by transistor in active region?**Answer:**

The total power dissipated (P_D) by a transistor is the sum of the power dissipated at the collector-base junction and the base-emitter junction. Since the voltage across the base-emitter junction (V_{BE}) is very small compared to the collector-emitter voltage (V_{CE}), the power dissipation is approximately the product of the collector current and the collector-emitter voltage.

Formula:

$$P_D \approx V_{CE} \cdot I_C + V_{BE} \cdot I_B$$

For most practical purposes, as I_B is very small:

$$P_D \approx V_{CE} \cdot I_C$$

This power is dissipated as heat.

Q-4: Explain all types of transistor configurations?**Answer:**

(This is a repeat of Question 1. Please refer to the answer for Question 1 above.)

Q-5: What are α , β and γ in a transistor? Derive their values and relations between them.**Answer:**

These are the transistor's current gain parameters.

- **α (Alpha) - Common Base (CB) Current Gain:**

- **Definition:** The ratio of the collector current (I_C) to the emitter current (I_E).
- **Formula:** $\alpha = \frac{I_C}{I_E}$
- **Value:** Always less than 1, typically between 0.95 and 0.995.

- **β (Beta) - Common Emitter (CE) Current Gain:**

- **Definition:** The ratio of the collector current (I_C) to the base current (I_B).
- **Formula:** $\beta = \frac{I_C}{I_B}$
- **Value:** Typically ranges from 20 to 1000 for most transistors.

- **γ (Gamma) - Common Collector (CC) Current Gain:**

- **Definition:** The ratio of the emitter current (I_E) to the base current (I_B).
- **Formula:** $\gamma = \frac{I_E}{I_B}$

Relation Derivation:

We know from transistor physics: $I_E = I_C + I_B$

- **Relation between β and α :**

- Start with the definition of β : $\beta = \frac{I_C}{I_B}$
- From $I_E = I_C + I_B$, we get $I_B = I_E - I_C$
- Substitute I_B : $\beta = \frac{I_C}{I_E - I_C}$
- Divide numerator and denominator by I_E : $\beta = \frac{\frac{I_C}{I_E}}{\frac{I_E - I_C}{I_E}} = \frac{\alpha}{1 - \alpha}$
- **Therefore:** $\beta = \frac{\alpha}{1 - \alpha}$

- **Relation between γ and β :**

- Start with the definition of γ : $\gamma = \frac{I_E}{I_B}$
- From $I_E = I_C + I_B$, we get $\gamma = \frac{I_C + I_B}{I_B} = \frac{I_C}{I_B} + 1$
- **Therefore:** $\gamma = \beta + 1$

- **Relation between γ and α :**

- We have $\gamma = \beta + 1$ and $\beta = \frac{\alpha}{1-\alpha}$
- Substitute: $\gamma = \frac{\alpha}{1-\alpha} + 1 = \frac{\alpha+1-\alpha}{1-\alpha} = \frac{1}{1-\alpha}$
- **Therefore:** $\gamma = \frac{1}{1-\alpha}$

Q-6: Explain input output characteristics of CE configuration of BJT

Answer:

The Common Emitter (CE) characteristics describe how the BJT behaves in its most common amplifier configuration. They are divided into two graphs:

A) Input Characteristics:

- This is a plot of **Base Current (I_B)** versus **Base-Emitter Voltage (V_{BE})**, with **Collector-Emitter Voltage (V_{CE})** kept constant.
- The curve looks like a diode characteristic. For a fixed V_{CE} , I_B increases rapidly once V_{BE} exceeds the cut-in voltage ($\sim 0.5V$ for Si).
- As V_{CE} increases, the curve shifts slightly right because the wider depletion region reduces the effective base width, slightly lowering I_B for the same V_{BE} . For $V_{CE} > 1V$, the curves merge.


B) Output Characteristics:

- This is a plot of **Collector Current (I_C)** versus **Collector-Emitter Voltage (V_{CE})**, for different constant values of **Base Current (I_B)**.
- This family of curves defines three key regions of operation:
 1. **Active Region:** (The flat, horizontal zone)
 - The transistor acts as an **amplifier**.
 - I_C is controlled by I_B ($I_C \approx \beta I_B$) and is largely independent of V_{CE} .
 - BE junction is forward-biased; BC junction is reverse-biased.
 2. **Saturation Region:** (The steep, left-side zone)
 - The transistor acts as a **closed switch**.
 - I_C is maximum and determined by the external circuit (V_{CC} / R_C).

- Both BE and BC junctions are forward-biased.

 3. Cut-off Region: (The area near the X-axis where $I_B = 0$)

- The transistor acts as an **open switch**.
- I_C is nearly zero (only leakage current I_{CEO} flows).
- Both BE and BC junctions are reverse-biased.



Q-7: What is I_{CBO} and I_{CEO} in a transistor what is relation between I_{CEO} , I_{CBO} and I_{CO} ?

Answer:

- **I_{CBO} :** This is the **Reverse Saturation Current** flowing between the Collector and Base terminals when the emitter is open-circuited. It is the leakage current of the reverse-biased Collector-Base junction.
- **I_{CEO} :** This is the **Collector Cut-off Current** flowing between the Collector and Emitter terminals when the base is open-circuited. It is much larger than I_{CBO} .

Relation Derivation:

- When the base is open ($I_B = 0$), the transistor is not completely off. I_{CBO} flows from collector to base.
- This I_{CBO} acts as a base current for the transistor. Since the transistor is in the active region (collector reverse-biased, emitter forward-biased), this small base current gets amplified.
- The resulting collector current will be: $I_C = \beta I_B + I_{CBO}$
- With $I_B = 0$, the equation becomes: $I_C = I_{CEO} = \beta \cdot 0 + (\beta + 1)I_{CBO}$

- **Therefore, the relation is:** $I_{CEO} = (\beta + 1)I_{CBO}$

Note: I_{CO} is an older, sometimes used symbol for I_{CBO} . So, $I_{CEO} = (\beta + 1)I_{CO}$

Q-8: What are the different regions of operation of transistor?

Answer:

A BJT has three main regions of operation:

1. Active Region:

- **Biasing:** Base-Emitter junction is **Forward Biased**. Base-Collector junction is **Reverse Biased**.
- **Operation:** The transistor acts as an **Amplifier**. Collector current (I_C) is proportional to the base current (I_B), i.e., $I_C = \beta I_B$.

2. Saturation Region:

- **Biasing:** Both Base-Emitter and Base-Collector junctions are **Forward Biased**.
- **Operation:** The transistor acts as a **Closed Switch**. Maximum collector current flows. V_{CE} is very low, typically 0.2V ($V_{CE(sat)}$).

3. Cut-off Region:


- **Biasing:** Both Base-Emitter and Base-Collector junctions are **Reverse Biased**.
- **Operation:** The transistor acts as an **Open Switch**. Negligible collector current flows ($I_C \approx 0$). The entire supply voltage V_{CC} appears across the collector and emitter.

Q-9: What is DC load line? Explain with necessary diagram.

Answer:

The DC load line is a straight line drawn on the output characteristic curves (I_C vs. V_{CE}) of a transistor that represents all possible operating points (I_C , V_{CE}) for the given bias circuit and supply voltage under DC conditions.

- **Purpose:** It is used to find the Quiescent (Q-) point, which is the DC operating point of the transistor in the absence of an AC signal.
- **Equation:** For a simple common-emitter circuit with collector resistance R_C and supply voltage V_{CC} , the equation is derived from KVL: $V_{CC} = I_C R_C + V_{CE}$. This is a linear equation.
- **Plotting:**
 - **Point A (Saturation Point):** When $V_{CE} = 0$, $I_C = V_{CC}/R_C$. This point is on the Y-axis.
 - **Point B (Cut-off Point):** When $I_C = 0$, $V_{CE} = V_{CC}$. This point is on the X-axis.
 - The straight line connecting these two points is the DC Load Line.

 

Q-10: Why biasing is important in transistor? Explain voltage divider bias with diagram.

Answer:

Importance of Biasing:


Biasing is crucial to set a stable DC operating point (Q-point) in the active region of the transistor. This ensures that:

1. The transistor operates over the linear portion of its characteristic curve for faithful amplification without distortion.
2. The Q-point remains stable despite variations in temperature and transistor parameters (like β).

Voltage Divider Bias (or Emitter Bias):

This is the most widely used biasing circuit due to its excellent stability.

- **Circuit Description:** It uses two resistors (R_1 and R_2) connected in series across the supply voltage V_{CC} to form a voltage divider. This divider provides a fixed base voltage (V_B). An emitter resistor (R_E) is added for stability.
- **Operation:**
 1. The voltage divider provides a relatively constant base voltage V_B .
 2. The emitter voltage is $V_E = V_B - V_{BE}$.
 3. The emitter current is $I_E = V_E/R_E \approx I_C$.
 4. The collector voltage is $V_C = V_{CC} - I_C R_C$.
 5. If I_C tries to increase due to temperature, I_E increases, causing V_E to increase. Since V_B is fixed, the increase in V_E reduces the base-emitter voltage ($V_{BE} = V_B - V_E$), which in turn reduces the base current I_B , opposing the original increase in I_C . This is negative feedback, which stabilizes the Q-point.

 

Q-11: What is stability factor? Explain.

Answer:

The Stability Factor (S) is a measure of how effectively a biasing circuit can maintain the Q-point stable against variations in the transistor parameters, primarily the reverse saturation current (I_{CBO}) and the current gain (β).

- **Definition:** It is defined as the rate of change of collector current (I_C) with respect to the reverse saturation current (I_{CBO}), keeping β and V_{BE} constant.

$$S = \frac{\partial I_C}{\partial I_{CBO}}$$

- **Interpretation:**
 - A lower value of Stability Factor (S) indicates a more stable circuit.
 - **Ideal Value:** $S = 1$ (perfect stability, but not practically achievable).
 - **Worst Case:** For a fixed-bias circuit, $S = \beta + 1$ (highly unstable).
 - **Good Stability:** For a voltage divider bias circuit, the value of S is much lower, typically between 5 and 15, indicating very good stability.
- **The goal of biasing circuit design is to achieve a low Stability Factor.**

Assignment – 3


Q-1: Draw and explain the transistor AC equivalent circuit.

Answer:


To analyze the AC (small-signal) performance of an amplifier, we replace the transistor with a model consisting of resistors and controlled sources. This simplifies the analysis of gain, input, and output impedance.

- **Explanation:** The AC equivalent circuit is derived by:
 1. Short-circuiting all DC voltage sources (like V_{CC}).
 2. Short-circuiting all large capacitors (coupling and bypass capacitors), as they act as short circuits at signal frequencies.
 3. Replacing the transistor with its small-signal model (like the hybrid- π or h-parameter model).
- **Key Components in a Common Hybrid- π Model:**
 - **r_{π} (Input Resistance):** The resistance between base and emitter, seen by the AC signal. $r_{\pi} = \frac{\beta}{g_m}$.
 - **g_m (Transconductance):** Represents the amplification. The dependent current source is $g_m v_{be}$, which means the output collector current is proportional to the input base-emitter voltage.
 - **r_o (Output Resistance):** The internal resistance between collector and emitter, representing the Early Effect.

Original Amplifier Circuit

 

AC Equivalent Circuit (Hybrid- π Model)

 

Q-2: Explain coupling and bypass capacitor function in amplifiers.

Answer:

- **Coupling Capacitor (e.g., C_{in} , C_{out}):**
 - **Function:** To block the DC component of a signal while allowing the AC component to pass.
 - **Purpose:** It isolates the DC bias of one amplifier stage from the next, preventing the DC operating point (Q-point) of one stage from disturbing the other. It "couples" the AC signal from one stage to the next.
- **Bypass Capacitor (e.g., C_e across R_e):**
 - **Function:** To provide a low-impedance AC path to ground for a resistor.
 - **Purpose:** In a CE amplifier with an emitter resistor (R_e) for DC stability, the capacitor (C_e) is placed in parallel with it. For DC, the capacitor is open, so R_e provides negative feedback for Q-point stability. For AC, the capacitor shorts R_e , eliminating the AC negative feedback and thus maximizing the voltage gain of the amplifier.

Q-3: Which are the transistor models for the small signal a.c. analysis? Explain hybrid model for any transistor configuration.

Answer:

The two main transistor models for small-signal AC analysis are:

1. **The h-parameter (Hybrid) model.**

2. The hybrid- π model.

Explanation of the h-parameter model for a Common Emitter configuration:

This model represents the transistor as a two-port network with input and output voltages and currents related by a set of parameters called h-parameters.

- **Input Equation:** $V_1 = h_{ie}I_1 + h_{re}V_2$
- **Output Equation:** $I_2 = h_{fe}I_1 + h_{oe}V_2$

Where for a CE configuration:

- h_{ie} : Short-circuit input impedance (Ω). It is the resistance seen looking into the base.
- h_{re} : Open-circuit reverse voltage gain (unitless). It gives the feedback effect of output voltage on input voltage.
- h_{fe} : Short-circuit forward current gain (β , unitless). This is the most important parameter, representing the current amplification.
- h_{oe} : Open-circuit output admittance ($1/\Omega$). It is the output conductance.

In practice, for simplified analysis, h_{re} is considered negligible (≈ 0) and h_{oe} is neglected if the load resistance is much smaller than $1/h_{oe}$.

Q-4: What is the a.c. load line in the transistor? Write its significance.

Answer:

- **Definition:** The AC load line is a straight line drawn on the output characteristic curves (I_c vs. V_{ce}) that represents all possible instantaneous operating points when an AC signal is applied. Its slope is determined by the total AC load resistance seen by the collector, which is often the parallel combination of R_c and the external load R_L ($R_{ac} = R_c \parallel R_L$).
- **Significance:**
 1. It determines the **maximum undistorted output voltage swing**.
 2. It shows how the collector current (i_c) and collector-emitter voltage (v_{ce}) vary with the AC signal around the Q-point.
 3. For maximum symmetrical swing (to avoid clipping), the Q-point should be positioned at the **center of the AC load line**.

Q-5: Explain common Emitter amplifier.

Answer:

The Common Emitter (CE) amplifier is the most widely used transistor amplifier configuration due to its high voltage and current gain.

- **Configuration:** The input signal is applied to the base, the output is taken from the collector, and the emitter is common to both (often connected to ground via a capacitor for AC signals).
- **Characteristics:**
 - **High Voltage Gain:** Provides a large inverted (180° phase shift) output voltage relative to the input.
 - **High Current Gain:** Current gain is approximately β .
 - **High Power Gain:** Product of voltage and current gain.
 - **Moderate Input Impedance.**
 - **Moderate Output Impedance.**
- **Usage:** It is the workhorse of audio and general-purpose voltage amplification stages.

Q-6: Explain the working of transistor as a switch.

Answer:

A transistor operates as a switch by alternating between its **Cut-off** and **Saturation** regions.

- **OFF State (Cut-off):**
 - **Condition:** The base-emitter voltage (V_{be}) is less than the cut-in voltage ($\sim 0.5V$ for Si). Effectively, base current $I_b \approx 0$.
 - **Operation:** The transistor is off. No collector current flows ($I_c \approx 0$). The full supply voltage V_{cc} appears across the collector and emitter ($V_{ce} \approx V_{cc}$). It acts as an **open switch**.
- **ON State (Saturation):**
 - **Condition:** A sufficient base current ($I_b > I_b(\min) = I_c(\text{sat})/\beta$) is applied to fully turn on the transistor.

- **Operation:** The transistor is driven into saturation. Maximum collector current flows, limited by the external resistor and supply voltage ($I_{c(sat)} \approx V_{cc} / R_c$). The voltage V_{ce} drops to a very low value, $V_{ce(sat)} (\sim 0.2V)$. It acts as a **closed switch**.

Q-7: Compare CE, CB and CC configurations.

Answer:

Parameter	Common Emitter (CE)	Common Base (CB)	Common Collector (CC) / Emitter Follower
Input Impedance	Medium (a few $k\Omega$)	Very Low (a few tens of Ω)	Very High (a few hundred $k\Omega$)
Output Impedance	Medium ($\approx R_c$)	Very High (a few hundred $k\Omega$)	Very Low (a few tens of Ω)
Voltage Gain	High ($\approx -gmR_c$)	High ($\approx gmR_c$)	Approximately 1 (slightly less)
Current Gain	High (β)	Low ($\alpha \approx 1$)	High ($\beta + 1$)
Power Gain	Highest	High	Medium
Phase Shift	180°	0°	0°
Application	Voltage Amplifier	High-Frequency Circuits, Current Buffer	Impedance Matching, Voltage Buffer

Assignment – 4

Q-1: Explain JFET construction and characteristics.

Answer:


A Junction Field-Effect Transistor (JFET) is a voltage-controlled, unipolar semiconductor device.

- **Construction:**

- It is made from a bar of n-type or p-type semiconductor, called the **channel** (n-channel or p-channel).
- The ends of the channel are called the **Drain (D)** and **Source (S)**.
- The **Gate (G)** is formed by heavily doping the opposite type of semiconductor (p-type for n-channel, n-type for p-channel) on the sides of the channel, creating two p-n junctions.
- The channel's conductivity is controlled by the width of the depletion region of these p-n junctions.

- **Characteristics:**

- **Output Characteristics (I_D vs. V_{DS}):** This plot shows a family of curves for different V_{GS} values.
 - **Ohmic/Linear Region:** At low V_{DS} , I_D increases linearly with V_{DS} . The channel acts like a voltage-controlled resistor.
 - **Saturation/Pinch-off Region:** As V_{DS} increases, the depletion regions widen near the drain, "pinching" the channel. I_D becomes constant and is controlled primarily by V_{GS} . This is the amplifier region.
 - **Breakdown Region:** At very high V_{DS} , the p-n junction breaks down, and I_D increases rapidly.
- **Transfer Characteristic (I_D vs. V_{GS}):** This shows how I_D decreases as V_{GS} becomes more negative (for n-channel), following the relation: $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$. Here, I_{DSS} is the drain current when $V_{GS} = 0$, and V_P is the pinch-off voltage.

 

Q-2: Write short note on E-type MOSFET.

Answer:

- **Full Name:** Enhancement-Type Metal-Oxide-Semiconductor Field-Effect Transistor.
- **Construction:** It has no pre-defined channel. The drain and source are two heavily doped regions of one type (e.g., n⁺ for n-MOS), separated by a lightly doped substrate of the opposite type (p-type for n-MOS). The gate is insulated from the substrate by a thin layer of silicon dioxide (SiO₂).
- **Operation:**
 - At $V_{GS} = 0$, no channel exists, so no current flows between drain and source ($I_D = 0$).
 - When a positive V_{GS} (for n-MOS) is applied, it repels holes and attracts electrons to the surface under the oxide, forming an **inversion layer** or "n-channel".
 - This induced channel connects the drain and source, allowing current (I_D) to flow when V_{DS} is applied.
 - The minimum V_{GS} required to form the channel is called the **Threshold Voltage (V_{TH})**.

Q-3: What are the advantages of N-channel MOSFET over P-channel MOSFET?

Answer:

- **Higher Mobility:** Electrons (charge carriers in n-channel) have higher mobility than holes (charge carriers in p-channel). This makes n-channel MOSFETs faster and can carry more current for the same physical size.
- **Lower On-Resistance ($R_{DS(on)}$):** Due to higher electron mobility, n-channel MOSFETs have a lower resistance when turned on, leading to higher efficiency and less power loss.
- **Smaller Size:** For the same current rating, an n-channel MOSFET can be made smaller than a p-channel one.
- **Cost-Effectiveness:** They are cheaper to manufacture for a given performance level.

Q-4: Compare BJT, FET and JFET

Answer:

Parameter	BJT (Bipolar)	JFET (Junction)	MOSFET (Metal-Oxide)
Charge Carriers	Both electrons & holes (Bipolar)	Majority only (Unipolar)	Majority only (Unipolar)
Control Mechanism	Current-controlled (I_B)	Voltage-controlled (V_{GS})	Voltage-controlled (V_{GS})
Input Impedance	Low	Very High	Extremely High
Switching Speed	Medium	Fast	Very Fast
Noise	Higher	Lower	Lowest
Thermal Stability	Poor	Better	Good

Parameter	BJT (Bipolar)	JFET (Junction)	MOSFET (Metal-Oxide)
Fabrication / Size	Larger	Smaller	Smallest (VLSI)

Q-5: Differentiate between JFET and MOSFET..

Answer:

Feature	JFET	MOSFET
Gate Structure	p-n Junction	Metal-Oxide-Semiconductor (Insulated Gate)
Input Impedance	Very High ($\sim 10^9 \Omega$)	Extremely High ($\sim 10^{10}$ to $10^{15} \Omega$)
Mode of Operation	Depletion-only	Depletion & Enhancement types available
Gate Current	Small leakage current	Negligible (almost zero)
Handling Static Electricity	Less sensitive	Very sensitive (can be damaged easily by ESD)
Cost	Low	Very Low (for mass production)

Q-6: Explain FET as an amplifier.

Answer:

A FET (JFET or MOSFET) can be used as a voltage amplifier in the **saturation (active) region**.

- **Principle:** A small change in the input voltage (V_{gs}) causes a large change in the output drain current (I_d). This varying current is passed through a drain resistor (R_D), producing a large, inverted output voltage swing (V_{ds}) across it.
- **Voltage Gain (A_v):** The voltage gain is given by $A_v = -g_m R_D$, where:
 - g_m is the **transconductance**, which measures how effectively the input voltage controls the output current.
 - R_D is the drain resistor.
 - The negative sign indicates a 180° phase inversion between input and output (for Common Source configuration).

Q-7: Define following for FET : a) transconductance b) Pinch-off voltage c) Drain resistance d) Amplification factor e) Power dissipation

Answer:

- **a) Transconductance (g_m):** It is the ratio of the change in drain current (ΔI_D) to the change in gate-source voltage (ΔV_{GS}) that caused it, with V_{DS} kept constant. $g_m = \frac{\Delta I_D}{\Delta V_{GS}} \Big|_{V_{DS}=\text{constant}}$. Unit: Siemens (S) or mho.
- **b) Pinch-off Voltage (V_P):** For a JFET, it is the gate-source voltage (V_{GS}) at which the drain current (I_D) becomes essentially zero (the channel is fully pinched off).
- **c) Drain Resistance (r_d):** The ratio of the change in drain-source voltage (ΔV_{DS}) to the change in drain current (ΔI_D), with V_{GS} kept constant. $r_d = \frac{\Delta V_{DS}}{\Delta I_D} \Big|_{V_{GS}=\text{constant}}$. It is the AC output resistance.
- **d) Amplification Factor (μ):** It is the ratio of the change in drain-source voltage (ΔV_{DS}) to the change in gate-source voltage (ΔV_{GS}) that maintains a constant drain current (I_D). $\mu = -\frac{\Delta V_{DS}}{\Delta V_{GS}} \Big|_{I_D=\text{constant}}$. It is related by $\mu = g_m \cdot r_d$.
- **e) Power Dissipation (P_D):** The maximum power the device can safely dissipate as heat, given by $P_D = V_{DS} \cdot I_D$.

Q-8: Write advantages and disadvantages of FET over BJT.

Answer:

- **Advantages:**

1. **Very High Input Impedance:** Draws negligible gate current, making it ideal for interfacing with sensors and high-impedance sources.
2. **Voltage-Controlled Device:** Easier to bias and interface with digital circuits.
3. **Lower Noise:** Better for low-noise amplifier input stages.
4. **Thermal Stability:** Less prone to thermal runaway.
5. **Higher Efficiency:** Can be made with very low on-resistance, leading to high switching efficiency.

- **Disadvantages:**

1. **Lower Gain-Bandwidth Product:** Generally slower than BJTs at very high frequencies (though MOSFETs excel in high-speed switching).
2. **Higher Cost** for high-power, high-frequency applications.
3. **ESD Sensitivity:** MOSFETs are easily damaged by electrostatic discharge.

Q-9: What is the different method for biasing the transistor? Explain any two methods with necessary circuit diagram.

Answer:

Common biasing methods for FETs are:


1. Fixed Bias
2. Self-Bias
3. Voltage Divider Bias
4. Source Bias

Explanation of Two Methods:

 1. Self-Bias (for JFET):


- **Circuit:** A resistor (R_S) is connected in series with the source terminal. The gate is connected to ground through a high-value resistor (R_G), making $V_G = 0V$.

- Operation:** Drain current (I_D) flows through R_S , developing a voltage $V_S = I_D R_S$. Since $V_G = 0$, the gate-source voltage is $V_{GS} = V_G - V_S = -I_D R_S$. This negative V_{GS} sets up the required reverse bias automatically. It provides good stability.



 2. Voltage Divider Bias (for MOSFET):

- Circuit:** Similar to BJT. Two resistors (R_1 and R_2) form a voltage divider from V_{DD} to ground, setting the gate voltage $V_G = V_{DD} \frac{R_2}{R_1 + R_2}$. A source resistor (R_S) is also used.
- Operation:** The gate voltage V_G is fixed by the divider. The source voltage is $V_S = I_D R_S$. Therefore, the gate-source voltage is $V_{GS} = V_G - V_S$. This method provides very stable Q-point and is commonly used with Enhancement MOSFETs.



Assignment – 5

Q-1: Explain the working principle of an LED and discuss its advantages and limitations in various applications.

Answer:

- **Working Principle:** A Light Emitting Diode (LED) is a p-n junction diode made from a direct bandgap semiconductor (like GaAs, GaP). When it is **forward-biased**, electrons from the n-region cross the junction and recombine with holes in the p-region. During this recombination process, the excess energy is released in the form of **photons** (light). The color of the emitted light depends on the bandgap energy of the semiconductor material used.
- **Advantages:**
 - **High Efficiency:** Converts a high percentage of electrical energy directly into light, minimizing heat loss.
 - **Long Lifespan:** Lasts significantly longer (50,000+ hours) than incandescent or fluorescent bulbs.
 - **Small Size & Ruggedness:** Solid-state construction makes them durable and very compact.
 - **Fast Switching Speed:** Can be turned on and off extremely quickly, useful for communication.
 - **Low Voltage & Current Operation:** Safe for low-power applications.
- **Limitations:**
 - **Higher Initial Cost:** More expensive to manufacture than traditional light sources.
 - **Temperature Sensitivity:** Performance and lifespan can degrade at high temperatures.
 - **Requires Precise Drive Current:** Needs a constant current source to prevent damage from current spikes.

Q-2: Explain the working principle of photodiodes.

Answer:


A photodiode operates in **reverse bias** mode. When light (photons) with energy greater than the material's bandgap strikes the depletion region, it generates electron-hole pairs. The strong electric field in the reverse-biased depletion region swiftly sweeps these charge carriers across the junction. This movement of carriers constitutes a **reverse current** (known as photocurrent) that is proportional to the intensity of the incident light. In essence, it converts light energy directly into electrical current.

Q-3: Explain the working principle of solar cell with necessary diagram..

Answer:

A solar cell is essentially a large-area **photodiode operated without an external bias**, in **photovoltaic mode**.

- **Working Principle:** It uses a p-n junction. When light photons strike the cell, they generate electron-hole pairs in the depletion region. The built-in electric field of the junction then separates these charges, pushing electrons toward the n-side and holes toward the p-side. This creates a potential difference (voltage) between the two layers. When an external load is connected, a direct current (DC) flows, powering the load.

 

Q-4: Explain the working of PIN diode.

Answer:

A PIN diode has a three-layer structure: p-type, **intrinsic** (undoped), and n-type. The intrinsic region is much wider than the p and n regions.

- **Working:**

- **Forward Bias:** Holes and electrons are injected from the p and n regions into the intrinsic layer. This makes it an excellent **conductor**, acting like a variable resistor controlled by the forward current.
- **Reverse Bias:** The intrinsic region gets depleted, making the diode a very good **insulator** with a constant, low capacitance.
- **Applications:** Used as a **RF switch**, **photodetector**, and in **attenuator circuits** due to its variable resistance characteristic.

Q-5: Explain the working of Varactor diode.

Answer:

A Varactor diode, or varicap diode, is a p-n junction diode operated under **reverse bias**.

- **Working:** In reverse bias, the depletion region acts as an insulator between the p and n regions, which act as capacitor plates. The width of this depletion region (and hence the **capacitance**) changes with the applied reverse voltage. A higher reverse voltage widens the depletion region, **decreasing the capacitance**, and vice-versa.
- **Application:** It is used as a **voltage-controlled capacitor** in electronic tuning circuits for oscillators, filters, and phase-locked loops (PLLs).

Q-6: Explain the working of Schottky diode.

Answer:

A Schottky diode is formed by a metal-semiconductor junction (e.g., metal and n-type silicon), instead of a p-n junction.

- **Working:** When forward-biased, electrons (majority carriers) are injected from the n-type semiconductor into the metal. Since there is no minority carrier injection and storage (as in a p-n junction), the diode can switch between on and off states very rapidly.
- **Key Features:**
 - **Very fast switching speed.**
 - **Lower forward voltage drop** (~0.15-0.3 V) than a silicon p-n junction diode.

- **Application:** Used in high-frequency applications, RF mixers, power rectifiers, and as clamping diodes in digital circuits.

Q-7: Explain the working of Tunnel diode.

Answer:

A Tunnel diode is a heavily doped p-n junction diode.


- **Working:** Due to extreme doping, the depletion region is very narrow. This allows electrons to "tunnel" through the potential barrier via a quantum mechanical effect, even when the forward bias is very low. This tunneling current causes a region in its I-V characteristic where an **increase in voltage leads to a decrease in current**, known as the **Negative Resistance Region**.
- **Application:** Used in high-frequency oscillators and microwave amplifiers because of its negative resistance property.

Q-8: Explain working of seven segment display

Answer:

A seven-segment display is an assembly of **seven Light Emitting Diodes (LEDs)** arranged in a specific pattern (like the number '8').

- **Working:** Each of the seven LEDs is labeled from 'a' to 'g'. By forward-biasing different combinations of these segments, different numerals (0-9) and some letters can be displayed. For example, to display the number '7', segments a, b, and c are lit up.
- **Types:**
 - **Common Anode (CA):** All anodes of the LEDs are connected to a common positive voltage. Segments are lit by applying a ground (low) signal to their cathodes.
 - **Common Cathode (CC):** All cathodes are connected to a common ground. Segments are lit by applying a positive voltage (high) to their anodes.

 

COMMON ANODE

COMMON CATHCODE

