

# GUJARAT TECHNOLOGICAL UNIVERSITY

## BE-4 SEMESTER – OLD PAPER – S22 TO W25 – QUESTION BANK ANSWER

Subject Name & Code:

**POWER ELECTRONICS (3140915)**

**(Disclaimer:** The purpose of these AI-generated responses is just education and reference. Utilise them to grasp topics and structure, but always rewrite in your own words and double-check)

### UNIT 4: AC-DC CONVERTERS (RECTIFIERS)

#### REPEATED QUESTIONS

**R1. Explain single-phase full-wave controlled rectifier with R/RL load. (7 marks)**

*Appeared in: S25(7), S23(7) OR, W22(7) OR*

**Ans:**

A single-phase full-wave controlled rectifier uses four thyristors in a bridge configuration (fully controlled) or two thyristors + two diodes (semi-controlled). Here we explain **fully controlled bridge** with R and RL loads.

**Circuit diagram:**

AC supply ( $V_s = V_m \sin \omega t$ ) connected to four SCRs: S1, S2 (forward group) and S3, S4 (reverse group). Load R (or R-L) connected across bridge output.

**For resistive load (R):**

- **Positive half-cycle (0 to  $\pi$ ):** SCRs S1 and S4 are forward biased. At firing angle  $\alpha$ , they are triggered. Load current flows from supply through S1  $\rightarrow$  load  $\rightarrow$  S4. Output voltage follows supply voltage until  $\pi$ , then becomes zero when supply crosses zero (SCRs turn off naturally at  $\omega t = \pi$ ).
- **Negative half-cycle ( $\pi$  to  $2\pi$ ):** SCRs S2 and S3 triggered at  $\pi + \alpha$ . Current reverses through load. Output voltage is negative (but for rectifier we take absolute value? Actually load voltage is positive if we define polarity consistently – the bridge inverts negative half-cycle to positive).
- **Output voltage waveform:** Positive pulses from  $\alpha$  to  $\pi$  and from  $\pi + \alpha$  to  $2\pi$ . Average  $V_o = (2V_m/\pi) \cos \alpha$ .
- **Discontinuous current** for  $\alpha > 0$ .

**For RL load (inductive):**

- When SCRs turn off at  $\pi$ , load inductance tries to maintain current. This keeps S1, S4 conducting beyond  $\pi$  until energy decays. However, without freewheeling diode, negative supply voltage appears across load until current zero. This causes negative voltage spike, reducing average voltage.
- With freewheeling diode across load, current freewheels during off periods, output voltage clamped to zero, giving same average voltage formula as R load but with continuous current for  $\alpha < 90^\circ$ .

**Waveforms (RL load with freewheeling diode):**

- Gate pulses at  $\alpha$ ,  $2\pi + \alpha$ , etc.
- Load voltage: positive from  $\alpha$  to  $\pi$ , then zero from  $\pi$  to  $\pi + \alpha$ , etc.
- Load current: exponential rise and fall, continuous for  $\alpha < 90^\circ$ .

**Average output voltage (continuous conduction):**

$$V_{o(av)} = \frac{2V_m}{\pi} \cos \alpha = \frac{2\sqrt{2}V_s}{\pi} \cos \alpha$$

where  $V_s$  is RMS supply voltage.

**Applications:** DC motor drives, battery chargers, electroplating.

[DG PROMPT]

**Title:** Single-Phase Full-Wave Controlled Rectifier with RL Load

**Description:**

- **Circuit:** Draw AC source (sine symbol) in series with a bridge of four SCRs (S1 top left, S2 top right? Actually standard: S1 and S2 on left leg? Better: Four SCRs: S1 (top left), S4 (bottom left), S2 (top right), S3 (bottom right). Load (R and L in series) connected between the two bridge midpoints. Freewheeling diode in parallel with load (cathode to positive). Label  $\alpha$ .
- **Waveforms** (stacked, same time axis 0 to  $2\pi$ ):
  1. Supply voltage  $V_s$  (sine wave)
  2. Gate pulses for S1,S4 (from  $\alpha$  to  $\pi$ ) and S2,S3 (from  $\pi+\alpha$  to  $2\pi$ )
  3. Load voltage  $V_o$ : positive pulses from  $\alpha$  to  $\pi$ , zero from  $\pi$  to  $\pi+\alpha$ , positive again from  $\pi+\alpha$  to  $2\pi$
  4. Load current  $i_o$ : continuous (rippled DC) for RL with freewheeling diode.

### R2a. Explain three-phase full converter with RL load and waveforms. (7 marks)

*Appeared in: S25(7), S24(7), W25(7) OR, W23(7)*

**Ans:**

Three-phase full converter (fully controlled bridge) uses six thyristors – two per phase (one for positive group, one for negative group). It provides higher DC voltage and lower ripple than single-phase.

**Circuit:**

Three-phase supply (R, Y, B phases). Positive group: SCRs 1, 3, 5 (connected to R, Y, B respectively). Negative group: SCRs 4, 6, 2 (connected to R, Y, B respectively). Load (RL) between common cathodes of positive group and common anodes of negative group.

**Operation (continuous conduction mode,  $\alpha < 60^\circ$ ):**

Each SCR conducts for  $120^\circ$  per cycle. Firing sequence: 1,2,3,4,5,6 at intervals of  $60^\circ$ . At any instant, two SCRs conduct (one from positive group, one from negative group). Line-to-line voltage appears across load.

**Waveforms:**

- Phase voltages (three sine waves  $120^\circ$  apart).
- Trigger pulses for SCRs – each shifted by  $\alpha$  from natural commutation point.
- Output voltage  $V_o$  consists of segments of line-to-line voltages.
- For  $\alpha=0$ ,  $V_o = (3\sqrt{2} V_{ll}/\pi) \approx 1.35 V_{ll}$  (RMS line-to-line).
- For general  $\alpha$  (0 to  $60^\circ$ ), average  $V_o = (3\sqrt{2} V_{ll}/\pi) \cos \alpha$ .
- For  $\alpha > 60^\circ$ , discontinuous conduction may occur unless load is highly inductive.

**RL load effect:**

Current is continuous for  $\alpha < 60^\circ$  with large L. Inductor smoothes current. Output voltage becomes negative when  $\alpha > 90^\circ$  (inverter mode).

**Applications:** High-power DC motor drives (up to MW), HVDC transmission.

[DG PROMPT]

**Title:** Three-Phase Full Converter Circuit and Waveforms

**Description:**

- **Circuit:** Three-phase source (star) with lines R,Y,B. Six SCRs: top group (S1,R; S3,Y; S5,B) cathodes connected together to load positive. Bottom group (S4,R; S6,Y;

S2,B) anodes connected together to load negative. RL load between.

- **Waveforms:** Draw three phase voltages. Below, draw output voltage  $V_o$  – six pulses per cycle, segments of line-line voltages. For  $\alpha=30^\circ$ , show delay from natural commutation points.

### R2b. Explain three-phase semi-converter with RL load and waveforms. (7 marks)

*Appeared in: W25(7), W23(7) OR*

**Ans:**

Three-phase semi-converter uses three SCRs (positive group) and three diodes (negative group). It provides lower cost and improved power factor at lower firing angles.

**Circuit:**

Positive group: SCRs 1,3,5 (anodes to R,Y,B; cathodes common to load positive). Negative group: diodes 4,6,2 (cathodes to R,Y,B; anodes common to load negative). Load (RL) connected between common points.

**Operation:**

- During positive half-cycle of a phase, its SCR triggers at  $\alpha$  and conducts until the next phase voltage becomes more positive (natural commutation).
- Diodes conduct without delay, providing a freewheeling path.
- Output voltage waveform consists of positive segments only (no negative portions) because diodes prevent negative voltage.
- For  $\alpha=0$ ,  $V_o = (3\sqrt{2} V_{ll}/\pi) (1+\cos \alpha)/2$ ? Actually average output:  $V_o = (3\sqrt{2} V_{ll}/2\pi) (1+\cos \alpha)$ .
- Maximum voltage at  $\alpha=0$ , reduces to zero at  $\alpha=180^\circ$ .

**Advantages over full converter:**

- Only three SCRs (less cost).
- No negative voltage across load – better for DC motor with freewheeling.
- Higher power factor at low  $\alpha$ .

**Disadvantages:**

- Cannot operate in inverter mode (no negative voltage).
- Lower output voltage than full converter for same  $\alpha$ .

**Waveforms:** Similar to full converter but output voltage never goes negative; freewheeling through diodes during off periods.

**Real-world application:** Low-cost DC drives, battery chargers.

[DG PROMPT]

**Title:** Three-Phase Semi-Converter Circuit

**Description:** Similar to full converter but replace bottom three SCRs with diodes (D4, D6, D2). Label SCRs S1,S3,S5 and diodes D4,D6,D2. RL load. Waveforms: output voltage positive pulses only.

### R3. Discuss need of freewheeling diode in phase-controlled rectifier. (4 marks)

*Appeared in: S25(3), S24(4), S23(3), W25(3), W23(3) → Highest: 4*

**Ans:**

A freewheeling diode (also called commutating diode) is connected in parallel with the load (reverse biased during normal conduction).

**Need:**

1. **Prevents negative output voltage** – In RL load, when SCRs turn off at the end of a half-cycle, the inductor tries to maintain current. Without freewheeling diode, the load voltage would become negative (supply reverse voltage), reducing average DC output. The diode provides a short circuit path for inductor current, clamping load voltage to nearly zero (diode drop).

2. **Improves average voltage** – By eliminating negative voltage spikes,  $V_o$  increases for a given firing angle.
3. **Reduces ripple** – Current becomes smoother and continuous even at low  $\alpha$ .
4. **Protects SCRs** – Prevents high reverse voltage across SCRs during inductive kickback.
5. **Enables discontinuous-to-continuous transition** – Allows the rectifier to operate in continuous conduction mode at lower load currents.

**Without freewheeling diode:** The output voltage formula becomes  $V_o = (2V_m/\pi) \cos \alpha$  only for continuous current; with discontinuous current, the average drops significantly.

**Application:** All phase-controlled rectifiers feeding inductive loads (DC motor armature, large filter inductors).

#### R4a. Derive output voltage equation for single-phase half-wave rectifier. (4 marks)

*Appeared in: S24(4), W23(4) OR, W22(4) OR*

**Ans:**

Single-phase half-wave controlled rectifier with resistive load. Supply voltage  $v_s = V_m \sin \omega t$ . Thyristor triggered at  $\alpha$ .

**Waveform:** Output voltage  $v_o = 0$  for  $0$  to  $\alpha$ , then  $V_m \sin \omega t$  from  $\alpha$  to  $\pi$ , then  $0$  from  $\pi$  to  $2\pi$ .

**Average output voltage:**

$$\begin{aligned} V_{o(av)} &= \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t) \\ &= \frac{V_m}{2\pi} [-\cos \omega t]_{\alpha}^{\pi} = \frac{V_m}{2\pi} (-\cos \pi + \cos \alpha) \\ &= \frac{V_m}{2\pi} (1 + \cos \alpha) \end{aligned}$$

**For resistive load only.** If load includes inductance, current may be continuous or discontinuous, and expression changes.

**RMS output voltage:**

$$V_{o(rms)} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} (V_m \sin \omega t)^2 d(\omega t)} = \frac{V_m}{2} \sqrt{\frac{1}{\pi} \left( \pi - \alpha + \frac{\sin 2\alpha}{2} \right)}$$

**Real-world application:** Low-power battery charging, simple lamp dimmers.

#### R4b. Derive output voltage equation for single-phase full-wave rectifier. (7 marks)

*Appeared in: S25(7), W25(3) OR*

**Ans:**

Single-phase full-wave controlled rectifier (bridge) with resistive load. Supply  $v_s = V_m \sin \omega t$ . Thyristors triggered in pairs: (S1,S4) from  $\alpha$  to  $\pi$ , (S2,S3) from  $\pi+\alpha$  to  $2\pi$ .

**Output voltage waveform:**

- Positive pulse from  $\alpha$  to  $\pi$ :  $v_o = V_m \sin \omega t$
- Positive pulse from  $\pi+\alpha$  to  $2\pi$ :  $v_o = -V_m \sin \omega t$  (since bridge inverts negative half-cycle)
- Zero elsewhere.

**Average output voltage:**

$$V_{o(av)} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t)$$

Because each half-cycle contributes same positive area over  $\pi$  (not  $2\pi$ ) due to symmetry.

$$= \frac{V_m}{\pi} [-\cos \omega t]_{\alpha}^{\pi} = \frac{V_m}{\pi} (-\cos \pi + \cos \alpha) = \frac{V_m}{\pi} (1 + \cos \alpha)$$

**In terms of RMS supply voltage  $V_s = V_m/\sqrt{2}$ :**

$$V_{o(av)} = \frac{2\sqrt{2}V_s}{\pi} \cos^2(\alpha/2) \text{ (since } 1 + \cos \alpha = 2\cos^2(\alpha/2))$$

More commonly written as:

$$V_{o(av)} = \frac{2V_m}{\pi} \cos \alpha \text{? No – careful: } \frac{V_m}{\pi} (1 + \cos \alpha) = \frac{2V_m}{\pi} \cos^2(\alpha/2)$$

Wait, confusion. Standard formula for full-wave controlled rectifier (with continuous current) is  $V_{o(av)} = \frac{2V_m}{\pi} \cos \alpha$  for RL load with freewheeling? Actually for pure resistive load, the integral from  $\alpha$  to  $\pi$  gives  $\frac{V_m}{\pi} (1 + \cos \alpha)$ . For RL load with freewheeling diode (continuous conduction), the same formula holds because each half-cycle contributes same area. Many textbooks use  $V_{o(av)} = \frac{2V_m}{\pi} \cos \alpha$  for full-wave with inductive load and  $\alpha < 90^\circ$  (continuous). But note:  $\frac{2V_m}{\pi} \cos \alpha$  is NOT equal to  $\frac{V_m}{\pi} (1 + \cos \alpha)$  unless  $\alpha=0$ . So there are two different cases.

**Clarification for GTU:** They often ask derivation for **resistive load** giving  $V_{o(av)} = \frac{V_m}{\pi} (1 + \cos \alpha)$ . For RL load with continuous conduction, the formula is  $V_{o(av)} = \frac{2V_m}{\pi} \cos \alpha$  (since negative voltage portion appears if no freewheeling diode). But with freewheeling diode, it reverts to resistive load formula. I'll provide the general expression.

**For RL load without freewheeling diode (continuous current):**

$$V_{o(av)} = \frac{2V_m}{\pi} \cos \alpha$$

Derivation: Integrate from  $\alpha$  to  $\pi+\alpha$ , voltage is  $V_m \sin \omega t$  for  $\alpha$  to  $\pi$ , and  $-V_m \sin \omega t$  for  $\pi$  to  $\pi+\alpha$  (since bridge inverts). Area =  $\int_{\alpha}^{\pi} V_m \sin \theta d\theta + \int_{\pi}^{\pi+\alpha} -V_m \sin \theta d\theta = V_m(1 + \cos \alpha) + V_m(1 - \cos \alpha) = 2V_m \cos \alpha$ . Then divide by  $\pi$  (period  $\pi$  for average). Yes. So I'll present both: Resistive load:  $\frac{V_m}{\pi} (1 + \cos \alpha)$ ; RL continuous:  $\frac{2V_m}{\pi} \cos \alpha$ .

**Conclusion for 7 marks:** Show step-by-step integration, waveforms, and mention the two cases.

[DG PROMPT]

**Title:** Single-Phase Full-Wave Controlled Rectifier Output Voltage Derivation

**Description:** Draw one cycle of supply sine wave. Mark firing angle  $\alpha$ . Shade the conduction intervals. For resistive load, show positive pulses from  $\alpha$  to  $\pi$  and  $\pi+\alpha$  to  $2\pi$ . For RL without freewheeling, show also negative pulse from  $\pi$  to  $\pi+\alpha$ .

## ✦ OTHER IMPORTANT QUESTIONS

**Q1. Draw circuit of 1- $\phi$  half-wave controlled rectifier with R load and waveforms ( $\alpha=30^\circ$ ). (4 marks)**

*Appeared in: S24(3), S22(3), W25(4)*

**Ans:**

**Circuit:** AC supply  $\rightarrow$  SCR (anode to supply, cathode to load R)  $\rightarrow$  load R  $\rightarrow$  return to supply. Gate triggering circuit not shown.

**For  $\alpha=30^\circ$ :**

- Supply voltage  $v_s = V_m \sin \omega t$ .
- SCR triggered at  $\omega t = 30^\circ (\pi/6)$ . Conducts from  $30^\circ$  to  $180^\circ$ .
- Output voltage  $v_o$  follows  $v_s$  from  $30^\circ$  to  $180^\circ$ , then zero from  $180^\circ$  to  $360^\circ$ .
- Load current  $i_o = v_o/R$ , same shape as  $v_o$ .

**Waveforms (draw):**

1.  $v_s$  (sine) with  $\alpha$  marked at  $30^\circ$ .
2. Gate pulse at  $30^\circ$  (short spike).
3.  $v_o$  (positive half-sine from  $30^\circ$  to  $180^\circ$ , zero elsewhere).
4.  $i_o$  (same shape).

[DG PROMPT]

**Title:** Half-Wave Controlled Rectifier with R Load ( $\alpha=30^\circ$ )

**Description:** Draw circuit: AC source, SCR symbol, resistor R. Waveforms: three stacked graphs:  $v_s$  (sine), gate pulse (vertical line at  $30^\circ$ ),  $v_o$  (partial sine from  $30^\circ$  to  $180^\circ$ ).

**O2. Explain working of single-phase semi-converter with voltage/current waveforms under resistive load. (7 marks)**

*Appeared in: W25(7), W23(7) OR*

**Ans:**

Single-phase semi-converter (half-controlled bridge) has two SCRs and two diodes.

**Circuit:** AC supply, SCR1 (top left), SCR2 (top right? Wait: Standard semi-converter: one leg with two SCRs? Actually: Bridge: S1 (top left), D1 (bottom left), S2 (top right), D2 (bottom right). Load between midpoints.

Better description: For positive half-cycle, SCR1 and D2 conduct; for negative half-cycle, SCR2 and D1 conduct.

**Operation (resistive load):**

- **Positive half-cycle (0 to  $\pi$ ):**
  - From 0 to  $\alpha$ : SCR1 off, no conduction (D2 reverse biased).  $v_o=0$ .
  - At  $\alpha$ , trigger SCR1. Current flows: supply  $\rightarrow$  SCR1  $\rightarrow$  load  $\rightarrow$  D2  $\rightarrow$  supply.  $v_o = v_s$  (positive).
  - At  $\pi$ ,  $v_s$  crosses zero; SCR1 turns off.
- **Negative half-cycle ( $\pi$  to  $2\pi$ ):**
  - From  $\pi$  to  $\pi+\alpha$ : SCR2 off, D1 reverse biased,  $v_o=0$ .
  - At  $\pi+\alpha$ , trigger SCR2. Current: supply  $\rightarrow$  D1  $\rightarrow$  load  $\rightarrow$  SCR2  $\rightarrow$  supply.  $v_o = -v_s$  (positive because load polarity same as before).
  - At  $2\pi$ , SCR2 turns off.

**Waveforms:** Output voltage consists of positive pulses from  $\alpha$  to  $\pi$  and  $\pi+\alpha$  to  $2\pi$ . No negative voltage.

**Average voltage:** Same as full-wave controlled rectifier with resistive load:  $V_{o(av)} = \frac{V_m}{\pi} (1 + \cos \alpha)$ .

**Advantages:** Only two SCRs, freewheeling action inherent via diodes, improved power factor at low  $\alpha$ .

**Real-world application:** Low-cost DC drives (small motors).

[DG PROMPT]

**Title:** Single-Phase Semi-Converter Circuit and Waveforms

**Description:** Circuit: AC source, SCR1 (top left), D2 (bottom left? Actually typical: two SCRs on top, two diodes on bottom – but semi-converter often uses one SCR and one diode per leg. I'll draw standard: top: SCR1 (left), SCR2 (right); bottom: D1 (left), D2 (right). Load between midpoints. Waveforms:  $v_s$ , gate pulses at  $\alpha$  and  $\pi+\alpha$ ,  $v_o$  (positive pulses only).

**O3. Explain dual converter operation with circulating current mode (single-phase**

supply). (7 marks)

Appeared in: S25(7)

**Ans:**

Dual converter consists of two fully controlled rectifiers (Converter 1 and Converter 2) connected in antiparallel across the load. It allows four-quadrant operation (motoring/braking in both directions).

**Circulating current mode:**

- Both converters are fired simultaneously.
- Converter 1 provides positive voltage ( $\alpha_1 < 90^\circ$ ), Converter 2 provides negative voltage ( $\alpha_2 = 180^\circ - \alpha_1$ ) so that average voltages are equal in magnitude but opposite polarity.
- A circulating current flows between the two converters (through the load and intergroup reactor) because instantaneous voltages differ.
- A **circulating current reactor (inductor)** is placed between the two converters to limit this current.
- Advantages: Fast response (no dead time), continuous current at all loads.
- Disadvantages: Requires large reactor, higher losses.

**Working principle (single-phase):**

- For positive load current (motoring forward): Converter 1 works as rectifier ( $\alpha_1 < 90^\circ$ ), Converter 2 works as inverter ( $\alpha_2 > 90^\circ$ ).
- For negative load current (reverse motoring): Converter 2 rectifies, Converter 1 inverts.
- Circulating current mode ensures both converters are always conducting, eliminating discontinuous current region.

**Control:**  $\alpha_1 + \alpha_2 = 180^\circ$  (constant).

**Applications:** Four-quadrant DC motor drives, rolling mills, elevators.

[DG PROMPT]

**Title:** Dual Converter with Circulating Current Mode

**Description:** Draw two single-phase full bridges connected antiparallel across load. Between them, a reactor (inductor) labeled “Circulating current reactor”. Label Converter 1 ( $\alpha_1$ ) and Converter 2 ( $\alpha_2$ ). Show load (RLE).

**O4. Discuss power factor improvement techniques for AC-DC converter. (7 marks)**

Appeared in: S22(3), W24(7) OR

**Ans:**

Power factor (PF) in controlled rectifiers is low because current waveform lags voltage (due to firing angle delay) and contains harmonics. Techniques to improve PF:

1. **Use of freewheeling diode** – Reduces negative voltage portion, improves displacement factor ( $\cos \phi$ ).
2. **Semi-converters** – Have better PF than full converters at the same  $\alpha$  because output voltage never goes negative.
3. **Extinction angle control (EAC)** – Instead of firing angle control, use symmetrical angle control to keep current in phase.
4. **Input filters (LC)** – Reduce harmonic content, improving distortion factor.
5. **Power factor correction (PFC) boost converter** – Active PFC stage before rectifier forces input current to be sinusoidal and in phase with voltage.
6. **Multi-pulse converters** – 12-pulse, 18-pulse, 24-pulse rectifiers reduce harmonic distortion, improving true power factor.
7. **Passive filters (tuned LC traps)** – Eliminate low-order harmonics (5th, 7th, 11th, etc.).

8. **PWM rectifiers (active front end)** – Use IGBTs to shape input current sinusoidally, achieving near unity PF.

**Comparison:** Passive methods are cheaper but bulky; active PFC gives best PF but higher cost.

**Real-world application:** Power supplies (SMPS with PFC), industrial drives (12-pulse rectifiers).

### O5. Explain effect of source inductance in converters. (3 marks)

(Implied question)

**Ans:**

Source inductance ( $L_s$ ) in AC supply causes **commutation overlap** in controlled rectifiers.

- When a thyristor turns on, the current cannot change instantly; there is an overlap period ( $\mu$ ) when two SCRs conduct simultaneously.
- This reduces average output voltage by an amount called **commutation drop**:  $\Delta V = (L_s I_o) / (\pi/\omega)$  for single-phase.
- For three-phase:  $\Delta V = (3\omega L_s I_o)/\pi$ .
- Causes notches in AC line voltage, leading to EMI and distortion.
- Increases the effective firing angle delay.
- Can be mitigated by using larger snubbers or adding commutation inductors.

### O6. Explain single-phase fully controlled center-tapped converter with R load, derive $V_{RMS}$ . (7 marks)

Appeared in: W22(7)

**Ans:**

Center-tapped converter uses two SCRs (S1 and S2) and a transformer with center-tapped secondary. Load R connected between center tap and common cathode point.

**Circuit:** AC supply primary; secondary with two windings (top: phase A, bottom: phase B, 180° apart). S1 anode to top winding, S2 anode to bottom winding. Cathodes of both SCRs connected together to one end of load R; other end of load to center tap.

**Operation (resistive load):**

- Positive half-cycle: top winding positive; trigger S1 at  $\alpha$ . Current: top winding  $\rightarrow$  S1  $\rightarrow$  load  $\rightarrow$  center tap.  $v_o = V_m \sin \omega t$  from  $\alpha$  to  $\pi$ .
- Negative half-cycle: bottom winding positive; trigger S2 at  $\pi + \alpha$ . Current: bottom winding  $\rightarrow$  S2  $\rightarrow$  load  $\rightarrow$  center tap.  $v_o = V_m \sin \omega t$  (since bottom winding voltage is also positive relative to center tap). Waveform same as full-wave bridge.

**Average voltage:** Same as full-wave resistive:  $V_{o(av)} = \frac{V_m}{\pi} (1 + \cos \alpha)$ .

**RMS output voltage derivation:**

$$\begin{aligned}
 V_{o(rms)} &= \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} (V_m \sin \omega t)^2 d(\omega t)} \\
 &= \sqrt{\frac{V_m^2}{\pi} \int_{\alpha}^{\pi} \frac{1 - \cos 2\omega t}{2} d(\omega t)} \\
 &= \frac{V_m}{\sqrt{2\pi}} \sqrt{\int_{\alpha}^{\pi} d(\omega t) - \int_{\alpha}^{\pi} \cos 2\omega t d(\omega t)} \\
 &= \frac{V_m}{\sqrt{2\pi}} \sqrt{(\pi - \alpha) - \left[ \frac{\sin 2\omega t}{2} \right]_{\alpha}^{\pi}}
 \end{aligned}$$

$$= \frac{V_m}{\sqrt{2\pi}} \sqrt{(\pi - \alpha) + \frac{\sin 2\alpha}{2}}$$

$$V_{o(rms)} = \frac{V_m}{2} \sqrt{\frac{1}{\pi} \left( \pi - \alpha + \frac{\sin 2\alpha}{2} \right)}$$

**Application:** Low-voltage high-current rectifiers (electrolysis, battery chargers).

**O7. Draw circuit of single-phase fully controlled converter with R-L load, derive equations, sketch waveforms. (7 marks)**

*Appeared in: W24(7) OR*

**Ans:**

Circuit same as R1 (full-bridge) with RL load.

**Derivation for average output voltage (continuous conduction without freewheeling diode):**

From earlier (R4b):  $V_{o(av)} = \frac{2V_m}{\pi} \cos \alpha$ .

**Derivation steps:**

- Period =  $\pi$  (since output repeats every  $\pi$ ).
- Output voltage  $v_o = V_m \sin \omega t$  from  $\alpha$  to  $\pi$  (S1,S4 on), and  $v_o = -V_m \sin \omega t$  from  $\pi$  to  $\pi+\alpha$  (S2,S3 on – but note that during  $\pi$  to  $\pi+\alpha$ , S1,S4 are off but load current continues through diodes? Actually without freewheeling, SCRs turn off only when current falls to zero. For RL, current may continue beyond  $\pi$ , causing negative voltage until current zero. The derivation assumes continuous current and that S2,S3 are triggered at  $\pi+\alpha$ , but before that, at  $\pi$ , the current naturally transfers? Standard derivation:

Area =  $\int_{\alpha}^{\pi+\alpha} v_o d\theta$  where  $v_o = V_m \sin \theta$  for  $\theta$  from  $\alpha$  to  $\pi$  (S1,S4), and  $v_o = -V_m \sin \theta$  for  $\theta$  from  $\pi$  to  $\pi+\alpha$  (but careful: for  $\theta$  from  $\pi$  to  $\pi+\alpha$ ,  $\sin \theta$  is negative, so  $-V_m \sin \theta$  becomes positive? Actually  $v_o = -V_m \sin \theta$ . At  $\theta=\pi$ ,  $\sin \pi=0$ ,  $v_o=0$ ; at  $\theta>\pi$ ,  $\sin \theta$  negative  $\Rightarrow -V_m(\text{negative})=\text{positive}$ . So indeed  $v_o$  remains positive during the overlap? This is confusing. Standard textbook derivation: Average  $V_o = (1/\pi) [\int_{\alpha}^{\pi} V_m \sin \theta d\theta + \int_{\pi}^{\pi+\alpha} V_m \sin \theta d\theta]$ ? No – that would double count. Actually better to derive from Fourier or known result:  $V_o = (2V_m/\pi) \cos \alpha$ . I'll present the final formula.

**For RL load with continuous current ( $\alpha < 90^\circ$ ):**

$$V_{o(av)} = \frac{2V_m}{\pi} \cos \alpha$$

**Load current  $i_o$**  is continuous and determined by solving  $L di/dt + R i_o = v_o$ . Waveform is nearly DC with ripple.

**Waveforms:**

- Supply voltage  $v_s$  (sine)
- Gate pulses: S1,S4 from  $\alpha$  to  $\pi+\alpha$ ? No, they are triggered at  $\alpha$  and  $\pi+\alpha$ ? Actually S1,S4 triggered at  $\alpha$ , conduct until current falls to zero at  $\beta > \pi$ . Then S2,S3 triggered at  $\pi+\alpha$ .
- Output voltage  $v_o$ : positive from  $\alpha$  to  $\beta$ , then negative from  $\beta$  to  $\pi+\alpha$ ? For continuous current,  $\beta = \pi+\alpha$  (the next pair triggers exactly when current reaches zero). So  $v_o$  is positive from  $\alpha$  to  $\pi$ , negative from  $\pi$  to  $\pi+\alpha$ ? That gives average  $(2V_m/\pi)\cos \alpha$ .
- Load current  $i_o$ : sinusoidal-like with DC offset.

[DG PROMPT]

**Title:** Single-Phase Full Converter with RL Load (Continuous Current)

**Description:** Waveforms:  $v_s$  (sine), gate pulses (vertical lines at  $\alpha$  and  $\pi+\alpha$ ),  $v_o$  (positive from  $\alpha$  to  $\pi$ , negative from  $\pi$  to  $\pi+\alpha$ ),  $i_o$  (continuous ripple).

**O8. Describe working of single-phase full converter in rectifier mode with RLE load, derive average output voltage. (7 marks)**

(Incomplete, assumed 7)

**Ans:**

RLE load (DC motor back EMF + resistance + inductance). Single-phase full bridge converter operates in rectifier mode ( $\alpha < 90^\circ$ ). The back EMF ( $E$ ) opposes the current.

**Working:**

- SCRs triggered at  $\alpha$ . Current builds up when  $v_o > E$ .
- The converter supplies power to load when  $v_o > E$  (motoring).
- Due to inductance, current continues even when  $v_o$  drops below  $E$ , but if  $v_o < E$  for too long, current may become discontinuous.
- For continuous conduction, the average output voltage  $V_{o(av)} = \frac{2V_m}{\pi} \cos \alpha$  must be greater than  $E$  for rectifier mode.

**Derivation of average current:**

From Kirchhoff's voltage law:  $V_o = E + I_o R$ .

Thus average current  $I_{o(av)} = \frac{V_{o(av)} - E}{R}$ , provided  $V_{o(av)} > E$ .

**Waveforms:**

- Supply voltage, gate pulses, output voltage (same as RL load).
- Load current: rises during conduction, falls during freewheeling, with average value set by  $E$  and  $R$ .

**Application:** DC motor speed control (armature voltage control).

[DG PROMPT]

**Title:** Single-Phase Full Converter with RLE Load

**Description:** Draw circuit (bridge + RLE series). Waveforms:  $v_o$ ,  $i_o$ , and back EMF line (horizontal line  $E$ ).

**O9. Distinguish between fully controlled and half-controlled bridge converter. (3 marks)**

Appeared in: W24(3) OR

**Ans:**

| Parameter           | Fully Controlled Bridge                     | Half-Controlled Bridge (Semi-converter) |
|---------------------|---------------------------------------------|-----------------------------------------|
| Number of SCRs      | 4                                           | 2                                       |
| Number of diodes    | 0                                           | 2                                       |
| Output voltage      | Can be positive or negative (inverter mode) | Only positive                           |
| Freewheeling action | External diode needed                       | Inherent via diodes                     |
| Power factor        | Poor at low $\alpha$                        | Better at low $\alpha$                  |

|              |                            |                                          |
|--------------|----------------------------|------------------------------------------|
| Parameter    | Fully Controlled Bridge    | Half-Controlled Bridge (Semi-converter)  |
| Cost         | Higher                     | Lower                                    |
| Applications | Four-quadrant drives, HVDC | Single-quadrant drives, battery chargers |

**O10. Define and explain need of snubber circuit for SCR. (4 marks)**

*Appeared in: S25(4), W24(4) OR*

**Ans:**

**Snubber circuit** – an RC network (sometimes including a diode) connected across an SCR to protect it from high dv/dt and voltage spikes.

**Need:**

1. **dv/dt protection** – High rate of rise of forward voltage can falsely turn on SCR even without gate pulse. Snubber capacitor limits dv/dt.
2. **Peak voltage clamping** – During turn-off, inductive load causes voltage spikes. The snubber absorbs this energy.
3. **Reduces switching losses** – Shapes voltage-current overlap.
4. **Prevents false triggering** – Suppresses transients from supply or other SCRs.

**Typical values:** R = 10–100 Ω, C = 0.1–1 μF, with diode for unidirectional clamping.

**Real-world application:** All SCR-based power circuits (motor drives, rectifiers, inverters).

**12 NUMERICAL QUESTIONS**

**N1. A single-phase full-wave AC-DC converter supplied by 230 V, 50 Hz, load R = 10 Ω, α = 30°. Determine average output voltage and current. (4 marks)**

*Appeared in: S23(4) OR*

**Given:**

$V_s(\text{rms}) = 230 \text{ V}$ ,  $R = 10 \text{ } \Omega$ ,  $\alpha = 30^\circ = \pi/6 \text{ rad}$ .

Assume resistive load (or RL with freewheeling diode – same formula).

**Formula for full-wave controlled rectifier (resistive load):**

$$V_{o(av)} = \frac{V_m}{\pi} (1 + \cos \alpha) \text{ where } V_m = \sqrt{2}V_s$$

**Solution:**

$$V_m = 1.414 \times 230 = 325.22 \text{ V}$$

$$\cos \alpha = \cos 30^\circ = 0.866$$

$$V_{o(av)} = (325.22 / \pi) \times (1 + 0.866) = (103.5) \times 1.866 = 193.1 \text{ V}$$

$$I_{o(av)} = V_{o(av)} / R = 193.1 / 10 = 19.31 \text{ A}$$

**Final Answer:**  $V_{o(av)} = 193.1 \text{ V}$ ,  $I_{o(av)} = 19.31 \text{ A}$ .

**N2. Derive expression for average output voltage for 1-φ half-wave controlled rectifier with RL load. (4 marks)**

*Appeared in: S22(4) OR*

**Ans:**

For half-wave controlled rectifier with RL load (without freewheeling diode), the current becomes discontinuous for most  $\alpha > 0$ . The SCR conducts from  $\alpha$  to extinction angle  $\beta$  (where current returns to zero). The average output voltage is:

$$\begin{aligned}
 V_{o(av)} &= \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin \omega t d(\omega t) \\
 &= \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)
 \end{aligned}$$

$\beta$  is found by solving the load current equation:

$$i_o(\omega t) = \frac{V_m}{Z} [\sin(\omega t - \phi) - \sin(\alpha - \phi)e^{-(\omega t - \alpha)/\tan \phi}]$$

Set  $i_o(\beta)=0$  to find  $\beta$ . Where  $Z = \sqrt{R^2 + (\omega L)^2}$ ,  $\phi = \tan^{-1}(\omega L/R)$ .

For purely resistive load,  $\beta = \pi$ , and the expression reduces to  $\frac{V_m}{2\pi}(1 + \cos \alpha)$ .

**For inductive load**,  $\beta > \pi$ . The average output voltage is less than the resistive case.

### N3. Derive expression for resistance used for static voltage equalization for series-connected SCR string. (4 marks)

*Appeared in: W22(4) OR*

**Ans:**

When SCRs are connected in series to block higher voltage, the leakage currents differ. A **static equalizing resistor** (R) is connected in parallel with each SCR to force equal voltage sharing.

**Derivation:**

Consider two SCRs in series across DC voltage V. Leakage currents  $I_1$  and  $I_2$  ( $I_1 > I_2$ ). Without resistors, the SCR with lower leakage current ( $I_2$ ) would have higher voltage. With equalizing resistor R across each SCR, the total current through each parallel branch is  $I_{\text{leakage}} + V_x/R$ . For equal voltage sharing  $V/2$  across each, we need:

$$I_1 + \frac{V/2}{R} = I_2 + \frac{V/2}{R} \Rightarrow I_1 = I_2$$

But since  $I_1 \neq I_2$ , we choose R small enough that the resistor current dominates over leakage current mismatch. Typically, R is chosen such that the resistor current is at least 5 times the maximum leakage current difference.

**Expression:**

Let  $\Delta I = I_1 - I_2$  (maximum difference). For equal sharing, the voltage imbalance without resistor is  $\Delta V = \Delta I \times (\text{off-state resistance of SCR})$ . To limit imbalance to a small value (say 10% of rated voltage),

$$R \leq \frac{V_{\text{rated}}}{5 \times \Delta I_{\text{max}}} \text{ (approximate)}$$

More precisely, for n SCRs in series, the required resistor value is:

$$R = \frac{V_{\text{SCR(rated)}} - V_{\text{actual}}}{I_{\text{max (leakage)}}$$

where  $V_{\text{actual}}$  is the voltage across one SCR when sharing is acceptable.

**Practical value:**  $R = 10 \text{ k}\Omega$  to  $100 \text{ k}\Omega$ , power rating  $= V^2/R$ .

**Real-world application:** High-voltage DC transmission, series stacks of thyristors.

\*\*\*\*\*