

GUJARAT TECHNOLOGICAL UNIVERSITY

BE-4 SEMESTER – OLD PAPER – S22 TO W25 – QUESTION BANK ANSWER

Subject Name & Code:

POWER ELECTRONICS (3140915)

(Disclaimer: The purpose of these AI-generated responses is just education and reference. Utilise them to grasp topics and structure, but always rewrite in your own words and double-check)

UNIT 5: AC VOLTAGE CONTROLLERS

REPEATED QUESTIONS

R1. Explain single-phase full-wave AC voltage controller with circuit and waveforms. Also give advantages, disadvantages, applications. (4 marks)

Appeared in: S25(3) OR, S23(3), W23(4) OR → Highest: 4

Ans:

A single-phase full-wave AC voltage controller uses two antiparallel SCRs (or a single TRIAC) to control the RMS voltage applied to an AC load by varying the firing angle α .

Circuit diagram:

AC supply ($V_s = V_m \sin \omega t$) → two SCRs (S1 and S2) connected in antiparallel → load R (or RL). Alternatively, a TRIAC can be used.

Operation (resistive load):

- **Positive half-cycle (0 to π):** S1 is forward biased. Trigger S1 at α . Conducts from α to π . Output voltage follows supply from α to π .
- **Negative half-cycle (π to 2π):** S2 is forward biased. Trigger S2 at $\pi + \alpha$. Conducts from $\pi + \alpha$ to 2π . Output voltage follows negative supply (positive half-sine shape).
- **Output voltage waveform:** Symmetrical chopped sine wave; RMS voltage decreases as α increases.

Waveforms:

- Supply voltage (sine)
- Gate pulses at α and $\pi + \alpha$
- Output voltage: zero from 0 to α , then sine from α to π , zero from π to $\pi + \alpha$, then sine from $\pi + \alpha$ to 2π .

RMS output voltage (resistive load):

$$V_{o(rms)} = V_s \sqrt{\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right)}$$

Advantages:

- Simple, low cost
- High efficiency (low losses)
- Continuous voltage control
- No harmonics below supply frequency

Disadvantages:

- Output waveform contains harmonics
- Poor power factor at low α
- EMI generation

Applications:

- Light dimmers
- Fan speed regulators
- Industrial heating control
- Soft starters for induction motors

[DG PROMPT]

Title: Single-Phase Full-Wave AC Voltage Controller**Description:**

- **Circuit:** Draw AC source (sine symbol) in series with two SCRs in antiparallel (S1 anode to line, cathode to load; S2 anode to load, cathode to line). Load resistor R in series. Alternatively show TRIAC.
- **Waveforms** (three stacked): v_s (sine), gate pulses (spikes at α and $\pi+\alpha$), v_o (zero, then sine segment, zero, then sine segment).

R2. Explain three-phase AC voltage controller with star-connected R load, waveforms for $\alpha = 60^\circ$. (7 marks)*Appeared in: S24(7) OR, S22(7) OR, W24(7), W23(7) OR***Ans:**

A three-phase AC voltage controller controls voltage to a three-phase load using six SCRs (two per phase) in antiparallel or three TRIACs. For star-connected resistive load, the firing angle α controls the RMS line/phase voltage.

Circuit:

Three-phase supply (R, Y, B) – each phase connected to a pair of antiparallel SCRs (e.g., phase R: SCR1 and SCR4). Load is star-connected resistive.

Operation for $\alpha = 60^\circ$ (resistive load):

- For $\alpha = 0^\circ$, output is full sine wave.
- At $\alpha = 60^\circ$, each SCR is triggered 60° after its natural turn-on point (voltage zero crossing).
- The output phase voltage waveform consists of segments of the input sine wave. For star load, the line voltage is controlled indirectly.

Waveforms (for one phase, say phase R to neutral):

- Input phase voltage v_{RN} (sine).
- Gate pulses for SCR1 (positive half) at $\omega t = 60^\circ, 180^\circ$, etc.
- Output phase voltage $v_{RN(out)}$: from 60° to 180° (input sine), then zero? Actually for $\alpha > 60^\circ$, the conduction may be discontinuous. For $\alpha = 60^\circ$, the output is still continuous? Need clarity.

Standard three-phase controller waveforms:

- For $\alpha < 60^\circ$, continuous conduction.
- For $\alpha = 60^\circ$, the output voltage just becomes discontinuous at the zero crossings.
- Each SCR conducts for $120^\circ - \alpha$? Actually typical: For star load with neutral, each SCR conducts from α to 180° (positive half) and next SCR from $180^\circ + \alpha$ to 360° .
- At $\alpha = 60^\circ$, the output phase voltage has a flat top? Better to describe: The RMS output voltage is given by:

$$\text{For } \alpha \leq 60^\circ: V_{o(ph)} = V_{ph} \sqrt{\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right)} \quad (\text{same as single-phase}).$$

For $\alpha > 60^\circ$, more complex.

Waveform sketch for $\alpha = 60^\circ$:

- Phase voltage waveform: positive half from 60° to 180° is a sine segment starting at $\sin 60^\circ = 0.866$, rising to 1 at 90° , then falling to 0 at 180° . Then zero from 180° to 240° ? Actually next SCR triggers at $180^\circ + 60^\circ = 240^\circ$ for negative half? Wait, careful:

For three-phase, the neutral point provides return path. But typical three-phase three-wire controller (no neutral) has different waveforms. The question likely expects **three-phase three-wire** star load. In that case, at $\alpha=60^\circ$, the line-to-line voltage is chopped.

Simplified explanation for GTU:

- Draw three-phase input phase voltages (120° apart).
- For $\alpha=60^\circ$, mark triggering points.
- Output phase voltage consists of segments from two different phases.
- Waveforms have six pulses per cycle.

Applications:

- Three-phase induction motor soft starters
- Large industrial heating
- Uninterruptible power supplies (AC line conditioning)

[DG PROMPT]

Title: Three-Phase AC Voltage Controller (Star Load, $\alpha=60^\circ$)

Description: Draw three sinusoidal phase voltages (R,Y,B) 120° apart. Below, draw output phase voltage for phase R: It follows input from 60° to 180° , then from 180° to 300° ?

Actually need to show correct segments. For three-wire system, the voltage across one phase load is not simply input phase voltage; it's the difference between two line voltages. I'll give a simplified diagram: Show six SCRs connected to three-phase supply and star load. Below, show gate pulses for SCR1 (phase R positive) at 60° , 180° , etc. Show output voltage waveform with notches.

R3. List industrial applications of AC voltage controllers, merits/demerits. (3 marks)

Appeared in: S24(3), S23(3), W25(3) OR, W24(3) OR, W22(3)

Ans:

Industrial applications:

1. **Lighting control** – incandescent and LED dimming
2. **Fan speed regulators** – ceiling fans, exhaust fans
3. **Induction motor soft starters** – reduces inrush current
4. **Industrial heating** – furnaces, ovens, heat sealers
5. **Pump and compressor speed control** (low-cost)
6. **Welding control** – AC resistance welding
7. **Voltage stabilizers / regulators**

Merits (Advantages):

- High efficiency (no series pass element)
- Continuous voltage variation
- Simple and rugged
- Low maintenance

Demerits (Disadvantages):

- Output waveform contains harmonics
- Low power factor at high firing angles
- EMI/RFI generation
- Not suitable for highly inductive loads without special design

R4. Distinguish between on-off control and phase angle control. (4 marks)

Appeared in: S24(4) OR, W25(3), W24(4), W22(4)

Ans:

Parameter	On-Off Control (Integral Cycle Control)	Phase Angle Control
-----------	---	---------------------

Parameter	On-Off Control (Integral Cycle Control)	Phase Angle Control
Principle	Switches ON for integer number of full cycles, OFF for next cycles	Fires SCR at a specific angle (α) within each half-cycle
Output waveform	Complete sine waves (whole cycles)	Chopped sine wave within each half-cycle
Harmonics	Subharmonics (low frequency)	High-frequency harmonics (near supply multiples)
Power factor	Good (near unity when ON)	Poor at large α
Flicker	Present if cycle period is long	No flicker
Control resolution	Coarse (step of one cycle)	Fine (continuous)
Applications	Heating (thermal inertia), ovens	Lighting, fan speed, motor soft starters

✦ OTHER IMPORTANT QUESTIONS

Q1. Explain integral cycle control of AC voltage controllers with equations and waveforms. (7 marks)

Appeared in: S25(7) OR

Ans:

Integral cycle control (also called burst firing or on-off control) switches the AC load on for an integer number of full cycles (N) and off for M cycles, repeating. The output voltage is a burst of undistorted sine waves.

Working principle:

- A zero-crossing detector triggers the SCRs at the start of a voltage zero crossing.
- For a period of (N+M) cycles, the load is ON for N cycles and OFF for M cycles.
- Average power is proportional to $N/(N+M)$.

Equations:

Let total cycles per control period = $N + M = T_c$.

Duty cycle = $N / (N+M)$.

RMS output voltage $V_{o(rms)} = V_s \sqrt{\frac{N}{N+M}}$, where V_s is supply RMS voltage.

Average power $P_o = \frac{N}{N+M} \times \frac{V_s^2}{R}$.

Waveforms:

- Supply voltage (continuous sine wave).
- Gate pulses: only present at the start of each ON cycle (zero crossing).
- Output voltage: N full sine waves, then M cycles of zero, repeat.

Advantages:

- No harmonics below supply frequency (except subharmonics at $1/(N+M) \times$ supply frequency)
- Good power factor

- No EMI from chopping within cycle

Disadvantages:

- Flicker at low duty cycles (long off periods)
- Slow response (not suitable for fast regulation)

Applications: Electric ovens, water heaters, industrial heating (high thermal inertia).

[DG PROMPT]

Title: Integral Cycle Control Waveforms

Description: Draw supply voltage (continuous sine wave). Below, draw output voltage: first N cycles identical to supply, then M cycles of zero voltage. Label N and M.

O2. Describe application of TRIAC as single-phase fan regulator with circuit and waveform. (4 marks)

Appeared in: S23(4), W23(4) OR

Ans:

A TRIAC is used as a fan speed regulator (ceiling fan or exhaust fan) by phase angle control. The circuit is called a **fan dimmer** or **AC regulator**.

Circuit description:

- AC supply (230V, 50Hz) → TRIAC (main terminal MT1 to load, MT2 to supply) → fan (inductive load).
- A DIAC (or small trigger circuit) connected between gate and MT1 via a variable resistor R (potentiometer) and capacitor C (RC phase shift network).
- Optional: Snubber circuit (RC) across TRIAC for inductive load protection.

Operation:

- At the start of each half-cycle, TRIAC is off. Capacitor C charges through R and the load.
- When capacitor voltage reaches DIAC breakdown voltage (~30V), DIAC conducts, triggering TRIAC.
- By varying R, the charging time constant changes, varying the firing angle α .
- Larger α reduces RMS voltage to fan, reducing speed.

Waveform:

Output voltage across fan is chopped sine wave (same as single-phase controller). For fan (inductive load), current lags, but TRIAC commutates at natural current zero.

Advantages:

- Low cost, compact
- Smooth speed variation
- High efficiency

Precautions:

- Use snubber to avoid false triggering.
- Not suitable for very low speeds (torque pulsation).

Real-world application: Ceiling fan regulators, exhaust fan controllers.

[DG PROMPT]

Title: TRIAC Based Fan Speed Regulator

Description: Circuit: AC source in series with fan (inductive load) and TRIAC (MT2 to supply, MT1 to fan). Gate connected to DIAC, and DIAC to junction of variable resistor R and capacitor C (other ends to MT1). Waveform: output voltage chopped sine wave with variable α .

O3. Draw only possible configurations of single-phase voltage controller. (3 marks)

Appeared in: W23(3) OR

Ans:

Single-phase AC voltage controller configurations:

1. **Single-switch (half-wave) controller** – One SCR in series with load, with a freewheeling diode? Not common.
2. **Two SCRs in antiparallel** – Most common full-wave controller.
3. **One TRIAC** – Equivalent to antiparallel SCRs.
4. **Four SCRs in bridge configuration** – For bidirectional control with separate paths (rare).

Drawings (text description):

- **Configuration A (Antiparallel SCRs):** Supply line $\rightarrow$ load $\rightarrow$ junction of two SCRs; one SCR cathode to load, anode to supply; other SCR cathode to supply, anode to load.
- **Configuration B (TRIAC):** Supply $\rightarrow$ TRIAC (MT2 $\rightarrow$ supply, MT1 $\rightarrow$ load) $\rightarrow$ load.
- **Configuration C (Bridge with four SCRs):** Not typical for AC controller.

The most common for GTU exams: **two SCRs in antiparallel**.

[DG PROMPT]

Title: Single-Phase AC Voltage Controller Configurations

Description: Draw two circuits side by side.

Left: Two SCRs (S1 and S2) in antiparallel with load. Right: One TRIAC symbol with load.

O4. Derive RMS output voltage equation for single-phase full-wave AC voltage controller with R load. (3 marks)

Appeared in: W22(3)

Ans:

Supply voltage $v_s = V_m \sin \omega t$. Firing angle α . Output voltage $v_o = 0$ for $0 < \omega t < \alpha$, then $V_m \sin \omega t$ for $\alpha < \omega t < \pi$, then 0 for $\pi < \omega t < \pi + \alpha$, then $V_m \sin \omega t$ for $\pi + \alpha < \omega t < 2\pi$.

RMS value definition:

$$V_{o(rms)} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_o^2 d(\omega t)}$$

Due to symmetry:

$$\begin{aligned} V_{o(rms)} &= \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} (V_m \sin \omega t)^2 d(\omega t)} \\ &= \sqrt{\frac{V_m^2}{\pi} \int_{\alpha}^{\pi} \frac{1 - \cos 2\omega t}{2} d(\omega t)} \\ &= \frac{V_m}{\sqrt{2\pi}} \sqrt{\int_{\alpha}^{\pi} d(\omega t) - \int_{\alpha}^{\pi} \cos 2\omega t d(\omega t)} \\ &= \frac{V_m}{\sqrt{2\pi}} \sqrt{(\pi - \alpha) - \left[\frac{\sin 2\omega t}{2} \right]_{\alpha}^{\pi}} \\ &= \frac{V_m}{\sqrt{2\pi}} \sqrt{\left(\pi - \alpha \right) - \frac{1}{2} (\sin 2\pi - \sin 2\alpha)} \\ &= \frac{V_m}{\sqrt{2\pi}} \sqrt{\left(\pi - \alpha \right) + \frac{\sin 2\alpha}{2}} \end{aligned}$$

Since $V_m = \sqrt{2} V_s$ (V_s is RMS supply):

$$V_{o(rms)} = V_s \sqrt{\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right)}$$

Final equation:

$$V_{o(rms)} = V_s \sqrt{\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right)}$$

O5. Derive AC voltage controller average output voltage equation. (3 marks)

Appeared in: W24(3) OR

Ans:

For AC voltage controllers, the **average output voltage** (DC component) is zero because the waveform is symmetrical about zero for pure resistive load. However, if the question refers to **average of absolute value** or **average for half-wave rectifier type**, clarify.

For a full-wave AC controller, the average (mean) over a full cycle is zero. For a **half-wave** controller, average output voltage:

$$V_{o(av)} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t) = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

But for full-wave, the average is zero.

GTU often asks: "Derive average output voltage for single-phase AC voltage controller" – they likely mean half-wave type or they want the RMS formula? Since O4 already gave RMS, this may be a duplicate. I'll provide the half-wave average formula as answer.

$$V_{o(av)} = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

O6. Derive output voltage equation of single-phase AC voltage controller. (4 marks)

Appeared in: W22(4)

Ans:

This is the same as RMS derivation in O4. I'll present the complete derivation with final RMS expression and also mention that the average is zero.

Output voltage equation (RMS):

$$V_{o(rms)} = V_s \sqrt{\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right)}$$

Output voltage equation (instantaneous):

For resistive load,

$$v_o(\omega t) = \begin{cases} 0, & 0 < \omega t < \alpha \\ V_m \sin \omega t, & \alpha < \omega t < \pi \\ 0, & \pi < \omega t < \pi + \alpha \\ V_m \sin \omega t, & \pi + \alpha < \omega t < 2\pi \end{cases}$$

This is the output voltage equation.

O7. Explain working of single-phase full-wave bidirectional controller, derive RMS output voltage for 230V input, $\alpha = 45^\circ$. (7 marks)

Appeared in: S22(7) OR

Ans:

A single-phase full-wave bidirectional AC voltage controller (same as R1) uses two SCRs in antiparallel or a TRIAC to control both half-cycles symmetrically. It is called "bidirectional" because current can flow in both directions.

Working: Already explained in R1.

Given: V_s (RMS) = 230 V, $\alpha = 45^\circ = \pi/4$ rad. Load is resistive (assumed).

Formula for RMS output voltage (resistive load):

$$V_{o(rms)} = V_s \sqrt{\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right)}$$

Step-by-step calculation:

1. $\alpha = 45^\circ = \pi/4 = 0.7854$ rad
2. $\pi - \alpha = 3.1416 - 0.7854 = 2.3562$ rad
3. $2\alpha = 90^\circ = \pi/2 = 1.5708$ rad
4. $\sin(2\alpha) = \sin 90^\circ = 1$
5. $\sin(2\alpha)/2 = 0.5$
6. $(\pi - \alpha) + \sin(2\alpha)/2 = 2.3562 + 0.5 = 2.8562$
7. Divide by π : $2.8562 / 3.1416 = 0.9091$
8. Square root: $\sqrt{0.9091} = 0.9535$
9. Multiply by V_s : $230 \times 0.9535 = \mathbf{219.3 \text{ V}}$

Final answer: RMS output voltage = **219.3 V** (approximately).

For inductive load: The formula changes because current may be continuous; but with $\alpha=45^\circ$, typically still discontinuous unless L is large. The question assumes resistive load unless specified.

Waveforms: Same as R1.
