

GUJARAT TECHNOLOGICAL UNIVERSITY

BE-4 SEMESTER – OLD PAPER – S22 TO W25 – QUESTION BANK ANSWER

Subject Name & Code:

ANALOG CIRCUIT DESIGN (3141002)

(Disclaimer: The purpose of these AI-generated responses is just education and reference. Utilise them to grasp topics and structure, but always rewrite in your own words and double-check)

Unit 5: Timer IC 555 and Phase-Locked Loop (PLL)

Q.1 – Explain the block diagram and working of IC 555 timer.

(7 marks)

Ans:

Block diagram of IC 555 timer:

The 555 timer IC consists of the following functional blocks:

- **Voltage divider:** Three equal resistors ($5k\Omega$ each) connected between V_{CC} and ground, producing reference voltages $\frac{2}{3}V_{CC}$ and $\frac{1}{3}V_{CC}$.
- **Two comparators:**
 - **Comparator 1 (Threshold comparator):** Compares threshold voltage (pin 6) with $\frac{2}{3}V_{CC}$.
 - **Comparator 2 (Trigger comparator):** Compares trigger voltage (pin 2) with $\frac{1}{3}V_{CC}$.
- **SR flip-flop:** Set and reset by comparator outputs.
- **Discharge transistor (NPN):** Controlled by flip-flop output (Q_{bar}). When ON, it discharges external capacitor.
- **Output buffer (inverter):** Provides output current drive.

Pin diagram (8-pin DIP):

1 – GND, 2 – Trigger, 3 – Output, 4 – Reset, 5 – Control Voltage, 6 – Threshold, 7 – Discharge, 8 – V_{CC} .

Diagram prompt:

[DG PROMPT]

Title: Internal block diagram of IC 555 timer

Description: Draw three equal resistors ($5k$ each) in series from V_{CC} (pin 8) to ground (pin 1).

Tap the node between first and second resistor as $\frac{2}{3}V_{CC}$ to non-inverting input of Comparator

1. Tap between second and third as $\frac{1}{3}V_{CC}$ to inverting input of Comparator 2. Comparator 1:

inverting input connected to Threshold pin (pin 6). Comparator 2: non-inverting input connected to Trigger pin (pin 2). Outputs of comparators go to SR flip-flop: Comparator 1 output to Reset, Comparator 2 output to Set. Flip-flop output (Q) goes to output buffer (inverter) to pin 3. Flip-flop complementary output (Q_{bar}) drives base of discharge transistor (NPN) whose collector is pin 7 (Discharge) and emitter to ground. Reset pin (pin 4) connected to flip-flop reset (active low). Control Voltage pin (pin 5) connected to the $\frac{2}{3}V_{CC}$ node (via a voltage follower internally). Label all pins.

Working principle:

1. **Voltage divider** provides fixed reference voltages of $\frac{1}{3}V_{CC}$ and $\frac{2}{3}V_{CC}$ regardless of V_{CC} (within limits).
2. **Trigger comparator (Comp 2):** When trigger voltage (pin 2) falls below $\frac{1}{3}V_{CC}$, Comp 2 output goes high \rightarrow sets the SR flip-flop \rightarrow output (pin 3) goes high, and discharge transistor turns OFF.
3. **Threshold comparator (Comp 1):** When threshold voltage (pin 6) rises above $\frac{2}{3}V_{CC}$, Comp 1 output goes high \rightarrow resets SR flip-flop \rightarrow output goes low, and discharge transistor turns ON (pin 7 connected to ground).
4. **Reset pin (pin 4):** When pulled low (0V), it forces flip-flop reset \rightarrow output low, transistor ON.
5. **Control voltage pin (pin 5):** Allows external adjustment of the $\frac{2}{3}V_{CC}$ reference (modulates timing).

Operating modes:

- **Astable mode:** Free-running oscillator (no stable state).
- **Monostable mode:** One-shot pulse generator.
- **Bistable mode (Schmitt trigger):** Two stable states.

Real-world application: 555 timers are used in pulse generation, time delay, LED flashers, tone generators, PWM controllers, and missing pulse detectors.

Q.2 – Explain monostable multivibrator using IC 555.

(7 marks)

Ans:

Definition: A monostable multivibrator (one-shot) produces a single output pulse of fixed duration when triggered. It has one stable state (output LOW) and one quasi-stable state (output HIGH).

Circuit connections (555 in monostable mode):

- Connect V_{CC} to pin 8, GND to pin 1.
- Reset pin (4) tied to V_{CC} (disable reset).
- Control voltage pin (5) grounded via $0.01\mu\text{F}$ capacitor (noise bypass).
- External resistor R from V_{CC} to pin 7 (Discharge).
- External capacitor C from pin 6 (Threshold) to ground.
- Pin 6 and pin 7 connected together (short).
- Trigger input applied to pin 2.
- Output taken from pin 3.

Diagram prompt:

[DG PROMPT]

Title: 555 timer monostable multivibrator circuit

Description: Draw IC 555 with pin numbers. Connect pin 8 to Vcc, pin 1 to ground. Connect pin 4 to Vcc. Connect pin 5 to ground via $0.01\mu\text{F}$ capacitor. Connect resistor R from Vcc to pin 7. Connect capacitor C from pin 6 to ground, and also connect pin 7 to pin 6 (short).

Trigger input (active low pulse) to pin 2. Output at pin 3. Show waveform: trigger pulse (negative spike), output pulse width $T = 1.1 RC$, capacitor voltage charging exponential from 0 to $\frac{2}{3}V_{CC}$.

Working principle (step-by-step):

1. **Stable state (output LOW):** Initially, trigger pin 2 is HIGH (above $\frac{1}{3}V_{CC}$). SR flip-flop is reset, output LOW, discharge transistor ON \rightarrow pin 7 at ground \rightarrow capacitor C fully discharged (0V).

2. **Triggering (negative pulse):** A negative trigger pulse applied to pin 2 brings it below $\frac{1}{3}V_{CC}$. Comparator 2 output goes HIGH \rightarrow sets flip-flop \rightarrow output goes HIGH, discharge transistor turns OFF.
3. **Timing phase (quasi-stable):** Transistor OFF, capacitor C charges through resistor R from V_{CC} with time constant $\tau = RC$. Voltage across C rises exponentially.
4. **Threshold detection:** When capacitor voltage reaches $\frac{2}{3}V_{CC}$, Comparator 1 output goes HIGH \rightarrow resets flip-flop \rightarrow output goes LOW, discharge transistor turns ON.
5. **Discharge:** Transistor ON rapidly discharges C to 0V. Circuit returns to stable state, waiting for next trigger.

Important: The trigger pulse must be shorter than the output pulse width. The circuit is **non-retriggerable** (additional triggers during timing have no effect).

Output pulse width formula:

$$T = 1.1 \times R \times C$$

(The factor 1.1 comes from $\ln(3) \approx 1.0986$.)

Numerical example: For $R = 10k\Omega$, $C = 100\mu F$, $T = 1.1 \times 10^4 \times 10^{-4} = 1.1$ seconds.

Applications:

- Debouncing mechanical switches
- Pulse stretcher
- Delay timers
- Missing pulse detector (with retriggerable monostable)

Q.3 – Explain astable multivibrator using timer IC.

(7 marks)

Ans:

Definition: An astable multivibrator is a free-running oscillator that produces a continuous square wave without any external trigger. The 555 timer in astable mode has no stable state – it continuously switches between HIGH and LOW.

Circuit connections (555 in astable mode):

- V_{CC} to pin 8, GND to pin 1.
- Reset pin (4) to V_{CC} .
- Control voltage pin (5) grounded via $0.01\mu F$ capacitor.
- Two resistors: R_1 from V_{CC} to pin 7 (Discharge), R_2 from pin 7 to pin 6 (Threshold) and also to pin 2 (Trigger).
- Capacitor C from pin 6 (and pin 2) to ground.
- Output from pin 3.

Diagram prompt:

[DG PROMPT]

Title: 555 timer astable multivibrator circuit

Description: Draw IC 555. Connect pin 8 to Vcc, pin 1 to ground, pin 4 to Vcc, pin 5 to ground via $0.01\mu F$. Connect resistor R1 from Vcc to pin 7. Connect resistor R2 from pin 7 to pin 6. Connect pin 6 to pin 2 (short). Connect capacitor C from pin 6 to ground. Output at pin 3. Show waveforms: capacitor voltage charging from $\frac{1}{3}V_{CC}$ to $\frac{2}{3}V_{CC}$ and discharging from $\frac{2}{3}V_{CC}$ to $\frac{1}{3}V_{CC}$; output square wave with period $T = T_1 + T_2$.

Working principle (step-by-step):

1. **Initial assumption:** Assume capacitor C initially discharged (0V). Output (pin 3) is HIGH, discharge transistor (pin 7) is OFF.
2. **Charging phase (T1):** Capacitor C charges through $R_1 + R_2$ toward V_{CC} . Voltage

rises exponentially.

3. **Threshold reaching $\frac{2}{3}V_{CC}$:** Comparator 1 triggers → resets flip-flop → output goes LOW, discharge transistor turns ON (pin 7 connected to ground).
4. **Discharging phase (T₂):** Capacitor discharges through R_2 only (since pin 7 is ground, R_1 is bypassed). Voltage falls exponentially.
5. **Trigger reaching $\frac{1}{3}V_{CC}$:** Comparator 2 triggers → sets flip-flop → output goes HIGH, discharge transistor turns OFF.
6. Cycle repeats indefinitely.

Timing equations:

- **Charging time (output HIGH):**

$$T_1 = 0.693(R_1 + R_2)C$$

- **Discharging time (output LOW):**

$$T_2 = 0.693(R_2)C$$

- **Total period:**

$$T = T_1 + T_2 = 0.693(R_1 + 2R_2)C$$

- **Frequency:**

$$f = \frac{1}{T} = \frac{1.44}{(R_1 + 2R_2)C}$$

- **Duty cycle:**

$$D = \frac{T_1}{T} = \frac{R_1 + R_2}{R_1 + 2R_2} \times 100\%$$

Duty cycle < 50%: To achieve duty cycle less than 50%, add a diode in parallel with R_2 (anode to pin 7, cathode to pin 6) so that charging path is only through R_1 and discharging through R_2 .

Numerical example:

Given $R_1 = 1k\Omega$, $R_2 = 10k\Omega$, $C = 0.1\mu F$.

$T_1 = 0.693(11k)(0.1\mu) = 0.7623 \text{ ms}$, $T_2 = 0.693(10k)(0.1\mu) = 0.693 \text{ ms}$,

$f = 1.44/(1k + 20k) \times 0.1\mu = 1.44/(2.1k \times 0.1\mu) = 1.44/0.00021 = 6.857 \text{ kHz}$.

Applications:

- Clock pulse generator
- LED flasher
- Tone generator (buzzer)
- PWM generation (with duty cycle control)

Q.4 – Explain the block diagram of PLL and briefly explain its operation.

(7 marks)

Ans:

Phase-Locked Loop (PLL) is a feedback control system that locks the output frequency of a voltage-controlled oscillator (VCO) to the frequency of an input reference signal.

Block diagram of PLL:

A basic PLL consists of four functional blocks:

Block	Function
-------	----------

Block	Function
Phase Detector (PD)	Compares phase of input signal f_{in} and VCO output f_{out} , produces an error voltage proportional to phase difference.
Loop Filter (LPF)	Low-pass filter removes high-frequency components and noise from PD output, provides a DC control voltage.
Voltage-Controlled Oscillator (VCO)	Generates output frequency proportional to control voltage.
Amplifier (optional)	Amplifies the filtered error voltage to drive the VCO.

Diagram prompt:

[DG PROMPT]

Title: Block diagram of Phase-Locked Loop (PLL)

Description: Draw four rectangular blocks in sequence, with feedback. Start with input signal f_{in} to a circle labeled "Phase Detector". Second block "Loop Filter (LPF)", third block "VCO". Output of VCO is f_{out} . Feedback path: VCO output connects back to the Phase Detector (second input). Also output f_{out} is the final PLL output. Add an optional "Amplifier" between LPF and VCO. Label error voltage V_e after PD, V_c (control voltage) after LPF.

Operation (step-by-step):

1. **Free-running state:** When input signal f_{in} is absent or out of lock, the VCO runs at its free-running frequency f_o (center frequency).
2. **Capture process:** When f_{in} is applied, the phase detector compares f_{in} and f_{out} . The output is a voltage that varies with phase difference. This voltage passes through the loop filter to become V_c , which adjusts the VCO frequency toward f_{in} .
3. **Lock state:** When $f_{out} = f_{in}$ (and phase difference is constant), the phase detector output becomes a steady DC voltage (or periodic with average DC). The loop filter smooths it, and VCO stays locked.
4. **Phase lock:** The phase difference is not zero but a small constant offset needed to produce the required control voltage.

Important parameters:

- **Lock range (hold-in range):** Frequency range over which PLL can maintain lock once acquired.
- **Capture range (pull-in range):** Frequency range over which PLL can acquire lock from an unlocked state.
- **Lock-in time:** Time taken to achieve lock.

Types of Phase Detectors:

- **Analog multiplier (Gilbert cell):** For sinusoidal signals.
- **Exclusive-OR gate:** For square waves.
- **Phase-frequency detector (PFD):** For wide capture range, used in digital PLLs.

Applications:

- Frequency synthesis (clock generation)
- FM demodulation
- Frequency multiplication/division
- Clock recovery in data communication
- Motor speed control

Real-world application: PLLs are used in microcontrollers (PLL clock multiplier), radio receivers (local oscillator), and CD/DVD drives (data clock recovery).

Q.5 – What is PLL? Explain operation with basic blocks and mention four applications in radio communication.

(4 marks)

Appeared in: S25 (Q2b)

Ans:

Phase-Locked Loop (PLL) is an electronic feedback circuit that synchronizes the output frequency of a voltage-controlled oscillator (VCO) with the frequency of an input reference signal.

Basic blocks and operation:

- **Phase Detector (PD):** Compares the phase difference between input signal f_{in} and VCO output f_{out} , produces an error voltage.
- **Loop Filter (LPF):** Low-pass filter removes high-frequency components, outputs a DC control voltage.
- **VCO:** Generates output frequency proportional to the control voltage.
- **Feedback loop:** VCO output is fed back to PD. When locked, $f_{out} = f_{in}$ with constant phase difference.

Four applications in radio communication:

1. **FM demodulation** – Recovering audio from FM signals.
2. **Frequency synthesis** – Generating stable local oscillator frequencies for receivers/transmitters.
3. **Clock recovery** – Extracting timing from serial data streams (e.g., in digital radio).
4. **Frequency multiplication/division** – Generating harmonics for up/down conversion.

Q.6 – Draw block diagram of PLL and briefly explain its operation.

(7 marks)

Appeared in: S23 (Q4b, 4 marks), S22 (Q3c, 7 marks) → Highest 7 marks

Ans:

Block diagram of PLL:

[DG PROMPT]

Title: Block diagram of Phase-Locked Loop (PLL)

Description: Draw four functional blocks in sequence with a feedback path.

- Block 1 (left): Phase Detector (PD) – circle with inputs: arrow from input f_{in} and arrow from VCO output. Output arrow to Block 2.
- Block 2: Loop Filter (LPF) – low-pass filter symbol. Output arrow to Block 3.
- Block 3: Voltage-Controlled Oscillator (VCO) – output arrow to f_{out} .
- Feedback: From VCO output back to PD (second input).
- Label: Error voltage V_e after PD, Control voltage V_c after LPF. Optional amplifier between LPF and VCO.

Operation (brief):

1. **Free-running state:** No input or unlocked – VCO runs at center frequency f_o .
2. **Capture:** Input f_{in} applied – PD produces an error voltage proportional to phase difference. LPF filters it to DC control voltage, which pulls VCO frequency toward f_{in} .
3. **Lock:** When $f_{out} = f_{in}$, the phase difference is constant, producing a steady control voltage. The PLL remains locked if input frequency changes slowly within lock range.
4. **Hold-in range:** Frequency range over which lock is maintained.

5. **Capture range:** Frequency range over which lock can be acquired.

Real-world application: PLLs are used in frequency synthesizers (e.g., in mobile phones for channel selection), FM demodulators, and clock multipliers in microprocessors.

Q.7 – Design a monostable multivibrator for $T_p = 11 \mu s$, $C = 0.01 \mu F$. (3 marks)

Appeared in: W25 (Q5a)

Ans:

Given:

$$T_p = 11 \mu s = 11 \times 10^{-6} s$$

$$C = 0.01 \mu F = 0.01 \times 10^{-6} = 10^{-8} F$$

Formula: For 555 monostable, $T_p = 1.1 \times R \times C$

Solution:

$$R = \frac{T_p}{1.1 \times C} = \frac{11 \times 10^{-6}}{1.1 \times 10^{-8}} = \frac{11}{1.1} \times 10^2 = 10 \times 100 = 1000 \Omega = 1 k\Omega$$

Final Answer:

$$\boxed{R = 1 k\Omega}$$

(Use standard resistor value: 1 k Ω .)

Q.8 – Design a monostable multivibrator using timer IC for $T_p = 11 \mu s$, $C = 0.1 \mu F$. (3 marks)

Appeared in: W22 (Q5a)

Ans:

Given:

$$T_p = 11 \mu s = 11 \times 10^{-6} s$$

$$C = 0.1 \mu F = 0.1 \times 10^{-6} = 10^{-7} F$$

Formula: $T_p = 1.1 \times R \times C$

Solution:

$$R = \frac{T_p}{1.1 \times C} = \frac{11 \times 10^{-6}}{1.1 \times 10^{-7}} = \frac{11}{1.1} \times 10^1 = 10 \times 10 = 100 \Omega$$

Final Answer:

$$\boxed{R = 100 \Omega}$$

(Use 100 Ω resistor.)

Q.9 – Design an astable multivibrator using IC 555 for $T = 50\%$ duty cycle, $F = 10 kHz$, $C = 0.01 \mu F$. (4 marks)

Appeared in: W25 (Q5b)

Ans:

Given:

Duty cycle $D = 50\% \rightarrow T_1 = T_2 \rightarrow$ Charging time = Discharging time.

For 50% duty cycle, need $R_1 = 0$ (or use diode configuration). Standard circuit with diode:

Connect a diode in parallel with R_2 (anode to pin 7, cathode to pin 6). Then charging path is only through R_1 , discharging through R_2 . For 50% duty cycle, set $R_1 = R_2$.

Frequency $f = 10 kHz = 10^4 Hz$

$$C = 0.01 \mu F = 10^{-8} F$$

Formula (with diode):

$$T_1 = 0.693R_1C, T_2 = 0.693R_2C$$

$$f = \frac{1}{T_1 + T_2} = \frac{1}{0.693(R_1 + R_2)C}$$

$$\text{For } R_1 = R_2 = R, f = \frac{1}{0.693 \times 2RC}$$

Solution:

$$R = \frac{1}{0.693 \times 2 \times f \times C} = \frac{1}{0.693 \times 2 \times 10^4 \times 10^{-8}} = \frac{1}{0.693 \times 2 \times 10^{-4}} = \frac{1}{1.386 \times 10^{-4}} \approx 7215 \Omega$$

Choose $R = 7.2 \text{ k}\Omega$ (standard).

Final Answer:

$$R_1 = R_2 \approx 7.2 \text{ k}\Omega, C = 0.01 \mu F$$

(Use diode 1N4148 across R_2 .)

Q.10 – Design an astable multivibrator using IC 555 for 75% duty cycle, $F = 1 \text{ kHz}$, $C = 0.1 \mu F$.

(4 marks)

Appeared in: W22 (Q5b)

Ans:

Given:

$$\text{Duty cycle } D = 75\% = T_1 / (T_1 + T_2) = 0.75 \rightarrow T_1 = 3T_2$$

$$f = 1 \text{ kHz} \rightarrow T = 1 \text{ ms}$$

$$C = 0.1 \mu F = 10^{-7} F$$

Formulas (without diode):

$$T_1 = 0.693(R_1 + R_2)C$$

$$T_2 = 0.693R_2C$$

$$T = 0.693(R_1 + 2R_2)C = 1 \text{ ms}$$

$$\text{Also } \frac{T_1}{T} = \frac{R_1 + R_2}{R_1 + 2R_2} = 0.75$$

$$\text{Let } k = R_2/R_1. \text{ Then } \frac{1+k}{1+2k} = 0.75 \rightarrow 1+k = 0.75 + 1.5k \rightarrow 0.25 = 0.5k \rightarrow k = 0.5.$$

$$\text{So } R_2 = 0.5R_1.$$

$$\text{Now } T = 0.693(R_1 + 2 \times 0.5R_1)C = 0.693(R_1 + R_1)C = 0.693 \times 2R_1C = 1.386R_1C = 10^{-3}$$

$$R_1 = \frac{10^{-3}}{1.386 \times 10^{-7}} = \frac{10^{-3}}{1.386 \times 10^{-7}} = \frac{10^4}{1.386} \approx 7215 \Omega$$

$$R_2 = 0.5 \times 7215 \approx 3607 \Omega$$

Final Answer:

$$R_1 \approx 7.2 \text{ k}\Omega, R_2 \approx 3.6 \text{ k}\Omega, C = 0.1 \mu F$$

Q.11 – Given $R_1 = 10 \text{ k}\Omega$, $R_2 = 50 \text{ k}\Omega$, $C = 0.01 \mu F$, calculate output frequency and duty cycle of 555 astable multivibrator.

(3 marks)

Appeared in: S23 (Q5a)

Ans:

Given:

$$\begin{aligned}R_1 &= 10 \text{ k}\Omega = 10 \times 10^3 \Omega \\R_2 &= 50 \text{ k}\Omega = 50 \times 10^3 \Omega \\C &= 0.01 \mu\text{F} = 10^{-8} \text{ F}\end{aligned}$$

Formulas:

$$\begin{aligned}T_1 &= 0.693(R_1 + R_2)C \\T_2 &= 0.693R_2C \\T &= T_1 + T_2 = 0.693(R_1 + 2R_2)C \\f &= 1/T \\D &= T_1/T \times 100\%\end{aligned}$$

Solution:

$$\begin{aligned}T_1 &= 0.693(10\text{k} + 50\text{k}) \times 10^{-8} = 0.693 \times 60 \times 10^3 \times 10^{-8} = 0.693 \times 60 \times 10^{-5} \\&= 0.693 \times 0.0006 = 4.158 \times 10^{-4} \text{ s} = 0.4158 \text{ ms} \\T_2 &= 0.693 \times 50\text{k} \times 10^{-8} = 0.693 \times 50 \times 10^{-5} = 0.693 \times 0.0005 = 3.465 \times 10^{-4} \text{ s} \\&= 0.3465 \text{ ms} \\T &= 0.4158 + 0.3465 = 0.7623 \text{ ms} \\f &= 1/(0.7623 \times 10^{-3}) = 1312 \text{ Hz} \approx 1.31 \text{ kHz} \\D &= \frac{0.4158}{0.7623} \times 100\% = 54.55\%\end{aligned}$$

Final Answer:

$$f \approx 1.31 \text{ kHz}, D \approx 54.55\%$$

Q.12 – Design an astable multivibrator with ~1 kHz using given components: resistors (2.2k, 3.9k, 4.7k), 0.1μF cap, IC555.

(7 marks)

Appeared in: W23 (Q1c)

Ans:

Given: Available resistors: 2.2 kΩ, 3.9 kΩ, 4.7 kΩ; Capacitor $C = 0.1 \mu\text{F} = 10^{-7} \text{ F}$; Target frequency $f \approx 1 \text{ kHz}$.

Objective: Choose R_1 and R_2 from available values to achieve f as close as possible to 1 kHz.

Formula for 555 astable (without diode):

$$\begin{aligned}f &= \frac{1.44}{(R_1 + 2R_2)C} \\R_1 + 2R_2 &= \frac{1.44}{fC} = \frac{1.44}{10^3 \times 10^{-7}} = \frac{1.44}{10^{-4}} = 14400 \Omega = 14.4 \text{ k}\Omega\end{aligned}$$

We need $R_1 + 2R_2 = 14.4 \text{ k}\Omega$, using available resistor values (2.2k, 3.9k, 4.7k). Try combinations:

Combination	R_1 (kΩ)	R_2 (kΩ)	$R_1 + 2R_2$ (kΩ)	f (kHz)
2.2, 2.2	2.2	2.2	$2.2 + 4.4 = 6.6$	$1.44/(6.6\text{e}3 \times 1\text{e-}7) = 2.18$
2.2, 3.9	2.2	3.9	$2.2 + 7.8 = 10.0$	$1.44/(10\text{e}3 \times 1\text{e-}7) = 1.44$
2.2, 4.7	2.2	4.7	$2.2 + 9.4 = 11.6$	$1.44/(11.6\text{e}3 \times 1\text{e-}7) = 1.24$

Combination	R_1 (k Ω)	R_2 (k Ω)	$R_1 + 2R_2$ (k Ω)	f (kHz)
3.9, 2.2	3.9	2.2	$3.9 + 4.4 = 8.3$	$1.44/0.00083=1.73$
3.9, 3.9	3.9	3.9	$3.9 + 7.8 = 11.7$	$1.44/0.00117=1.23$
3.9, 4.7	3.9	4.7	$3.9 + 9.4 = 13.3$	$1.44/0.00133=1.08$
4.7, 2.2	4.7	2.2	$4.7 + 4.4 = 9.1$	$1.44/0.00091=1.58$
4.7, 3.9	4.7	3.9	$4.7 + 7.8 = 12.5$	$1.44/0.00125=1.15$
4.7, 4.7	4.7	4.7	$4.7 + 9.4 = 14.1$	$1.44/0.00141=1.02$

Best choice: $R_1 = 4.7 \text{ k}\Omega$, $R_2 = 4.7 \text{ k}\Omega$ gives $f \approx 1.02 \text{ kHz}$ (closest to 1 kHz).

Alternatively, $R_1 = 3.9 \text{ k}\Omega$, $R_2 = 4.7 \text{ k}\Omega$ gives 1.08 kHz.

Final design:

$$R_1 = 4.7 \text{ k}\Omega, R_2 = 4.7 \text{ k}\Omega, C = 0.1 \mu\text{F}$$

Expected frequency $\approx 1.02 \text{ kHz}$.

Circuit: Standard 555 astable with pin connections as per Q.3.

Q.13 – Explain applications of astable multivibrator using timer IC.

(7 marks)

Appeared in: W25 (Q5c)

Ans:

The IC 555 in **astable mode** generates a continuous square wave and has numerous applications:

1. Clock pulse generator

- Used in digital circuits (microcontrollers, counters, shift registers) as a timing source.
- Frequency can be adjusted by varying R_1 , R_2 , C .

2. LED flasher / Blinker

- Drives LEDs at desired flash rate (e.g., 1 Hz for indicator).
- Duty cycle can be set to control brightness.

3. Tone generator (Buzzer driver)

- Produces audio frequencies (200 Hz – 10 kHz) to drive a speaker or piezo buzzer.
- Used in alarms, timers, electronic metronomes.

4. Pulse Width Modulation (PWM) generator

- By adding a diode across R_2 , duty cycle can be varied from <50% to >50%.
- Applications: DC motor speed control, LED dimming, servo motor control.

5. Frequency shift keying (FSK) generator

- Two different frequencies generated by switching another resistor in parallel with R_2 .
- Used in low-cost data transmission (e.g., DTMF tones).

6. Missing pulse detector (with retriggerable monostable, but astable can be used as a reference)

- Astable provides a reference clock; missing input pulse triggers an alarm.

7. Voltage-controlled oscillator (VCO)

- By applying a control voltage to pin 5, the frequency varies.
- Used in PLLs, function generators.

8. Capacitance / Inductance meter

- Frequency of astable changes with external C or L; measure frequency to determine value.

Real-world example: A 555 astable with $f = 1 \text{ kHz}$ and 50% duty cycle can be used to drive a small DC motor with a transistor switch for speed control via PWM.

Q.14 – Write short note on voltage regulator.

(4 marks)

Appeared in: W25 (Q5b), W22 (Q5b), S23 (Q4a) → Highest 4 marks

Ans:

Voltage regulator is an electronic circuit that maintains a constant output voltage regardless of variations in input voltage or load current.

Functions:

- **Line regulation:** Rejects input voltage fluctuations (e.g., ripple from rectifier).
- **Load regulation:** Keeps output voltage stable when load current changes.
- **Output voltage setting:** Provides fixed or adjustable DC voltage.
- **Protection:** Includes overcurrent, short-circuit, and thermal shutdown.

Types of voltage regulators:

Type	Examples	Features
Linear series regulator	78XX, LM317	Low noise, simple, but inefficient for high I/O differential
Linear shunt regulator	Zener + transistor	Used for low power, reference
Switching regulator	Buck, Boost, Buck-boost	High efficiency (80–95%), more complex, noisy
Three-terminal fixed	7805 (+5V), 7912 (-12V)	Easy to use, requires input/output capacitors
Three-terminal adjustable	LM317 (positive), LM337 (negative)	Output set by two resistors

Key parameters:

- Output voltage tolerance ($\pm 2\%$ to $\pm 5\%$)
- Dropout voltage (minimum input-output difference)
- Quiescent current
- Ripple rejection (PSRR)

Real-world application: Every DC power supply (wall adapter, bench supply, battery charger) uses a voltage regulator. 7805 is common in microcontroller projects to step down 9V–12V to 5V.

Q.15 – What is a voltage regulator? List types.

(3 marks)

Appeared in: S23 (Q4a)

Ans:

Voltage regulator is a circuit that automatically maintains a constant output voltage despite changes in input voltage or load current.

Types of voltage regulators:

1. **Based on operation mode:**
 - Linear regulator (series or shunt)
 - Switching regulator (buck, boost, buck-boost, Cuk)
2. **Based on output polarity:**
 - Positive voltage regulators (78XX series)
 - Negative voltage regulators (79XX series)
3. **Based on adjustability:**
 - Fixed voltage regulators (e.g., 7805, 7812)
 - Adjustable voltage regulators (e.g., LM317, LM338)
4. **Based on application:**
 - Low dropout regulators (LDO)
 - High voltage regulators
 - Precision reference (TL431)

Q.16 – Explain simple op-amp voltage regulator, three-terminal regulators (78XX, LM317), heat sink, dual power supply.**(7 marks)** (from syllabus – provide comprehensive answer)**Ans:****A. Simple op-amp voltage regulator (series pass):**

- **Circuit:** Op-amp as error amplifier, Zener diode as reference, pass transistor (BJT/MOSFET) in series with load.
- **Operation:** Output voltage sampled by voltage divider and compared to Zener reference. Op-amp amplifies the error and drives the pass transistor to keep output constant.
- **Output voltage:** $V_o = V_{ref} \times (1 + R_2/R_1)$.

B. Three-terminal fixed regulators (78XX series):

- **78XX:** Positive voltage regulators (7805 = +5V, 7812 = +12V).
- **79XX:** Negative voltage regulators (7905 = -5V).
- **Pinout (TO-220):** Input, Ground, Output.
- **Typical application:** Connect input and output capacitors (0.33 μ F at input, 0.1 μ F at output) for stability.
- **Features:** Built-in overcurrent protection, thermal shutdown, safe-area protection.

C. Three-terminal adjustable regulator (LM317):

- **LM317** – positive adjustable regulator (1.25V to 37V).
- **Pinout:** Adjust, Output, Input (TO-220).
- **Output voltage formula:** $V_o = 1.25 \times (1 + R_2/R_1) + I_{adj}R_2$. Typically $I_{adj} \approx 100\mu A$ and $R_1 = 240\Omega$.
- **Application circuit:** R_1 between Output and Adjust, R_2 from Adjust to ground.

D. Heat sink:

- **Purpose:** Dissipate heat generated by the regulator (power loss $P = (V_{in} - V_o) \times I_L$).
- **Material:** Aluminum (extruded or stamped).
- **Thermal resistance θ_{JA}** determines temperature rise.
- **Selection:** Ensure junction temperature $T_j < 150^\circ C$.
- **Installation:** Use thermal grease or insulating pad.

E. Dual power supply:

- Provides both positive and negative regulated voltages (e.g., $\pm 12V$ for op-amps).
- **Construction:** Use a center-tapped transformer, full-wave rectifier, then 7812 (positive) and 7912 (negative) regulators.
- **Common ground:** Connect the common terminal of both regulators together.

Diagram prompt (dual supply):

[DG PROMPT]

Title: Dual power supply using 7812 and 7912

Description: Draw center-tapped transformer secondary. Two diodes for positive half and two for negative? Better: Full-wave rectifier with center tap as ground. Positive output to 7812 (Input), negative output to 7912 (Input). Ground common. 7812 Output gives +12V, 7912 Output gives -12V. Add capacitors on input and output of each regulator.

Q.17 – Design an adjustable voltage regulator using LM317 for $V_o = 5$ to $12V$, $I_o = 1A$, $I_{adj} = 100\mu A$, $R_1 = 240\Omega$.

(7 marks)*Appeared in: W23 (Q5c)***Ans:****Given:**Output range: $V_{o(min)} = 5V$, $V_{o(max)} = 12V$ Load current $I_o = 1A$ (max)

$$I_{adj} = 100\mu A = 10^{-4}A$$

 $R_1 = 240\Omega$ (connected between Output and Adjust pins)**Formula for LM317:**

$$V_o = 1.25 \left(1 + \frac{R_2}{R_1}\right) + I_{adj}R_2$$

where $V_{ref} = 1.25V$ (internal reference).**Step 1: Find R_2 for $V_o = 5V$**

$$5 = 1.25 \left(1 + \frac{R_2}{240}\right) + 10^{-4}R_2$$

$$5 - 1.25 = 1.25 \times \frac{R_2}{240} + 10^{-4}R_2$$

$$3.75 = \frac{1.25}{240}R_2 + 0.0001R_2 = (0.0052083 + 0.0001)R_2 = 0.0053083R_2$$

$$R_2 = \frac{3.75}{0.0053083} \approx 706 \Omega$$

Step 2: Find R_2 for $V_o = 12V$

$$12 = 1.25 \left(1 + \frac{R_2}{240}\right) + 10^{-4}R_2$$

$$12 - 1.25 = \frac{1.25}{240}R_2 + 0.0001R_2$$

$$10.75 = 0.0053083R_2$$

$$R_2 = \frac{10.75}{0.0053083} \approx 2025 \Omega$$

Step 3: Select practical potentiometer

Use a potentiometer R_2 variable from about 700Ω to 2025Ω . Standard value: $2.5 \text{ k}\Omega$ (or $2.2 \text{ k}\Omega$ + series resistor). For continuous adjustment, use a $2 \text{ k}\Omega$ pot in series with a fixed 220Ω to get range $\sim 220\Omega$ to 2220Ω .

Step 4: Additional components

- Input capacitor $C_{in} = 0.33\mu F$ (ceramic)
- Output capacitor $C_{out} = 1\mu F$ (tantalum or electrolytic)
- Protection diode across input-output (1N4007)

- Heat sink for LM317 (power dissipation $P = (V_{in} - V_o) \times I_o$, choose V_{in} at least 15V for 12V output)

Final Answer:

$$R_1 = 240\Omega, R_2 \approx 700\Omega \text{ to } 2025\Omega \text{ (use 2.5k pot)}$$

Q.18 – Explain the design of LM317-based voltage regulator with example.

(7 marks)

Appeared in: W24 (Q5c)

Ans:

Design procedure for LM317 adjustable voltage regulator:

Step 1: Determine required output voltage range

Example: Design a regulator to output $V_o = 9V$ at 1A.

Step 2: Choose R_1 value

LM317 datasheet recommends $R_1 = 240\Omega$ (or 120Ω for higher output current). R_1 sets the minimum load current.

Step 3: Calculate R_2 using formula

$$V_o = 1.25 \left(1 + \frac{R_2}{R_1}\right) + I_{adj}R_2$$

Neglect I_{adj} for first approximation (error < 1%):

$$9 \approx 1.25 \left(1 + \frac{R_2}{240}\right) \Rightarrow \frac{9}{1.25} = 1 + \frac{R_2}{240} \Rightarrow 7.2 = 1 + \frac{R_2}{240} \Rightarrow \frac{R_2}{240} = 6.2 \Rightarrow R_2 = 1488\Omega$$

Use standard 1.5 k Ω .

Step 4: Select components

- $C_{in} = 0.33\mu F$ (ceramic) close to input pins
- $C_{out} = 1\mu F$ (tantalum) at output
- Protection diode D_1 from output to input (in case of shorted input)
- Protection diode D_2 from adjust to output (prevents capacitor discharge into adjust pin)

Step 5: Heat sink calculation

Power dissipation $P = (V_{in} - V_o)I_o$. Choose $V_{in} \approx V_o + 3V = 12V$ (dropout $\sim 2V$, plus safety).

$$P = (12 - 9) \times 1 = 3W.$$

Thermal resistance θ_{JA} of LM317 (TO-220) without heatsink $\sim 65^\circ C/W \rightarrow$ temperature rise $195^\circ C$ (exceeds $125^\circ C$). Need heatsink.

Required θ_{HS} : $T_j - T_a = P \times (\theta_{JC} + \theta_{CS} + \theta_{SA})$. For $T_j = 125^\circ C, T_a = 40^\circ C, \theta_{JC} \approx 3^\circ C/W, \theta_{CS} \approx 1^\circ C/W$:

$$85 = 3 \times (3 + 1 + \theta_{SA}) \Rightarrow \theta_{SA} \approx 24^\circ C/W. \text{ Use a small clip-on heatsink.}$$

Example design summary:

- $R_1 = 240\Omega, R_2 = 1.5\text{ k}\Omega$ (fixed) for 9V output. For adjustable, use 2.5k pot.
- Input voltage: 12V DC (from rectified transformer).
- Capacitors: $C_{in} = 0.33\mu F, C_{out} = 1\mu F, C_{adj} = 10\mu F$ (improves ripple rejection).
- Heatsink: TO-220 heatsink with $\theta_{SA} < 25^\circ C/W$.

Final Answer: LM317 with $R_1 = 240\Omega, R_2 = 1.5\text{ k}\Omega$ gives $V_o \approx 9V$.

Q.19 – What are advantages of adjustable over fixed voltage regulators?

(3 marks)

Appeared in: S22 (Q3a OR)

Ans:

Advantages of adjustable voltage regulators (e.g., LM317) over fixed regulators (e.g., 7805):

1. **Versatility** – One device can produce any output voltage within its range (1.25V to 37V) by changing two external resistors.
2. **Higher output voltage** – Fixed regulators are limited to standard values (5V, 12V, 15V). Adjustable can provide non-standard voltages (e.g., 8.5V, 14.2V).
3. **Better regulation** – Adjustable regulators often have lower temperature coefficient and tighter line/load regulation.
4. **Programmable** – Can be used as current source, battery charger, or with external pass transistor for higher current.
5. **Floating operation** – The LM317 can regulate high voltages (up to 37V differential) independent of ground.
6. **Lower dropout voltage** – Some adjustable LDOs (e.g., LM1085) have lower dropout than fixed 78xx series.

Disadvantage: Requires two external resistors and optionally a potentiometer, increasing component count.
