

GUJARAT TECHNOLOGICAL UNIVERSITY

BE- SEMESTER-III (NEW) EXAMINATION – WINTER 2024

Subject Code: 3130907

Date: 29-11-2024

Subject Name: Analog & Digital Electronics

Time: 10:30 AM TO 01:00 PM

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

MARKS

- | | | |
|------------|---|-----------|
| Q.1 | (a) Explain memory and differentiate between 1-bit memory and 1-byte memory. | 03 |
| | (b) Describe Amplifiers and Oscillators. State basic difference between them. | 04 |
| | (c) Draw and explain working of zero crossing detector, and state its applications. | 07 |
| Q.2 | (a) Define input bias current, input offset current, and slew rate. | 03 |
| | (b) State the non-idealities in an op-amp. | 04 |
| | (c) Draw and explain the internal structure of an operational amplifier. | 07 |
| | OR | |
| | (c) Draw and explain the working of a differential amplifier. | 07 |
| Q.3 | (a) Write the features of an ideal op-amp. | 03 |
| | (b) Draw and explain Op-Amp as an integrator. | 04 |
| | (c) Draw and explain the working of an inverting amplifier. | 07 |
| | OR | |
| Q.3 | (a) Explain Op-amp as phase shift amplifier. | 03 |
| | (b) Draw and explain Op-Amp as an instrumentation amplifier. | 04 |
| | (c) Draw and explain summing amplifier. | 07 |
| Q.4 | (a) Compare combinational and sequential circuits. | 03 |
| | (b) Draw and explain peak detector. | 04 |
| | (c) State and explain don't care conditions in K-Map. Give suitable example. | 07 |
| | OR | |
| Q.4 | (a) Explain in brief the difference between latch and flip-flop. | 03 |
| | (b) Draw and explain precision rectifier. | 04 |
| | (c) State truth table of full subtractor and design it using 3 X 8 decoder. | 07 |
| Q.5 | (a) State applications of shift registers. | 03 |
| | (b) Explain parallel comparator A/D converter | 04 |
| | (c) Discuss asynchronous and synchronous counters. Compare them. | 07 |
| | OR | |
| Q.5 | (a) Explain sample and hold circuit. | 03 |
| | (b) Draw and explain the working of RS Flip-Flop. | 04 |
| | (c) Draw and explain the working of successive approximation A/D converter. | 07 |
