

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III (NEW) EXAMINATION – WINTER 2023

Subject Code:3130907

Date:18-01-2024

Subject Name:Analog & Digital Electronics

Time:10:30 AM TO 01:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) Draw transistor C-E amplifier circuit. Draw its ac equivalent circuit.	03
	(b) What is cross over distortion in power amplifier?	04
	(c) Draw equivalent circuit of OP-Amp. Explain each part.	07
Q.2	(a) List applications of instrumentation amplifier.	03
	(b) Prove that voltage follower has unity gain.	04
	(c) Discuss the classification of active filter and explain the frequency response of each type.	07
	OR	
	(c) What do you mean by slew rate in an OP-AMP? Also mention about causes of slew rate and explain its significance in applications.	07
Q.3	(a) How to detect peak of waveform using OP-AMP?	03
	(b) Sketch and explain Wein bridge oscillator.	04
	(c) Draw and explain the use of op-amp as a zero-crossing detector.	07
	OR	
Q.3	(a) Explain how to generate triangular wave using OPAMP.	03
	(b) Write a short note on Precision rectifier.	04
	(c) Draw and explain the block diagram of basic three terminal IC regulator.	07
Q.4	(a) Explain the different types of triggering methods used for flip flops.	03
	(b) Write short note on binary codes.	04
	(c) Explain Master-Slave J-K flip-flop configuration.	07
	OR	
Q.4	(a) What is multiplexer?	03
	(b) Design full adder circuit.	04
	(c) Minimize following Boolean function using K-map and implement using basic logic gates: $F(A,B,C,D) = \sum m(1, 2, 3, 8, 9, 11, 14)$ with $d(7, 15)$	07
Q.5	(a) Define following specification of DAC a) Accuracy b) Resolution c) Setting time	03
	(b) Compare combinational logic circuit with sequential logic circuit.	04
	(c) Design a 4 bit synchronous up counter.	07

OR

- | | | |
|------------|--|-----------|
| Q.5 | (a) Sketch sample and hold circuit and explain its working. | 03 |
| | (b) Which are the different methods for A/D conversion? | 04 |
| | (c) Explain in detail 7 segment LED display. | 07 |
