

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III EXAMINATION – SUMMER 2025****Subject Code:3130907****Date:31-05-2025****Subject Name:Analog & Digital Electronics****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) State all ideal characteristics of an opamp	03
	(b) Describe Input Offset Voltage and Input Bias Current	04
	(c) Describe the working of JK master slave FF with necessary truth tables and waveforms	07
Q.2	(a) Discuss the working of Zero Crossing Detector with necessary diagram and waveforms	03
	(b) Sketch the block diagram of an opamp and briefly explain the function of each block	04
	(c) Discuss (i) CMRR (ii) Slew Rate	07
	OR	
	(c) Explain the working of an Integrator with necessary diagrams	07
Q.3	(a) Compare RC phase shift and Wien bridge oscillator	03
	(b) A noninverting opamp with $R_1 = 1k\Omega$ and $R_F = 10k\Omega$ has following parameters: $A = 200,000$, $R_i = 2M\Omega$, $R_o = 75\Omega$, $f_o = 5Hz$, Supply voltages $= \pm 15V$, Output Voltage Swing $= \pm 13V$. Solve and find the values of A_F , R_{iF} , R_{oF}	04
	(c) Describe the working of Instrumentation Amplifier using opamp. List it's advantages and applications	07
	OR	
Q.3	(a) Write a brief note on Voltage Follower circuit	03
	(b) Compare a Comparator and Schmitt Trigger circuit	04
	(c) Explain the working of closed loop opamp in non-inverting mode and derive the voltage gain formula	07
Q.4	(a) Compare Combinational and Sequential Digital circuits	03
	(b) Discuss the applications of shift registers	04
	(c) Minimize the following expressions using K maps:	07
	(i) $F = \sum m(4,5,7,12,14,15) + \sum d(3,8,10)$	
	(ii) $F = \prod M(0,3,7,8,9,10,11,15) \cdot \prod d(2,4)$	
	OR	
Q.4	(a) List the steps to be followed in Quine Mckluskey method	03
	(b) Describe the working of a decimal to binary encoder with the help of logic diagram and truth table	04
	(c) Write a note on Ring Counter	07
Q.5	(a) Explain the following terms of DAC: a) Accuracy b) Resolution c) Setting time	03
	(b) Explain resolution and quantization error about ADC	04

- (c) Draw & explain R-2R ladder D/A converter with necessary equations **07**

OR

- Q.5** (a) List Analog to Digital Converter ICs **03**
(b) Illustrate different methods for analog to digital conversion **04**
(c) Draw the block diagram and explain about a 3 terminal voltage regulator **07**
