

GUJARAT TECHNOLOGICAL UNIVERSITY**BE- SEMESTER– III EXAMINATION – SUMMER 2026****Subject Code:3130906****Date:17-06-2026****Subject Name:Electrical Circuit Analysis****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) State Thevenin and Norton theorem.	03
	(b) Discuss short-circuit admittance parameters and draw equivalent circuit for short circuit admittance parameters.	04
	(c) In the network shown in fig.1, contains two voltage sources V_1 and V_2 . With $V_1=30\angle 0^\circ$ V, Calculate V_2 such that the current in the $2+j3\ \Omega$ impedance is zero.	07
Q.2	(a) In the circuit shown in fig.2, a dc voltage suddenly applied to a series circuit. The inductor and capacitor are initially uncharged. Determine the particular solution for current $i(t)$ in the circuit.	03
	(b) Describe maximum power transfer theorem and write different conditions for maximum power transfer theorem for AC circuits.	04
	(c) Explain Superposition theorem with suitable example.	07
	OR	
	(c) Explain Reciprocity theorem with suitable example.	07
Q.3	(a) Elaborate series-parallel connection for two-port network.	03
	(b) Define Kirchhoff Voltage Law and Kirchhoff Current Law with suitable example.	04
	(c) In the network shown in fig.3, a steady state is reached with the switch k open. At time $t=0$. Switch k is closed. For the element values given, Figure out the values $V_a(0^-)$ and $V_a(0^+)$.	07
	OR	
Q.3	(a) Explain parallel-parallel connection for two-port network.	03
	(b) List difference between ideal and practical voltage source and Describe about source transformation.	04
	(c) In the network shown in fig.4, the switch k is moved from position 1 to 2 at $t=0$ a steady state having previously been attained. Find out $d^2i/dt^2(0^+)$ at $t=0^+$.	07
Q.4	(a) Explore the dual of the network shown in Fig.5.	03
	(b) In the network shown in fig.6, a steady state is reached with the switch k open. At $t=0$ the switch k is closed, Compute $i(t)$ for the numerical values given.	04
	(c) In the network of fig.7, the switch k is opened at time $t=0$. Evaluate the particular solution for voltage $v(t)$ across the parallel circuit using Laplace transformation. Assume that there is no charge across the capacitor C and no current in the inductor L before switching.	07
	OR	
Q.4	(a) In the two mesh network shown in fig.8, Identify the mesh currents I_1 and I_2 .	03
	(b) In the network shown in fig.9, the network attains a steady state, and at $t=0$, the switch is closed. Calculate $V_a(t)$ for $t \geq 0$.	04

- (c) In a series R-L-C circuit, $R=5\Omega$, $L=1\text{H}$ and $C=0.25\text{ F}$ and $v(t) = 8e^{-2t}$ Volts. Switch k is closed at time $t=0$. Evaluate particular solution for the current using Laplace transform method. Assume zero initial conditions in the elements. 07

- Q.5** (a) Find out reciprocity condition for g-Parameters. 03
 (b) Generalize relationship of h-parameter to z-parameters. 04
 (c) For the network shown in fig.10, the switch k is closed at time $t=0$. Capacitor C is initially charged to V_0 volts. Using Laplace transformation method, discover the expression for the current $i(t)$. 07

OR

- Q.5** (a) Find out symmetry condition for inverse ABCD-parameters 03
 (b) Generalize relationship of ABCD-parameters to y-parameters. 04
 (c) In R-L circuit shown in fig.11, the switch is in position 1 long enough to establish steady state conditions and at $t=0$ is switched to position 2. Discover the expression for the current in the circuit using Laplace transform. 07

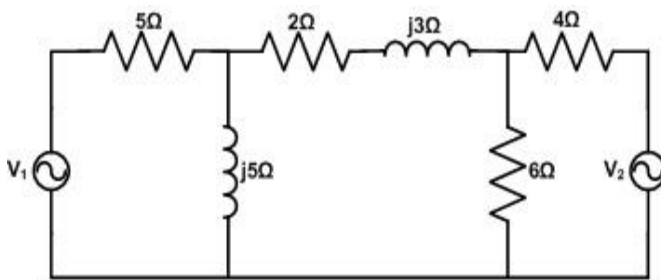


Fig.01

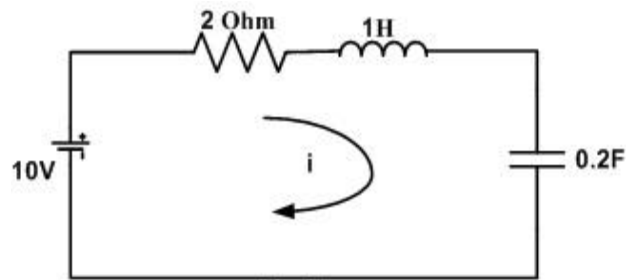


Fig.2

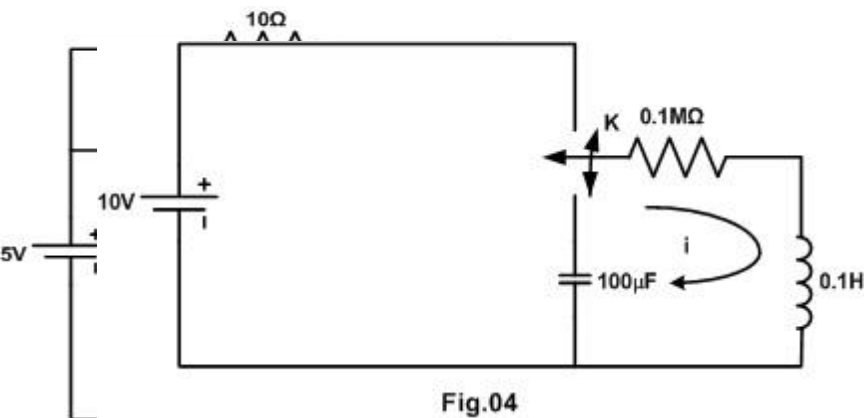


Fig.04

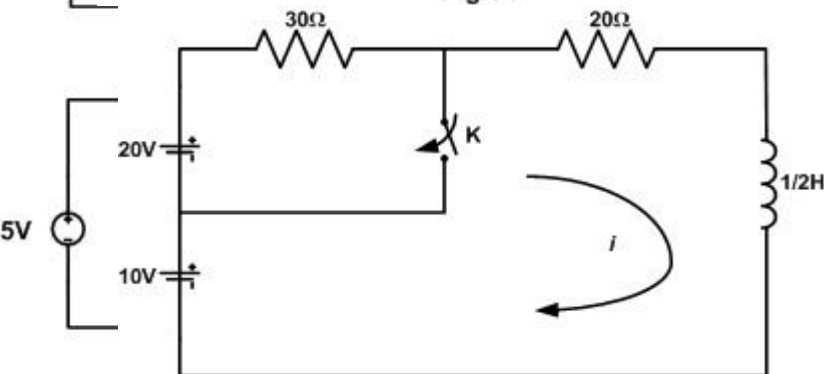


Fig.06

