

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III (NEW) EXAMINATION – WINTER 2023

Subject Code:3130906

Date:16-01-2024

Subject Name:Electrical Circuit Analysis


Time:10:30 AM TO 01:00 PM

Total Marks:70


Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

- | | | Marks |
|-----|--|-------|
| Q.1 | (a) Explain Norton's theorem. | 03 |
| | (b) Develop Step by step solution to solve electrical networks by using Superposition Theorem. | 04 |
| | (c) Determine the load current of figure 1 given below using Thevenin's Theorem. | 07 |

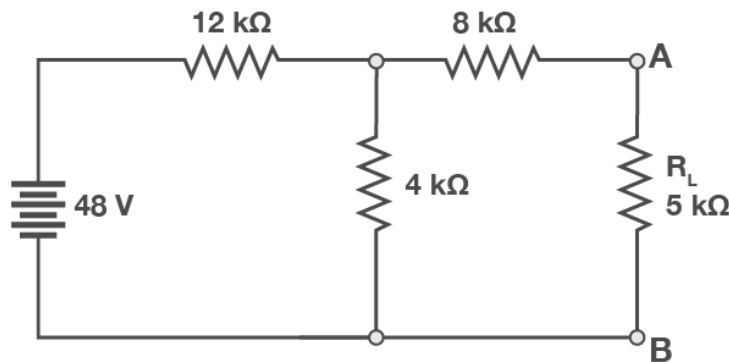


- | | | |
|-----|--|----|
| Q.2 | (a) Explain in brief about the ideal transformer. | 03 |
| | (b) Derive the step response to R-L series circuit using Laplace Transformation method. | 04 |
| | (c) For the circuit shown in Figure 2 switch K is changed from position a to b at $t=0$, steady state condition having been reached before switching. Find the values of i ; di/dt , d^2i/dt^2 at $t = 0^+$. | 07 |

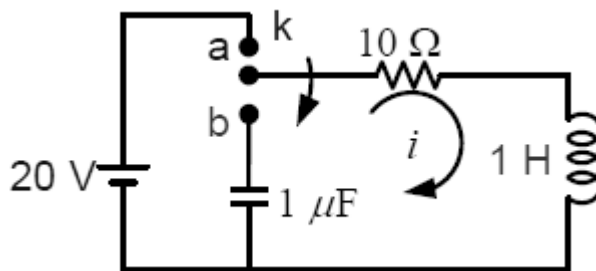

OR

- | | | |
|-----|--|----|
| (c) | In the circuit shown in Figure 3 determine the mesh currents i_1, i_2, i_3 | 07 |
|-----|--|----|

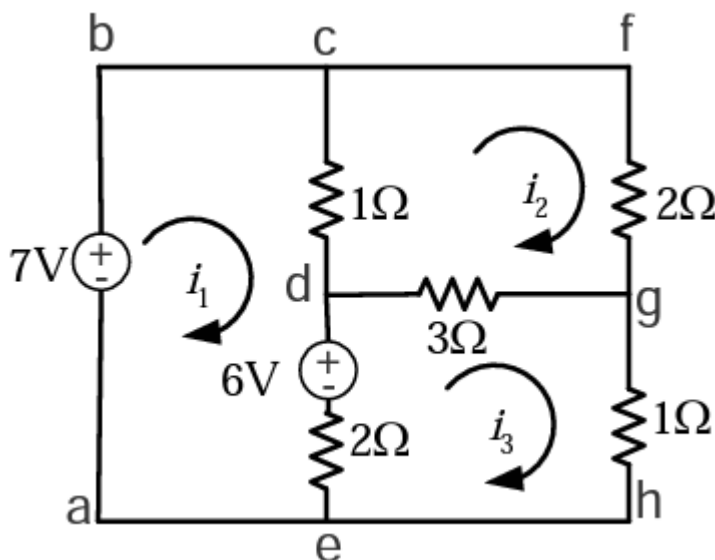

- Q.3**
- (a) Explain the initial condition in different passive electrical elements. What is the importance of initial conditions in network analysis? **03**
 - (b) Discuss why. **04**
 - (i) The current in inductor cannot change instantaneously.
 - (ii) The voltage across a capacitor cannot change instantaneously.
 - (c) Prove Initial and Final Value theorems. **07**


OR

- Q.3**
- (a) Explain the importance of Dot convention in coupled circuit with suitable example. **03**
 - (b) What are the properties of Laplace transformation? Explain in detail. **04**
 - (c) What is time constant? What is its significance? Illustrate through an example. **07**

- Q.4**
- (a) Specify the term (i) RMS values (ii) Apparent power (iii) Complex power. **03**
 - (b) Convert the capacitance C (passive element) to Laplace domain using Laplace transformation. **04**
 - (c) Define poles and zeros of network function. Explain significance of poles and zeros in different network functions. **07**

OR

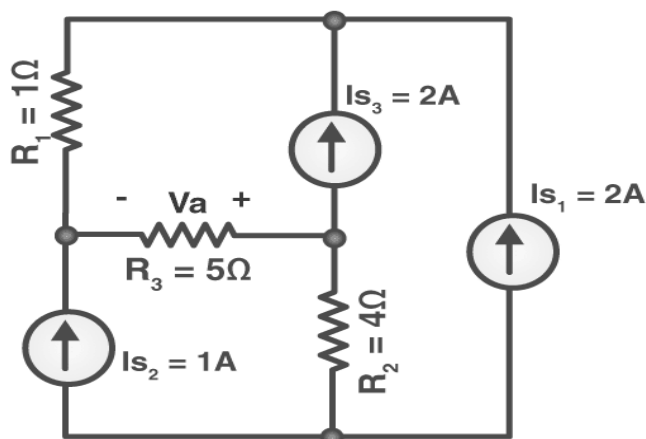- Q.4**
- (a) Explain characteristics of unit ramp function. **03**
 - (b) Explain time constant in case of series R-L and series R-C circuit. **04**
 - (c) Find the value of voltage across R_3 resistance of figure 4 using Nodal Analysis. **07**



- Q.5** (a) What is the condition of symmetry of all different two port parameters? **03**
 (b) Generalize relationship of h-parameters to y-parameters. **04**
 (c) Obtain ABCD parameters in terms of Z-parameters for a two-port network. **07**

OR

- Q.5** (a) Define H-parameter of a two-port network. **03**
 (b) Find out reciprocity condition for h-Parameters. **04**
 (c) Determine Y-parameters of the circuit shown in figure 5. **07**

