

GUJARAT TECHNOLOGICAL UNIVERSITY

BE- SEMESTER- III EXAMINATION – SUMMER 2026

Subject Code:3131102

Date:19-06-2026

Subject Name:Digital System Design

Time:02:30 PM TO 05:00 PM



Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

Marks

  - Q.1** (a) What do you mean by positional weighted system. Name some positional weighted system. **03**
- (b) Given that $292_{10} = 1204_b$ Than find the value of b. **04**
- (c) What are the characteristic of 2's complement numbers. What are the three methods of obtaining 2's complement of given number. Explain with suitable example. **07**
- Q.2** (a) Write a short note on Gray Codes. **03**
- (b) If the waveforms A, B, C are applied to the gate circuit shown below, determine the output waveform. **04**



- (c) Write a short note on magnitude comparator. **07**
- OR**
- (c) Write a short note on binary full adder and implement the circuit using universal logic. **07**
- Q.3** (a) How do you convert AOI logic to universal logic. **03**
- (b) Reduce using mapping the expression $f = \sum m(0, 1, 2, 3, 5, 8, 9, 10, 12, 13)$ **04**
- (c) Explain working principal of Master Slave flip flop using suitable diagram. **07**

OR

- Q.3** (a) Why do we need to reduce Boolean expression before realization. What is the systematic procedure to reduce the Boolean expression? **03**
(b) Write a Short note on SR flip flop **04**
(c) Explain Quine-McCluskey method for the minimization of Boolean expression. **07**

- Q.4** (a) Write a short note on programmable array logic. **03**
(b) Give comparison of programmable logic device such as PROM, PAL, PLA. **04**
(c) Write a short note on TTL logic families. **07**

OR

- Q.4** (a) Distinguished between combinational and sequential logic circuit. **03**
(b) What are moore and mealy machines? Compare them. **04**
(c) Write a short note on universal shift register. **07**

- Q.5** (a) Write a short note on weighted resistor type D to A converter. **03**
(b) Explain R-2R ladder type D to A converter. **04**
(c) Explain following parameter for D to A conversion. **07**
Resolution, Accuracy, settling time, offset voltage.

OR

- Q.5** (a) What do you mean by test bench in VHDL design. **03**
(b) List and explain the data types used in HDL **04**
(c) Compare data flow ,behavioral and structural modeling. **07**

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III EXAMINATION – SUMMER 2025****Subject Code:3131102****Date:31-05-2025****Subject Name:Digital System Design****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) Convert the decimal Number 250.5 to base 4 and base 8.	03
	(b) State and prove DeMorgan's Theorem.	04
	(c) Minimize the following function in SOP and POS minimal form using K-Maps: $F(A, B, C, D) = \sum m(1, 2, 6, 7, 8, 13, 14, 15) + d(3, 5, 12)$	07
Q.2	(a) Convert $F(A,B,C) = BC+A$ into standard minterm form.	03
	(b) Implement Ex -NOR and Ex-OR using NAND and NOR only.	04
	(c) Implement the full adder & full subtractor using Multiplexer.	07
	OR	
	(c) Design and implement binary to Excess-3 code converter.	07
Q.3	(a) Obtain the truth table of the function: $F = xy+yz+zx$.	03
	(b) Obtain JK flip-flop from SR flip-flop.	04
	(c) Draw the circuit diagrams and truth table of SR, D, T and JK flip flops.	07
	OR	
Q.3	(a) What is "Lock out" condition in counter? How to avoid it?	03
	(b) Implement 4x16 decoder using two 3x8 decoder.	04
	(c) Explain Master Slave JK flip-flop with truth table and circuit diagram.	07
Q.4	(a) Compare sequential and combinational circuits.	03
	(b) Define the following characteristics of IC: (i) Propagation Delay (ii) Figure of Merit (iii) Fan out (vi) Noise Margin	04
	(c) Compare ROM, PLA and PAL.	07
	OR	
Q.4	(a) Compare Latch and a Flip flop.	03
	(b) Give classification of logic families and compare CMOS and TTL.	04
	(c) Explain Moore machine.	07
Q.5	(a) List the steps in VLSI Design flow.	03
	(b) Design Modulo-8 counter using T flip flop.	04
	(c) With neat sketch design 4-bit bidirectional shift register.	07
	OR	
Q.5	(a) Define State Table and State Diagram.	03
	(b) Design mod-6 asynchronous counter using T flip-flop.	04
	(c) Design 4-bit ripple counter using negative edge triggered JK flip flop.	07

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III (NEW) EXAMINATION – SUMMER 2024****Subject Code:3131102****Date:29-06-2024****Subject Name: Digital System Design****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) Convert the decimal number 250.5 to base 3, base 7 and base 8.	03
	(b) Show that NAND Gate is a Universal Gate.	04
	(c) simplify the following Boolean function, $F(w,x,y,z)=\sum m(2,6,8,9,10,11,14,15)$ using Quine-McClukey tabular Method.	07
Q.2	(a) Show that $(A \oplus B \oplus C)' = (A \odot B \odot C)$.	03
	(b) Obtain the truth table of the function: $F = xy + xy' + y'z$.	04
	(c) Minimize the logic function $F(A,B,C,D) = \Pi_M(1, 2, 3, 8, 9, 10, 11, 14)$ using K map & Draw the logic circuit for the simplified function using NOR gates only.	07
	OR	
	(c) What is multiplexer? With logic circuit and function table explain the working of 4 to 1 line multiplexer.	07
Q.3	(a) What is race around condition in JK flip flop?	03
	(b) List out problems of asynchronous circuit. Also exemplify any two problems with suitable examples.	04
	(c) With necessary sketch explain Bidirectional Shift Register with parallel load.	07
	OR	
Q.3	(a) Implement 8x1 MUX using 4x1 MUX.	03
	(b) Implement 4x16 decoder using two 3x8 decoder.	04
	(c) Explain working of master-slave JK flip-flop with necessary logic diagram, state equation and state diagram.	07
Q.4	(a) Define the terms 1. Fan out 2.Noise Margin 3. Fan in	03
	(b) Design Modulo-8 counter using T flip flop.	04
	(c) Explain Moore machine.	07
	OR	
Q.4	(a) How many flip-flops are required to build a digital counter to count from 0 to 63? Justify.	03
	(b) What are the classifications of Logic families? Also list the characteristics of digital IC.	04
	(c) Compare ROM, PLA and PAL.	07
Q.5	(a) List the steps in VLSI Design flow.	03
	(b) Describe General State Machine Architecture with suitable diagrams.	04
	(c) Design a synchronous BCD counter with JK flip-flops.	07
	OR	
Q.5	(a) Implement T flip flop using D flip flop.	03
	(b) Explain 4 bit serial in serial out shift register.	04
	(c) Design 4-bit ripple counter using negative edge triggered JK flip flop.	07

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III(NEW) EXAMINATION – SUMMER 2023****Subject Code:3131102****Date:28-07-2023****Subject Name:Digital System Design****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

	Marks
Q.1 (a) Convert the following numbers form given base to the base indicates.	03
(1) $(AEF2.B6)_{16} = (\quad)_{2}$	
(2) $(674.12)_8 = (\quad)_{10}$	
(3) $(110110.1011)_2 = (\quad)_{16}$	
(b) State and prove DeMorgan's Theorem.	04
(c) simplify the following Boolean function, $f(w,x,y,z) = \sum m(2,6,8,9,10,11,14,15)$ using Quine-McClukey tabular Method.	07
Q.2 (a) Obtain canonical Sum of Product form of following function: $F = AB + ACD$.	03
(b) Show that NAND & NOR are universal gates.	04
(c) Implement the following Boolean functions with a multiplexer and Decoder. $F(w, x, y, z) = \sum (2, 3, 5, 6, 11, 14, 15)$	07
OR	
(c) Design and implement binary to gray code converter.	07
Q.3 (a) Implement 8x1 MUX using 4x1 MUX.	03
(b) Give the comparison between synchronous and asynchronous counters.	04
(c) Explain JK flip flop with its characteristic table and excitation table.	07
OR	
Q.3 (a) What is race around condition in JK flip flop?	03
(b) Implement 4x16 decoder using two 3x8 decoder.	04
(c) Explain Master Slave JK flip-flop with truth table and circuit diagram	07
Q.4 (a) Define following terms w.r.t Digital Logic Family: 1. Figure of merit 2.Noise Margin 3. Power Dissipation	03
(b) Describe General State Machine Architecture with suitable diagrams.	04
(c) Compare ROM, PLA and PAL.	07
OR	
Q.4 (a) Define following terms w.r.t State Machine 1. State Table 2. State Diagram	03
(b) Give classification of logic families. Also list the characteristics of digital IC.	04
(c) Explain Moore machine.	07
Q.5 (a) List the steps in VLSI Design flow.	03
(b) Design Modulo-8 counter using T flip flop.	04

(c) With neat sketch design 4-bit bidirectional shift register. **07**

OR

Q.5 (a) Explain the problem associate of an asynchronous state machine with the help of one example. **03**

(b) Design 3-bit synchronous up counter using T flip flop. **04**

(c) Design 4-bit ripple counter using negative edge triggered JK flip flop. **07**
