

Enrolment No./Seat No _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE- SEMESTER- V EXAMINATION – SUMMER 2026

Subject Code:3151106

Date:25-05-2026

Subject Name:Power Electronics

Time:02:30 PM TO 05:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks	CO (Course Outcome)	Cognitive Level (As per Revised Bloom's Taxonomy)
Q.1	(a) Explain the various Turn On methods of SCR.	03	CO-2	U
	(b) What are dv/dt and di/dt ratings of SCR? What happens if these rating exceeded? Explain	04	CO-1	U
	(c) What is commutation? Explain complementary commutation circuit.	07	CO-2	E
Q.2	(a) Explain snubber circuit.	03	CO-1	
	(b) With help of neat diagram and associated waveform, explain the operation of resistance triggering circuit	04	CO-2	A
	(c) A single phase semi converter is operated from 120 V, 60 Hz ac supply. The load resistance is $10\ \Omega$, if the average output voltage is 25% of the maximum possible average output voltage, finds: 1. Delay angle 2. Average and rms output voltage 3. Average and rms thyristor current.	07	CO-4	A
	OR			
	(c) A DC type A chopper has resistive load $20\ \Omega$ and input voltage of 220 volts. When the chopper remains on, its voltage drop is $V_{ch} = 1.5$ volts and chopping frequency is 10 kHz, if duty cycle is 80% determine: 1. Average output voltage 2. RMS output voltage 3. Chopper efficiency 4. Effective input resistance.	07	CO-5	E
Q.3	(a) What is the function of Chopper? Explain the working of step down chopper.	03	CO-5	U
	(b) With help of circuit diagram explain the working of class D chopper.	04	CO-5	A
	(c) With help of neat circuit diagram and waveforms, explain the operation of PWM full bridge inverter with resistive load.	07	CO-5	A
	OR			
Q.3	(a) Explain the multiphase choppers.	03	CO-5	A
	(b) With help of circuit diagram explain the working of class B chopper.	04	CO-5	N

	(c)	With help of neat circuit diagram and waveforms, explain the operation of single phase current source inverter.	07	CO-5	U
Q.4	(a)	Explain the structure and characteristic of TRIAC.	03	CO-1	R
	(b)	Compare SCR and IGBT.	04	CO-1	N
	(c)	What are the on conditions for SCR? Explain the RC triggering circuit in detail.	07	CO-2	U
OR					
Q.4	(a)	Explain the effect of freewheeling diode.	03	CO-1	U
	(b)	Compare static and dynamic latch up in IGBT.	04	CO-1	
	(c)	With help of neat circuit diagram and associated waveform explain the operation of single phase bridge converter for resistive load.	07	CO-4	N
Q.5	(a)	What are the advantages of SMPS over normal power supply? List out the various applications of SMPS.	03	CO-5	N
	(b)	Explain the working of fly back converter SMPS.	04	CO-5	U
	(c)	With help of block diagram explain the operation of off line uninterrupted power supply. Write the detail specifications of off line UPS.	07	CO-7	A
OR					
Q.5	(a)	Define and explain power line disturbances.	03	CO-7	N
	(b)	Explain the design and application of power conditioner.	04	CO-7	A
	(c)	Explain the construction, working and applications of permanent magnet stepper motor drive.	07	CO-6	A

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-V EXAMINATION – SUMMER 2025****Subject Code:3151106****Date:15-05-2025****Subject Name:Power Electronics****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) Explain briefly the concept of power electronics.	03
	(b) Define and compare holding and latching currents of SCR.	04
	(c) What is commutation? With help of circuit and wave form explain self commutation by an LC circuit.	07
Q.2	(a) Compare simple rectifier and controlled rectifier.	03
	(b) With help of neat diagram and associated waveform, explain the operation of half wave RC triggering circuit.	04
	(c) A complementary commutation circuits operate from DC supply of 120 V and use $R_1 = R_2 = 10 \Omega$, commutating capacitor $C = 10 \mu\text{F}$. Calculate circuit turn off time and peak thyristor current.	07
	OR	
	(c) A single phase full converter is supplied from 230 V, 50 Hz supply. The load current is continuous and ripples free. If the average current is 150 A and source inductance is 0.1 mH determine the overlap angle at (i) $\alpha = 10^\circ$ (ii) $\alpha = 30^\circ$ (iii) $\alpha = 60^\circ$	07
Q.3	(a) Write the classification of DC Chopper.	03
	(b) With help of circuit diagram explain the working of class E chopper.	04
	(c) Explain the various voltage control methods of single phase inverter.	07
	OR	
Q.3	(a) Enumerate the merits and demerits of load commutated chopper.	03
	(b) With help of circuit diagram explain the working of Jones chopper.	04
	(c) With help of neat circuit diagram and waveforms, explain the operation of single phase voltage source inverter.	07
Q.4	(a) Explain the power integrated circuits.	03
	(b) Compare DIAC and TRIAC.	04
	(c) Which are the conditions to make SCR on? Explain the full wave RC triggering circuit in detail.	07
	OR	
Q.4	(a) Explain the effect of freewheeling diode.	03
	(b) What are advantages of IGBT? Explain the basic structure of IGBT.	04
	(c) With help of neat circuit diagram and associated waveform explain the operation of single phase full wave controlled rectifier with resistive and inductive load.	07
Q.5	(a) Explain the discontinuous mode of isolated fly back SMPS.	03
	(b) Explain MOS controlled thyristor.	04

- (c) With help of block diagram explain the operation of on line uninterrupted power supply. Write the detail specifications of on line UPS. **07**

OR

- Q.5** (a) What is meant by EMI and EMC? **03**
(b) Explain the capacity and efficiency of batteries used in UPS. **04**
(c) Explain the construction, working and applications of separately excited DC motor drive. **07**

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-V (NEW) EXAMINATION – SUMMER 2024****Subject Code: 3151106****Date: 18-05-2024****Subject Name: Power Electronics****Time: 02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) Explain the basic requirements for the successful firing of SCR.	03
	(b) Explain the structure and various triggering modes of operation of TRIAC.	04
	(c) The half wave controlled rectifier has purely resistive load of R and delay angle $\alpha = 60^\circ$ determine. (i) Rectification efficiency (ii) Form factor and (iii) Ripple factor.	07
Q.2	(a) Compare natural and forced commutations of SCR.	03
	(b) Explain the various Turn-On methods of SCR in brief.	04
	(c) Derive the average load voltage and load current equations of single phase half wave controlled rectifier with resistive and inductive load.	07
	OR	
	(c) A dc chopper operates on 300V dc and frequency of 200 Hz, feeds an R-L load. Determine the ON times of the chopper for output voltage of 150V.	07
Q.3	(a) Draw the schematic of step-up chopper and derive an expression for output voltage of chopper.	03
	(b) Compare the Time Ratio control and current limit control strategies of chopper.	04
	(c) With help of neat circuit diagram and waveforms, explain the operation of single phase half bridge voltage source inverter with resistive load.	07
	OR	
Q.3	(a) What are the applications of chopper? Explain the working of class A chopper.	03
	(b) Explain the multiphase chopper.	04
	(c) With help of neat circuit diagram and waveforms, explain the operation of single phase full bridge square wave inverter with resistive load.	07
Q.4	(a) Explain the dv/dt and di/dt ratings of SCR.	03
	(b) What is commutation? Explain class D forced commutation.	04
	(c) Design the basic structure of MCT and explain its turn on and turn off operations.	07
	OR	
Q.4	(a) Explain the internal control pulse width modulation control method of inverter.	03
	(b) Compare IGBT and Power MOSFET.	04
	(c) Design the structure of MOSFET and explain its operation and V-I characteristics.	07

- | | | | |
|------------|-----|---|-----------|
| Q.5 | (a) | Compare General Power supply and SMPS. | 03 |
| | (b) | Explain the working of fly back converter SMPS. | 04 |
| | (c) | With help of block diagram, explain the operation of on line UPS. List the important specifications of on line UPS. | 07 |
| OR | | | |
| Q.5 | (a) | What do you mean by EMI and EMC? | 03 |
| | (b) | Explain the working of induction motor. | 04 |
| | (c) | Write short note on permanent magnet stepper motor drive. | 07 |

GUJARAT TECHNOLOGICAL UNIVERSITY**BE – SEMESTER- V EXAMINATION-SUMMER 2023****Subject Code: 3151106****Date: 26/06/2023****Subject Name: Power Electronics****Time: 02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

- Q.1** (a) Explain the structure and symbol of SCR. **03**
(b) Draw and explain the class – B self-commutation of SCR using LC circuit. **04**
(c) Explain the working of half wave-controlled rectifier with resistive load. **07**
- Q.2** (a) Differentiate between one quadrant and two quadrant converter. **03**
(b) What is power MOSFET? Explain its output characteristics. **04**
(c) What is MOS controlled thyristor (MCT)? Explain turn on process of N-MCT. **07**
- OR**
- (c) Draw and explain the operation of fully controlled bridge circuit with RL load for single-phase controlled rectifier. **07**
- Q.3** (a) Explain the basic structure of IGBT. **03**
(b) Explain any one time ratio control (TRC) strategy for chopper operation. **04**
(c) What is DC chopper? Explain the principle of chopper operation. **07**
- OR**
- Q.3** (a) What is power integrated circuit (PIC)? **03**
(b) What is step-up chopper? Explain in brief. **04**
(c) Draw the circuit of Type B chopper and explain its operation with waveforms. **07**
- Q.4** (a) List the advantages and disadvantages of pulse width modulated (PWM) inverters. **03**
(b) A chopper circuit is operating on time ratio control (TRC) principal at a frequency of 2 kHz on a 220 V DC supply. If load voltage is 170 V, compute the conduction and blocking period of thyristor in each cycle. **04**
(c) What is inverter? Explain the operation of single-phase full bridge inverter. **07**
- OR**
- Q.4** (a) What are the drawbacks of square wave inverter? **03**
(b) Explain the single-phase, half-wave converter for controlling separately excited DC motor. **04**
(c) Explain the working of single phase current source inverter with resistive load. **07**
- Q.5** (a) Draw the characteristics of TRIAC. **03**
(b) Explain the block diagram of online UPS system. **04**
(c) Explain the operation of flyback converter (SMPS) with circuit diagram and waveform. **07**
- OR**
- Q.5** (a) Explain the chopper circuit used to drive DC series motor. **03**
(b) How to calculate capacity and efficiency of UPS battery? **04**
(c) What is resonant converter? Explain the working of series resonant inverter with unidirectional switch. **07**

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-V(NEW) EXAMINATION – SUMMER 2022****Subject Code:3151106****Date:04/06/2022****Subject Name:Power Electronics****Time:02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) Give classification of thyristors family.	03
	(b) Explain advantages of IGBT.	04
	(c) Explain the construction, operation and characteristics of SCR	07
Q.2	(a) Give the classification of inverters.	03
	(b) Explain single phase AC chopper with necessary diagram.	04
	(c) Draw and explain Three Phase Half wave controlled rectifier with required waveforms and equations.	07
	OR	
	(c) Draw and explain the circuit of ac phase control using DIAC and TRIAC.	07
Q.3	(a) Draw and explain Phase Locked Loop Control of DC Drives.	03
	(b) Differentiate between online and offline UPS systems.	04
	(c) What is SMPS? Give the classification of SMPS. Also List out advantages and disadvantages of SMPS.	07
	OR	
Q.3	(a) What is Commutation? Explain briefly the classification of commutation techniques.	03
	(b) Gives comparison between DC and AC Drives.	04
	(c) Explain the principal of Dielectric Heating. Also gives application of Dielectric Heating.	07
Q.4	(a) What is SMPS? Give the classification of SMPS.	03
	(b) A 200 A SCR is to be connected in parallel with 300 A SCR. The on state voltage drops of the SCRs are 2.1 V and 1.75 V respectively. Calculate the series resistance that should be connected with each SCR if the two SCRs have to share the total current 500 A in proportion to their ratings.	04
	(c) Draw and explain the V-I characteristics of UJT.	07
	OR	
Q.4	(a) Why a freewheeling diode is connected in inductive loaded circuit?	03
	(b) What is Pulse Width Modulation? How can it be used to control the output of chopper?	04
	(c) Explain single phase half wave controlled rectifier with RL load with proper waveforms.	07
Q.5	(a) Explain Step down Chopper.	03
	(b) Explain regenerative and dynamic braking of dc motor.	04
	(c) Explain Speed control of Motor	07

OR

- | | | | |
|------------|------------|--|-----------|
| Q.5 | (a) | Write down the basic principle of induction heating. | 03 |
| | (b) | Explain UJT as relaxation oscillator. | 04 |
| | (c) | Write a short note on online UPS system. | 07 |
