

# GUJARAT TECHNOLOGICAL UNIVERSITY

BE- SEMESTER-IV (NEW) EXAMINATION – WINTER 2024

**Subject Code:3140915**

**Date:03-12-2024**

**Subject Name:Power Electronics**

**Time:02:30 PM TO 05:00 PM**

**Total Marks:70**

**Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
<b>Q.1</b>	(a) Explain IGBT with its physical construction diagram and characteristics.	<b>03</b>
	(b) Draw the SCR static V-I characteristics and explain its behavior in forward conduction, forward blocking and reverse blocking modes.	<b>04</b>
	(c) Describe the working of UJT Relaxation Oscillator circuit. Discuss its Design criterion.	<b>07</b>
<b>Q.2</b>	(a) Describe briefly three adverse effects of electromagnetic interference. Discuss briefly one remedial step to reduce EMI	<b>03</b>
	(b) Define and explain the need of snubber circuit. Draw such circuit for SCR and give guidelines for selecting its components.	<b>04</b>
	(c) Discuss discontinuous mode of operation in buck boost converter with waveforms.	<b>07</b>
	<b>OR</b>	
	(c) Draw the circuit of a single phase fully controlled converter with R-L load. Derive necessary equations and sketch output waveforms.	<b>07</b>
<b>Q.3</b>	(a) What do you mean by freewheeling action? Explain How diode can provide freewheeling action?	<b>03</b>
	(b) Give four points of difference between on-off control and phase angle control.	<b>04</b>
	(c) Discuss the various techniques of improving power factor in phase controlled converters. Explain PWM techniques in detail with necessary waveforms.	<b>07</b>
	<b>OR</b>	
<b>Q.3</b>	(a) Distinguish between full controlled bridge converter and half controlled bridge converter.	<b>03</b>
	(b) Explain pulse transformer and opto-coupler	<b>04</b>
	(c) Discuss operation of Flyback converter. Draw its circuit diagram and waveforms.	<b>07</b>
<b>Q.4</b>	(a) Write advantages and disadvantages of PWM technique to generate gate Pulse.	<b>03</b>
	(b) Compare 120° and 180° modes of conduction on the basis of 1) conduction of number of device 2) conduction of each device 3) output phase voltage (draw waveform for each case)	<b>04</b>
	(c) Explain working of 3- $\phi$ A.C. voltage controller with star connected R load using circuit diagram and waveforms of input phase voltages, triggering waveforms and output R phase voltage for $\alpha=60^\circ$ .	<b>07</b>

**OR**

- Q.4** (a) Derive AC voltage controller average output voltage equation. **03**  
(b) Explain the turn-on and turn-off characteristics of an SCR. **04**  
(c) Describe the working of a single phase full converter in the rectifier mode with RLE load. Derive an expression for the average output voltage in terms of source voltage and firing angle. **07**

- Q.5** (a) Compare CSI and VSI. **03**  
(b) Explain Concept of switching voltage regulators and advantages **04**  
(c) Describe the working of series inverter with diagram and waveforms. **07**

**OR**

- Q.5** (a) List any three industrial applications of ac voltage controller. Enumerate its merits and demerits. **03**  
(b) Explain working principle of Matrix converter. **04**  
(c) Describe the basic principle of operation of a single phase to single phase bridge type cycloconverter for continuous conduction **07**

\*\*\*\*\*