

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-IV (NEW) EXAMINATION – WINTER 2023****Subject Code:3140915****Date:01-02-2024****Subject Name: Power Electronics****Time: 10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
<b>Q.1</b>	(a) What is an IGBT? Sketch the equivalent circuit and transfer characteristics of an IGBT.	<b>03</b>
	(b) Draw the SCR static V-I characteristics and explain its behavior in forward conduction, forward blocking and reverse blocking modes.	<b>04</b>
	(c) Draw and explain the resistance triggering and R-C triggering circuits.	<b>07</b>
<b>Q.2</b>	(a) Draw only switching characteristics of SCR during turn-on and turn-off process.	<b>03</b>
	(b) State the advantages & disadvantages of current source inverter & voltage source inverter.	<b>04</b>
	(c) Draw gate voltage and phase voltage waveform and explain 3 phase inverter operation for 120° conduction mode	<b>07</b>
	<b>OR</b>	
	(c) Explain Space Vector Pulse Width Modulation Technique in brief.	<b>07</b>
<b>Q.3</b>	(a) What is pulse width modulation? List the various PWM techniques.	<b>03</b>
	(b) Classify of different techniques for voltage control of inverter. Explain anyone.	<b>04</b>
	(c) Draw the circuit diagram of three-phase full converter connected to RL load with continuous conduction. Draw the waveforms of output voltage, output current for firing angle equal to 45°.	<b>07</b>
	<b>OR</b>	
<b>Q.3</b>	(a) What is the purpose of connecting diodes in antiparallel with thyristors in inverter circuits?	<b>03</b>
	(b) Derive output voltage equation for single phase half wave rectifier.	<b>04</b>
	(c) Explain working of 1- $\phi$ semi converter with the help of voltage and current waveform under resistive load.	<b>07</b>
<b>Q.4</b>	(a) Describe the working of freewheeling diode in phase-controlled rectifier.	<b>03</b>
	(b) Write advantages disadvantages and application of single-phase full wave AC voltage controller.	<b>04</b>
	(c) Explain multi-quadrant operation of DC-DC converter.	<b>07</b>
	<b>OR</b>	
<b>Q.4</b>	(a) Draw only the possible configurations of a single-phase voltage controller.	<b>03</b>
	(b) Describe application of TRIAC as Single-phase Fan regulator with circuit diagram and waveform.	<b>04</b>
	(c) Explain AC Voltage controllers with (i) on-off control method and (ii) integral cycle control method.	<b>07</b>

- Q.5** (a) What is a cycloconverter? Enumerate some of its industrial applications. **03**
- (b) Write a short note on matrix converter. **04**
- (c) Explain the operation of three-phase to single phase cycloconverters. **07**
- OR**
- Q.5** (a) Draw the basic circuit diagram of 3-phase to 3-phase cycloconverter. **03**
- (b) Explain the snubber circuit and its design. **04**
- (c) Explain working of 1- $\phi$  to 1- $\phi$  cycloconverter with input frequency 50Hz and output frequency 10Hz. **07**

\*\*\*\*\*