

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-IV EXAMINATION – SUMMER 2025****Subject Code: 3140915****Date: 27-05-2025****Subject Name: Power Electronics****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) Draw and explain static characteristics of SCR.	03
	(b) Describe bipolar PWM techniques in detail.	04
	(c) Discuss three-phase semi converter connected to RL load in continuous conduction mode with circuit diagram and waveforms of output voltage/current for firing angle of 30° .	07
Q.2	(a) Discuss the need of freewheeling diode in phase-controlled rectifier.	03
	(b) Discuss the requirement of Snubber circuit for reliable operation of an SCR.	04
	(c) Derive output voltage equation for single phase full wave controlled rectifier with R load. Assume α is firing angle.	07
	OR	
	(c) Explain working of single phase to single phase step down cycloconverter with circuit diagram and waveforms for continuous and discontinuous load current.	07
Q.3	(a) SCR is not suitable for dc to ac converter for low power applications. Justify.	03
	(b) Describe the SVPWM control technique in brief.	04
	(c) Explain the working of three phase 120° mode voltage source inverter. Also draw the necessary waveforms and circuit diagrams.	07
	OR	
Q.3	(a) Classify different techniques for voltage control of inverter. Discuss any one in brief.	03
	(b) Describe the SPWM control technique in detail.	04
	(c) Explain the working of three phase 180° mode voltage source inverter. Also draw the necessary waveforms and circuit diagrams.	07
Q.4	(a) Discuss the operation of DC/DC Flyback converter.	03
	(b) Discuss the effect of high switching frequency on harmonics spectrum in single phase full bridge voltage source inverter.	04
	(c) Describe the dual converter operation with circulating current mode in case of single phase input supply. Also draw the voltage and current waveforms.	07
	OR	
Q.4	(a) Discuss single phase full wave AC voltage controller with circuit diagram and necessary waveforms.	03
	(b) Discuss matrix converter with necessary circuit diagram.	04
	(c) Explain integral cycle control of AC voltage controllers with necessary equations and waveforms.	07
Q.5	(a) Explain the basic structure of IGBT with schematic diagram.	03
	(b) Discuss two transistor model of SCR.	04
	(c) Explain multi-quadrant operation of DC-DC converter.	07

OR

- | | | | |
|------------|-----|--|-----------|
| Q.5 | (a) | Explain the basic structure of MOSFET with schematic diagram. | 03 |
| | (b) | List out the various SCR turn on methods. Discuss any one in detail. | 04 |
| | (c) | Explain the working of buck converter with necessary circuit diagrams and waveforms. | 07 |
