

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**BE - SEMESTER– IV(NEW) EXAMINATION – SUMMER 2023**

**Subject Code:3140915****Date:27-07-2023****Subject Name:Power Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
<b>Q.1</b>	(a) Draw the symbol of Transistor, MOSFET, IGBT, DIAC, TRIAC, GTO.	<b>03</b>
	(b) Explain construction, VI characteristics of SCR.	<b>04</b>
	(c) Draw and explain any three triggering methods for Thyristors.	<b>07</b>
<b>Q.2</b>	(a) Give classification and types of DC-DC converter topologies.	<b>03</b>
	(b) Define Holding current, latching current for SCR.	<b>04</b>
	(c) A step up chopper has input voltage of 220 V and output voltage of 660V. if the turn off time is 100 microsecond. Compute turn on time.	<b>07</b>
	<b>OR</b>	
	(c) A boost converter has an input voltage of 6 V. The average output voltage is 15 V. The switching frequency is 20 kHz. Find the duty cycle.	<b>07</b>
<b>Q.3</b>	(a) Explain Buck converter with circuit diagram and waveform.	<b>03</b>
	(b) Explain working of Flyback converter with circuit and waveform.	<b>04</b>
	(c) Describe Full-bridge single-phase voltage source inverter with circuit diagram and waveform.	<b>07</b>
	<b>OR</b>	
<b>Q.3</b>	(a) Write advantages of SVPWM technique over SPWM techniques.	<b>03</b>
	(b) State the term Harmonic Factor, THD, LOH, DF with respect to converter.	<b>04</b>
	(c) Explain three phase inverter with 120 <sup>0</sup> mode of conduction with circuit and waveform.	<b>07</b>
<b>Q.4</b>	(a) Write significance of freewheeling diode in control rectifier.	<b>03</b>
	(b) Define the term Harmonics, its causes and effects.	<b>04</b>
	(c) Explain single phase full wave controlled rectifier with RL load with circuit and waveform.	<b>07</b>
	<b>OR</b>	
<b>Q.4</b>	(a) Explain UJT relaxation oscillator circuit.	<b>03</b>
	(b) A single phase full wave AC-DC converter is supplied by 230 V 50 Hz supply. The load consists of R=10 ohm. A firing angle delay of 30 <sup>0</sup> . Determine the average output voltage, Average output current.	<b>04</b>
	(c) Describe three phase full wave controlled AC –DC converter with R load with circuit and waveform.	<b>07</b>
<b>Q.5</b>	(a) Write advantages disadvantages and application of single phase full wave AC voltage controller.	<b>03</b>
	(b) Describe application of TRIAC as Single-phase Fan regulator with circuit diagram and waveform.	<b>04</b>
	(c) Explain single phase Cycloconverter with circuit and waveform.	<b>07</b>

**OR**

- |            |     |   |           |
|------------|-----|---|-----------|
| <b>Q.5</b> | (a) | Explain two transistor model of Thyristor.              | <b>03</b> |
|            | (b) | Explain working of Dual converter with circuit diagram. | <b>04</b> |
|            | (c) | Explain Matrix converter with circuit and waveform.     | <b>07</b> |

\*\*\*\*\*