

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III EXAMINATION – SUMMER 2025****Subject Code:3131102****Date:31-05-2025****Subject Name:Digital System Design****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) Convert the decimal Number 250.5 to base 4 and base 8.	03
	(b) State and prove DeMorgan's Theorem.	04
	(c) Minimize the following function in SOP and POS minimal form using K-Maps: $F(A, B, C, D) = \sum m(1, 2, 6, 7, 8, 13, 14, 15) + d(3, 5, 12)$	07
Q.2	(a) Convert $F(A,B,C) = BC+A$ into standard minterm form.	03
	(b) Implement Ex -NOR and Ex-OR using NAND and NOR only.	04
	(c) Implement the full adder & full subtractor using Multiplexer.	07
	OR	
	(c) Design and implement binary to Excess-3 code converter.	07
Q.3	(a) Obtain the truth table of the function: $F = xy+yz+zx$.	03
	(b) Obtain JK flip-flop from SR flip-flop.	04
	(c) Draw the circuit diagrams and truth table of SR, D, T and JK flip flops.	07
	OR	
Q.3	(a) What is "Lock out" condition in counter? How to avoid it?	03
	(b) Implement 4x16 decoder using two 3x8 decoder.	04
	(c) Explain Master Slave JK flip-flop with truth table and circuit diagram.	07
Q.4	(a) Compare sequential and combinational circuits.	03
	(b) Define the following characteristics of IC: (i) Propagation Delay (ii) Figure of Merit (iii) Fan out (vi) Noise Margin	04
	(c) Compare ROM, PLA and PAL.	07
	OR	
Q.4	(a) Compare Latch and a Flip flop.	03
	(b) Give classification of logic families and compare CMOS and TTL.	04
	(c) Explain Moore machine.	07
Q.5	(a) List the steps in VLSI Design flow.	03
	(b) Design Modulo-8 counter using T flip flop.	04
	(c) With neat sketch design 4-bit bidirectional shift register.	07
	OR	
Q.5	(a) Define State Table and State Diagram.	03
	(b) Design mod-6 asynchronous counter using T flip-flop.	04
	(c) Design 4-bit ripple counter using negative edge triggered JK flip flop.	07
