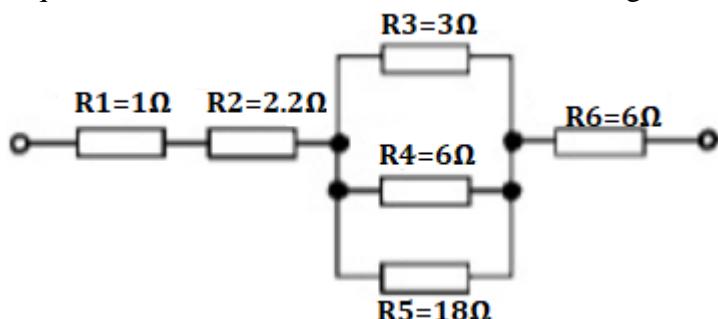


GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III EXAMINATION – SUMMER 2025****Subject Code:3131103****Date:06-06-2025****Subject Name:Network Theory****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

Q.1 (a) Do as directed:**14**

- 1) What is mutual-inductance (M)?
- 2) Find the equivalent resistance for the circuit shown in Figure



- 3) What is the difference between the unilateral and bilateral network?
- 4) Justify: The inductors act as an open circuit at time $t=0+$.
- 5) State Kirchhoff's current law (KCL).
- 6) What is the condition for reciprocal network for Y-parameters?
- 7) State Kirchhoff's voltage law (KVL).
- 8) Define "Tree" of a connected graph.
- 9) What is co-tree and links?
- 10) What is the Laplace transform of a unit step signal?
- 11) What is fundamental cut set matrix?
- 12) Write the equation for hybrid parameters of a two-port network.
- 13) For a frequency of 200 Hz, the time period will be_____.
- 14) Ohm is unit of all of the following except_____.
 - inductive reactance
 - capacitive reactance
 - resistance
 - capacitance

Q.2 (a) What is time constant? What is its significance?**03****(b) Explain dot convention for coupled coils with suitable example.****04****(c) Find current in 20-ohm resistance in the circuit shown in **figure:1** using superposition theorem.****07****OR****(c) For the network shown in **figure:2** the switch k is closed at $t=0$, also it reaches a steady state with the switch k open. Find the current $i(t)$ for all time.****07****Q.3 (a) State and explain initial value theorem of Laplace transform.****03****(b) Explain characteristic of an ideal voltage source.****04****(c) Calculate the node voltages for all the nodes V1, V2 and V3 shown in **figure:3** using nodal analysis.****07**

OR

Q.3 (a) Derive the condition of maximum power transfer for the variable resistance as a load circuit. **03**
 (b) In the Network shown in **figure:4** steady state is reached with switch k is open. At $t=0$, the switch is closed. For the element values given determine $V_a(0-)$ and $V_a(0+)$. **04**
 (c) Find the Z parameters for the network shown in **figure:5**. **07**

Q.4 (a) Define fundamental loop and cut-set. **03**
 (b) Find the current in 4Ω resistor for the circuit shown in **figure:6** using Thevenin's theorem and also find maximum power dissipation by the 4Ω . **04**
 (c) For the circuit of **figure:7**, using mesh analysis find the mesh currents I_1 , I_2 and I_3 . Also find voltage v across a dependent source. **07**

OR

Q.4 (a) Find the inverse Laplace Transform of: **03**


$$F(s) = 1 + \frac{4}{s+3} - \frac{5s}{s^2 + 25}$$

 (b) Find the Norton's equivalent with respect to terminals $a - b$ in the circuit shown in **figure: 8**. **04**
 (c) In the network of the **figure:9**, the switch K is in position a for a long time. At $t = 0$, the switch is moved from a to b. Find $v_2(t)$ with assumption that the initial current in the 2 H inductor is zero. **07**

Q.5 (a) Find Laplace transform of $f(t) = t^2 u(t)$. **03**
 (b) Explain the terms: **04**
 1) Bilateral
 2) Passive
 3) Oriented graph
 4) Time invariant
 (c) For the network shown in **figure:10** draw the oriented graph. Also obtain incidence matrix (A), fundamental tie-set matrix (Bf) and fundamental cut-set matrix (Qf). **07**

OR

Q.5 (a) Obtain Laplace transform of (1) Unit Impulse function (2) Unit Ramp function (3) $\sin \omega t$. **03**
 (b) Determine h-parameters in terms of z-parameters. **04**
 (c) In the network of **figure:11**, determine i_x . **07**

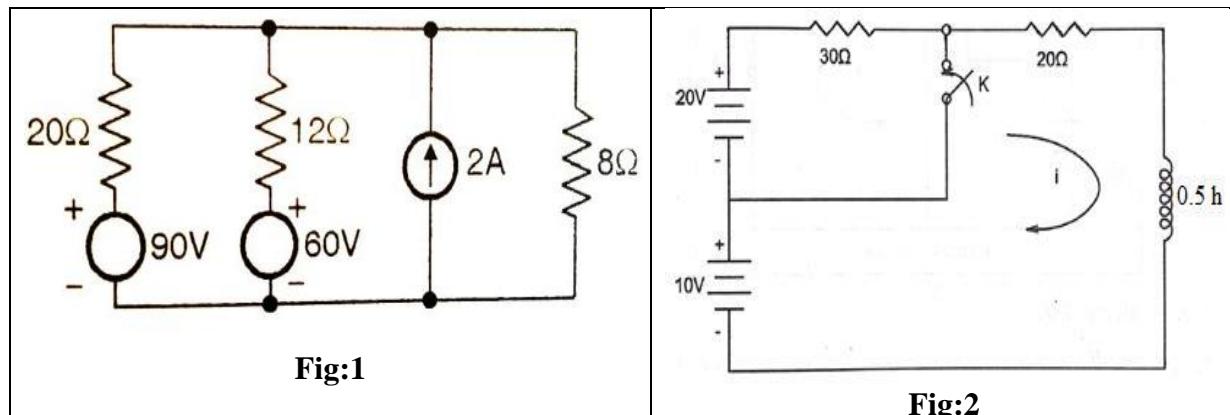

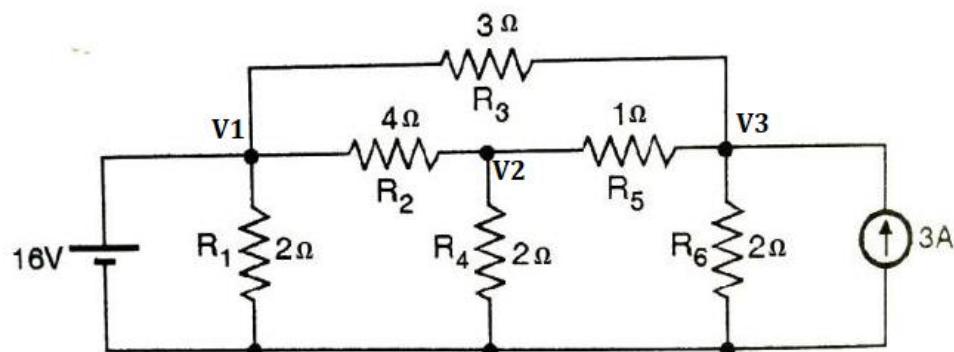


Fig:3

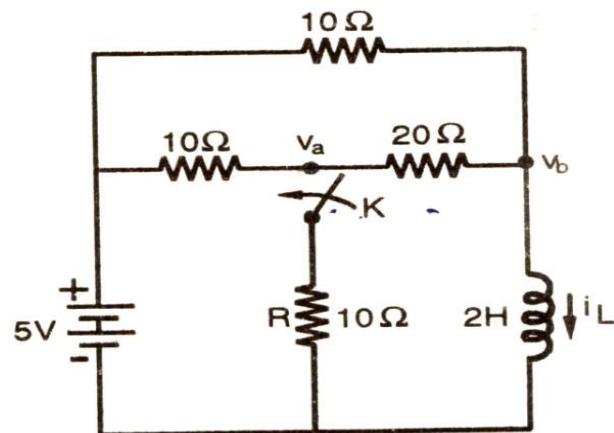


Fig:4

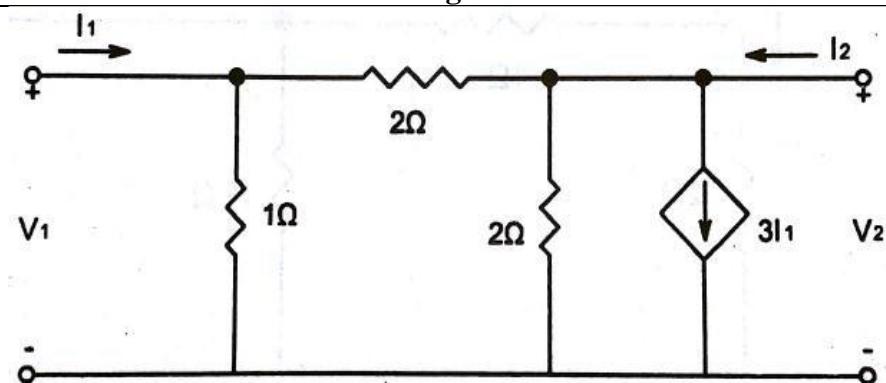


Fig:5

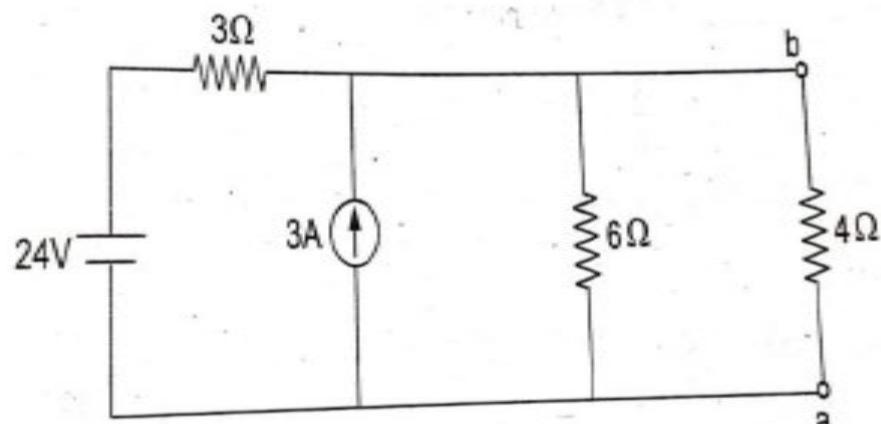


Fig:6

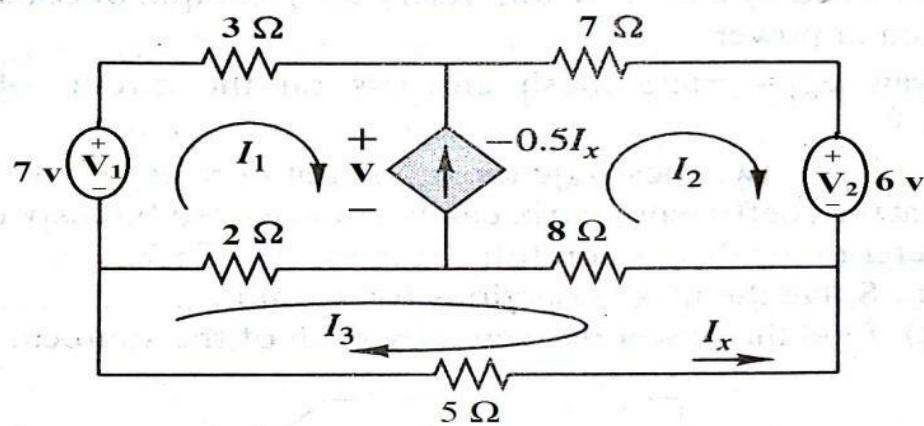


Fig:7

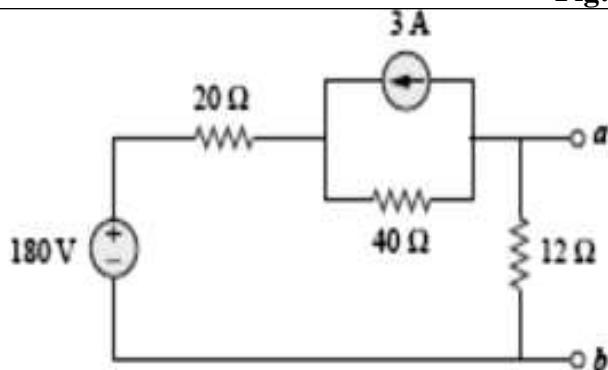


Fig:8

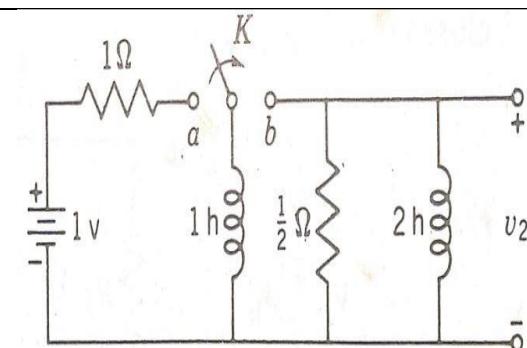


Fig:9

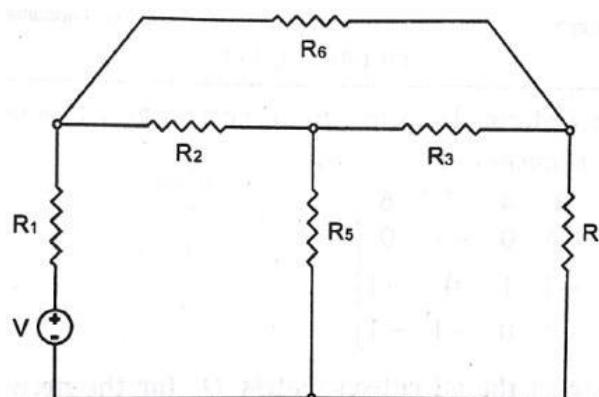


Fig:10

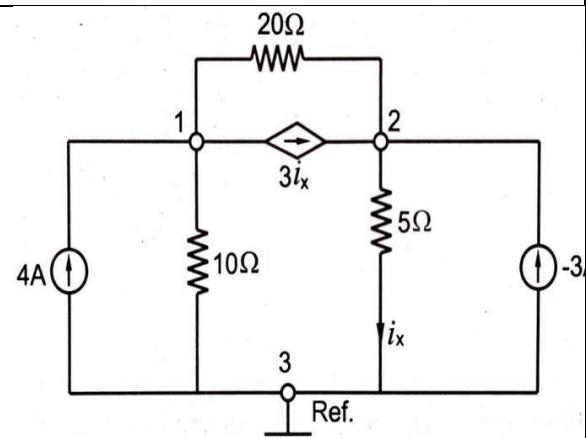


Fig:11
