

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-III (NEW) EXAMINATION – SUMMER 2024****Subject Code:3131103****Date:06-07-2024****Subject Name: Network Theory****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**


1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		<b>Marks</b>
<b>Q-1</b>	(a) Discuss the following.	<b>03</b>
	(i) Linear and Nonlinear elements	
	(ii) Bilateral and Unilateral elements	
	(iii) Active and Passive elements	
	(b) Find the total inductance of the three series connected coupled coils as shown in Figure 1.	<b>04</b>
	(c) Name the three parameters of electric Network. Discuss the characteristics of each one of them. Write equation for voltage-current and energy relation.	<b>07</b>
<b>Q-2</b>	(a) Explain Ideal and Practical energy sources.	<b>03</b>
	(b) Use nodal analysis to find the voltages across the $5\Omega$ resistor in the network as shown in figure 2.	<b>04</b>
	(c) Determine the mesh currents $i_1$ , $i_2$ and $i_3$ in a network of figure 3.	<b>07</b>
	<b>OR</b>	
	(c) Determine the values of unknown node-to- reference voltages in the circuit as shown in figure 4.	<b>07</b>
<b>Q-3</b>	(a) Explain Why?	<b>03</b>
	(i) The current in an inductor cannot change instantaneously.	
	(ii) The voltage across a capacitor cannot change instantaneously.	
	(b) A series RLC circuit with zero inductor current and zero capacitor voltage is excited by 50V dc source. Find $i(0^+)$ and $\frac{di}{dt} 0^+$ for the circuit as shown in figure 5.	<b>04</b>
	(c) Determine the numerical value of $i_2$ using source transformation method for the circuit given in figure 6.	<b>07</b>
	<b>OR</b>	
<b>Q-3</b>	(a) How the following elements will behave at $t = 0$ and $t = \infty$ . Draw the equivalent network.	<b>03</b>
	(i)Resistor (ii)Inductor (iii) Capacitor	
	(b) In the figure 7, the switch K is closed at $t=0$ , $v=100V$ , $R=1K\Omega$ , $C=0.5 \mu F$ , $L=1H$ . Find (i) $\frac{di}{dt}$ and (ii) $\frac{d^2i}{dt^2}$ at $t=0$ .	<b>04</b>
	(c) For network shown in figure 8, All sources are time invariant. Determine the branch current in $2\Omega$ resistor using source transformation method.	<b>07</b>
<b>Q-4</b>	(a) State and explain: Thevenin's theorem in brief by giving suitable example.	<b>03</b>
	(b) What is time constant? Explain time constant in terms of RL circuit.	<b>04</b>
	(c) Determine the current in $R=1\Omega$ resistor of the network shown in Figure 9, using Norton's theorem.	<b>07</b>

**OR**

- Q-4** (a) State and explain: superposition theorem in brief by giving suitable example. **03**  
 (b) State and explain initial value theorem. **04**  
 (c) For the circuit shown in figure 10, determine the value of  $R_L$  for maximum power transfer. What will be the value of power transfer under this condition? **07**
- Q-5** (a) Determine h-parameters in terms of z-parameters. **03**  
 (b) Define the terms: (i) Planner graph (ii) Non- Planner graph (iii) Loop **04**  
 (c) Find z-parameters of the circuit shown in Figure 11. **07**
- OR**
- Q-5** (a) Determine ABCD -parameters in terms of Y-parameters. **03**  
 (b) Briefly describe the network synthesis and its application. **04**  
 (c) Determine Y-parameters for the network shown in Figure 12. Calculate Z-parameters from Y-parameters. **07**

\*\*\*\*\*

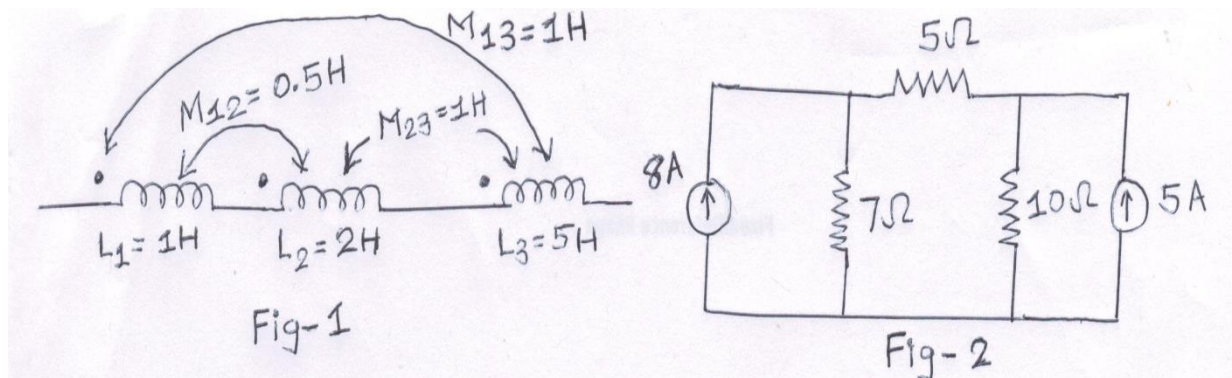

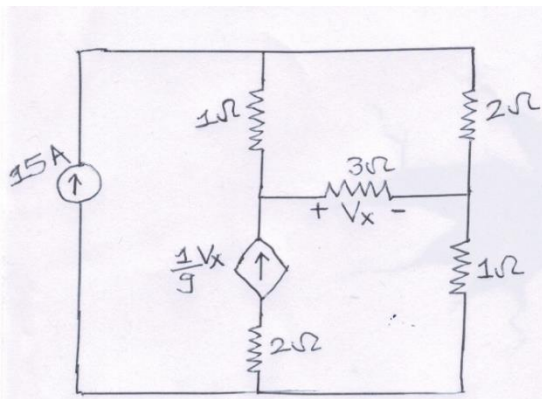


Fig-3

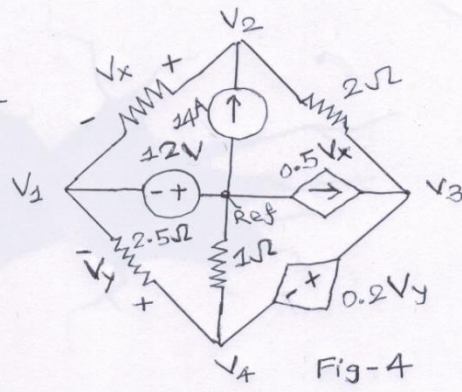


Fig-4

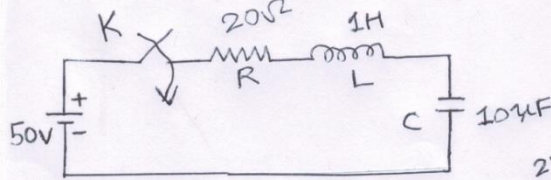


Fig-5

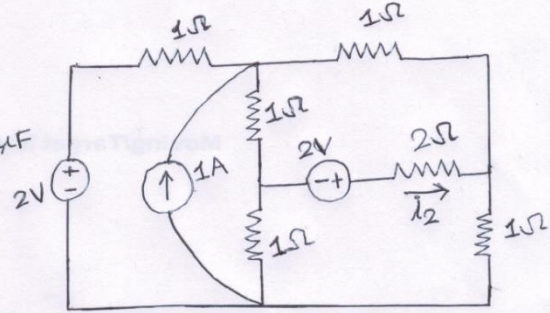


Fig-6

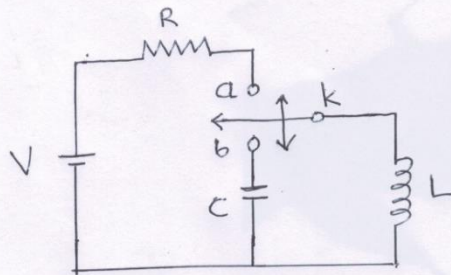


Fig-7

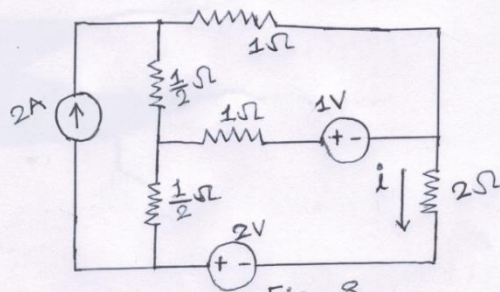


Fig-8

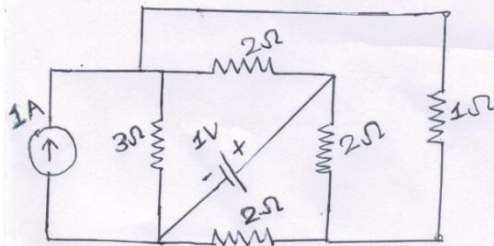


Fig-9

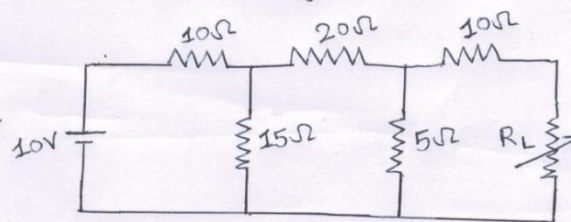


Fig-10

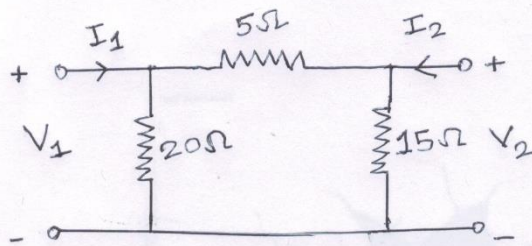


Fig-11

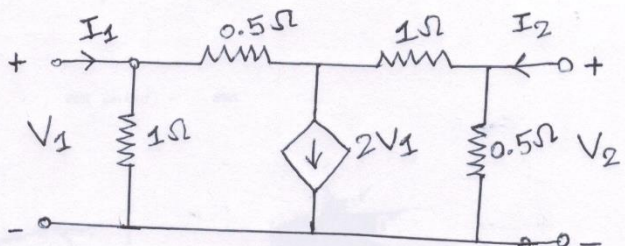


Fig-12

\*\*\*\*\*