

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-VI EXAMINATION – SUMMER 2025

Subject Code: 3160919

Date: 30-05-2025

Subject Name: Electric Drives

Time: 10:30 AM TO 01:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

- Q.1** (a) Derive torque equation of DC motor. **03**
(b) Explain the principal of motoring and regenerative braking mode of DC motor. **04**
(c) Discuss the block diagram of close loop DC drive with current limit control. **07**

- Q.2** (a) Draw and explain different types of load torque speed characteristics. **03**
(b) Draw torque speed characteristic of DC shunt motor and explain how change in armature voltage will change in speed of motor **04**
(c) Derive the output voltage equation of step-down chopper fed DC drive and explain the operation with necessary diagram and waveforms. **07**

OR

- (c) Discuss the operation of Class E chopper fed DC drive with necessary diagram and waveforms. **07**

- Q.3** (a) Explain current controller specification for chopper-based speed control of separately excited DC motor. **03**
(b) Based on the block diagram of close loop control of DC drives, derive the transfer function. **04**
(c) Explain the feature of PWM inverter fed Induction motor drive. **07**

OR

- Q.3** (a) Draw only block diagram of close loop armature control with field flux weakening. **03**
(b) Give of comparison between converter fed dc drives and chopper fed dc drives. **04**
(c) Explain the types of output voltage control methods with the help of chopper. **07**

- Q.4** (a) How torque speed characteristic of induction motor will be modified with change in rotor resistance. **03**
(b) What is slip speed control of induction motor drives? **04**
(c) Derive the torque equation from equivalent circuit of three phase induction motor. **07**

OR

- Q.4** (a) What is above base speed and below base speed operation of the motor? **03**
(b) What is slip power? What are the different methods used for control the slip power? **04**
(c) Discuss principle of constant flux operation of induction motor in detail with necessary equation and diagram. **07**

- Q.5** (a) Compare all the PWM technique for voltage source inverter. **03**
(b) Draw and discuss motor characteristics for constant torque and flux weakening region. **04**
(c) Draw the neat circuit diagram and explain the speed control of 3 phase induction motor by static scherbius system. **07**

OR

- Q.5** **(a)** Explain three regions of torque speed characteristic of induction motor based on slip. **03**
- (b)** How torque speed characteristic of induction motor will be modified with (i) change in applied voltage (ii) change in applied frequency **04**
- (c)** Discuss the operation of 3 phase AC voltage controller driven induction motor drive with necessary diagram and waveforms. **07**
