

GUJARAT TECHNOLOGICAL UNIVERSITY**BE- SEMESTER-VI (NEW) EXAMINATION – WINTER 2024****Subject Code:3160919****Date:05-12-2024****Subject Name:Electric Drives****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) Define electric drives and state their applications in industrial systems.	03
	(b) Discuss at least four differences between flux weakening and armature voltage control in DC motors.	04
	(c) A separately excited DC motor operates from a 220 V supply and runs at a speed of 1000 RPM while drawing 15 A. The armature resistance is 1 Ω . Calculate:	07
	(i) Back EMF of the motor at 1000 RPM. (ii) The speed if the armature current is 20 A	
Q.2	(a) Explain how smooth starting of a DC motor is achieved using a chopper.	03
	(b) By taking a suitable example discuss how the duty cycle of a chopper affects the speed of a DC motor.	04
	(c) A separately excited DC motor is fed from a half-controlled single-phase rectifier connected to a 230 V, 50 Hz AC supply. The motor has an armature resistance of 0.3 Ω and operates at 1200 RPM while drawing an armature current of 50 A. The firing angle of the rectifier is set to $\alpha=60^\circ$	07
	(i) Calculate the average DC output voltage of the rectifier. (ii) If the motor speed is reduced to 800 RPM while the armature current remains the same, calculate the new firing angle required to maintain the same armature current.	
OR		
	(c) A 220 V, 875 RPM, 150 A separately excited DC motor has an armature resistance of 0.05 Ω . The motor is fed from a single-phase fully controlled rectifier with an AC source of 230 V, 50 Hz. Calculate the firing angle required for the motor to produce a torque of 120 Nm at 750 RPM.	07
Q.3	(a) Draw the torque-speed characteristics of an induction motor when operated under varying terminal voltage control.	03
	(b) Explain the significance of slip regulation in induction motor control.	04
	(c) A separately excited DC motor operates in regenerative braking mode. The motor is rated for 220 V and 1500 RPM, with an armature resistance of 0.5 Ω . If the motor is running at 1000 RPM and delivering a current of 30 A during braking, calculate the back EMF and braking torque. (Assume back emf at rated condition to be approximately equal to supply voltage.)	07
OR		
Q.3	(a) Compare constant flux operation with flux weakening operation in induction motors.	03
	(b) Discuss the V/f control technique for an induction motor, and mention its advantages.	04
	(c) Explain with necessary block diagram the closed loop control of dc drive capable of controlling the motor in both above and below base speed regions.	07

- Q.4** (a) What are the different methods for speed control of an induction motor? Explain one in brief. **03**
- (b) Draw the torque-speed characteristics of an induction motor operated in above and below base speed regions through a v/f control drive. **04**
- (c) A 415 V, 50 Hz, 6-pole, three-phase induction motor has the following parameters: **07**
- Rotor resistance referred to the stator: $R_r=0.5 \Omega$
 - Rotor reactance referred to the stator: $X_r=2.5 \Omega$
 - Stator reactance: $X_s=1.5 \Omega$
 - Full-load slip: $s=0.05$
- The motor operates under full-load conditions, and the stator resistance is negligible.
- (i) Calculate the rotor current at full load.
- (ii) Determine the developed torque if the rotor current is found to be 35 A.
- OR**
- Q.4** (a) Draw the equivalent circuit of a three-phase induction motor and explain the function of each component. **03**
- (b) Explain the role of power electronics in the speed control of induction motors. **04**
- (c) A 440 V, 50 Hz, 6-pole, slip ring induction motor has a rotor resistance of $R_r=0.3 \Omega$, and an external rotor resistance of $R_{ext}=2 \Omega$. The motor runs at a speed of 960 RPM under full-load conditions with an external rotor resistance connected. The total rotor current is 50 A, and the rotor slip at full load is 0.04. **07**
- (i) Calculate the power dissipated in the external rotor resistance.
- (ii) Determine the torque produced by the motor at full load.
- Q.5** (a) Compare 120° conduction Mode and 180° conduction mode of inverter for induction motor drive. **03**
- (b) Discuss the role of rotor resistance in slip-ring induction motor drives and its impact on motor performance. **04**
- (c) Explain the space vector PWM technique for controlling voltage source inverters. **07**
- OR**
- Q.5** (a) What is slip power recovery? Explain its significance in slip ring induction motors. **03**
- (b) Draw and explain the speed-torque characteristics of a three-phase induction motor under different rotor resistances. **04**
- (c) Explain closed-loop V/f control of an induction motor and its significance in maintaining constant torque. **07**
