

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VI (NEW) EXAMINATION – SUMMER 2022****Subject Code:3160919****Date:10/06/2022****Subject Name:Electric Drives****Time:10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

MARKS

- | | | |
|------------|--|-----------|
| Q.1 | (a) Draw speed torque characteristic of DC separately excited, shunt and series motor with proper labeling. | 03 |
| | (b) Enlist methods for speed control of DC motor. Explain any one in brief. | 04 |
| | (c) Describe four quadrant operation of a dc motor. | 07 |
| Q.2 | (a) Give of comparison between converter fed dc drives and chopper fed dc drives. | 03 |
| | (b) Explain dynamic model of DC motor drive. | 04 |
| | (c) Explain chopper controlled DC shunt motor drive operation for motoring mode and regenerative mode. | 07 |
| OR | | |
| | (c) A dc chopper is used for regenerative braking of a separately excited dc motor. The dc supply voltage is 400 V. The motor has $r_a=0.2 \Omega$, $k_m=1.2\text{V-s/rad}$. The average armature current during regenerative braking is kept constant at 300 A with negligible ripple. For a duty cycle of 60% for a chopper, determine: (a) power returned to the dc supply (b) equivalent load resistance of motor acting as a generator (c) minimum and maximum permissible breaking speeds and (d) speed during regenerative braking. | 07 |
| Q.3 | (a) Draw the circuit and waveform of 1- ϕ dual converter drive for the speed control of separately excited dc motor. | 03 |
| | (b) Explain the closed loop speed control technique for DC motor. | 04 |
| | (c) Discuss chopper controlled Separately excited DC motor drive operation for motoring mode. | 07 |
| OR | | |
| Q.3 | (a) Define the principle of vector control. | 03 |
| | (b) Compare DC Drive with AC Drive. | 04 |
| | (c) Explain closed loop speed control of induction motor using slip control scheme. | 07 |
| Q.4 | (a) Discuss the points to be considered while selecting carrier frequency for inverter. | 03 |
| | (b) Compare VSI with CSI fed induction motor drives. | 04 |
| | (c) Draw and explain block diagram of CSI variable frequency drive with current control. | 07 |

OR

- Q.4** (a) List advantages of V/f control over scalar control. **03**
(b) Discuss effect of various harmonic torques of VSI based induction motor drive. **04**
(c) Explain the feature of PWM inverter fed Induction motor drive. **07**
- Q.5** (a) Explain the effect of non-sinusoidal supply on VSI. **03**
(b) Explain stator voltage control of induction motor. **04**
(c) Explain constant air gap flux control scheme for induction motor drives. **07**

OR

- Q.5** (a) Explain operation of doubly fed induction machine in sub synchronous mode. **03**
(b) Compare scalar control and vector control. **04**
(c) Apply the slip recovery scheme for speed controlling of induction motor drive. **07**
