

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VI (NEW) EXAMINATION – WINTER 2023****Subject Code:3160921****Date:13-12-2023****Subject Name: HVDC Transmission Systems****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

MARKS

- | | | |
|------------|---|-----------|
| Q.1 | (a) List out the application of DC Transmission. | 03 |
| | (b) What are the Limitations of HVDC Transmission lines? | 04 |
| | (c) Give Comparison of AC and DC Transmission. | 07 |
| Q.2 | (a) List out the Components of a HVDC system. | 03 |
| | (b) Why Commutation is required in HVDC system? | 04 |
| | (c) Explain Line Commutated Converter based HVDC Systems. | 07 |
| | OR | |
| | (c) Explain Voltage Source Converter based HVDC Systems. | 07 |
| Q.3 | (a) What will be the Effect of Delaying the Firing Instant? | 03 |
| | (b) What is commutation process in HVDC system? | 04 |
| | (c) Explain Basic Principal of three-phase AC–DC Conversion, six pulse converter operation. | 07 |
| | OR | |
| Q.3 | (a) What is the Importance of Reactive power? | 03 |
| | (b) What do you mean by Rectifier and Inverter operation? | 04 |
| | (c) Explain Twelve Pulse Converters operation in detail. | 07 |
| Q.4 | (a) Write down only VSC Operating Principle. | 03 |
| | (b) Explain Selective Harmonic Elimination | 04 |
| | (c) Discuss PWM schemes in detail. | 07 |
| | OR | |
| Q.4 | (a) How Real and Reactive power control using a VSC? | 03 |
| | (b) Explain Phase Lock Loop (PLL). | 04 |
| | (c) Discuss Principles of DC Link Control in a VSC based HVDC system in detail. | 07 |
| Q.5 | (a) What is the role of Smoothing Reactors? | 03 |
| | (b) Explain Corona effect in DC Line. | 04 |
| | (c) Discuss Voltage Stability Problem in AC/DC systems. | 07 |
| | OR | |
| Q.5 | (a) Write down a Principle of Power modulation. | 03 |
| | (b) List out the Types of Multi-terminal HVDC System. | 04 |
| | (c) Write a short note on “Modern Trends in HVDC Technology.” | 07 |
