

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VI(NEW) EXAMINATION – WINTER 2022****Subject Code:3160921****Date:17-12-2022****Subject Name:HVDC Transmission Systems****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) Compare AC and DC Transmission in view of economy and reliability.	03
	(b) Enlist limitations of HVDC transmission lines.	04
	(c) Explain six pulse converter with neat diagram.	07
Q.2	(a) Explain characteristics of harmonics.	03
	(b) What will happen, when a line commutated converter operates in inverter mode?	04
	(c) Analyze the effect of delaying the firing angle.	07
	OR	
	(c) Explain twelve pulse converters.	07
Q.3	(a) Write components of HVDC system.	03
	(b) Write short note on “corona effect”.	04
	(c) Explain power flow and dc voltage control in VSC based HVDC system	07
	OR	
Q.3	(a) What is the function of smoothening reactor?	03
	(b) Write short note on DC breaker.	04
	(c) Explain real and reactive power control using VSC.	07
Q.4	(a) Explain multi-level converter.	03
	(b) Classify PWM techniques.	04
	(c) Explain rotating reference frame theory.	07
	OR	
Q.4	(a) Write about PWM.	03
	(b) Explain “Phase-Locked Loop”	04
	(c) What is selective harmonic elimination technic? How to eliminate selective harmonics?	07
Q.5	(a) Differentiate between synchronous and asynchronous link.	03
	(b) How to enhance frequency stability using HVDC control.	04
	(c) Explain mono-polar operation of HVDC.	07
	OR	
Q.5	(a) Explain parallel operation of HVDC system.	03
	(b) Explain about multi-terminal HVDC system.	04
	(c) Explain control of power in MTDC.	07
