

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VI EXAMINATION – SUMMER 2025****Subject Code: 3160921****Date: 30-05-2025****Subject Name: HVDC Transmission Systems****Time: 10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) List out the Components of a HVDC system.	03
	(b) What are the Limitations of HVDC Transmission lines?	04
	(c) Explain twelve pulse converters.	07
Q.2	(a) Explain characteristics of harmonics.	03
	(b) What will happen, when a line commutated converter operates in inverter mode?	04
	(c) Analyze the effect of delaying the firing angle.	07
	OR	
	(c) Explain effects of firing angle delay in line commutated converters.	07
Q.3	(a) What do you mean by Rectifier and Inverter operation?	03
	(b) Write short note on “corona effect”.	04
	(c) Write short note on high level controllers.	07
	OR	
Q.3	(a) What is commutation process in HVDC system?	03
	(b) Write short note on DC breaker.	04
	(c) Explain mono-polar operation of HVDC.	07
Q.4	(a) Write down a Principle of Power modulation.	03
	(b) Explain “Phase-Locked Loop”	04
	(c) What is selective harmonic elimination technic? How to eliminate selective harmonics?	07
	OR	
Q.4	(a) List out the Types of Multi-terminal HVDC System.	03
	(b) Classify PWM techniques.	04
	(c) Explain rotating reference frame theory.	07
Q.5	(a) Explain basic principles of synchronous and asynchronous links.	03
	(b) Explain DC line faults in VSC systems.	04
	(c) Write a short note on “Modern Trends in HVDC Technology.”	07
	OR	
Q.5	(a) Explain DC line faults in LCC systems.	03
	(b) Explain modular multi-level converters.	04
	(c) Discuss Voltage Stability Problem in AC/DC systems.	07
