

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VI (NEW) EXAMINATION – SUMMER 2024****Subject Code:3160921****Date:24-05-2024****Subject Name:HVDC Transmission Systems****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) State the relative merits of HVDC transmission and HVAC transmission by taking in to consideration (i) Economics of power transmission (ii) Technical Performance (iii) Reliability	03
	(b) Explain with neat sketch different types of HVDC links (i) Monopolar HVDC link (ii) Bipolar Homopolar HVDC link and (iii) Homopolar HVDC link.	04
	(c) With a neat schematic diagram, state the various apparatus required for HVDC station and explain the purpose of each.	07
Q.2	(a) Sketch the waveforms of output voltage and the transformer secondary current in the case of 3 – phase, 6 pulse bridge circuit (Graetz's circuit)	03
	(b) Identify the various sources for generation of harmonics in HVDC systems and mention the various adverse effects caused due to the presence of harmonics.	04
	(c) Distinguish between delay in firing angle α and extinction angle γ of an HVDC converter. Explain the operation of a converter when working as an inverter, and state the necessary conditions required for inverter operation.	07
OR		
	(c) Explain 12 pulse converter with schematic diagram.	07
Q.3	(a) State difference in power control in HVDC and HVAC systems and explain the necessity of power control in an HVDC link.	03
	(b) Explain the operation of pulse frequency control and state why it is preferred in modern HVDC systems?	04
	(c) What do you understand by constant extinction angle control? What are the parameters that should be taken in to account while designing constant extinction angle controller?	07
OR		
Q.3	(a) Explain starting and stopping of an HVDC link.	03
	(b) Explain the relative merits and demerits of constant current and constant voltage operation of an HVDC link.	04
	(c) Explain real and reactive power control using VSC.	07
Q.4	(a) Explain principles of DC Link control in a LCC HVDC system.	03

- (b) Describe selective harmonic elimination techniques. **04**
- (c) Explain basic principles of synchronous and asynchronous links. **07**

OR

- Q.4**
- (a) Mention the essential requirements of ground electrodes in HVDC systems and explain the necessity of each item briefly. **03**
 - (b) How are insulators for DC different from that for AC? What are their requirements? **04**
 - (c) Write notes on voltage stability problems in HVAC/DC systems. **07**
- Q.5**
- (a) Why are multiterminal DC systems needed? What are the different types of MTDC systems used? **03**
 - (b) How is power sharing and power control achieved in an MTDC systems. **04**
 - (c) Give the principle of different types of DC circuit breaker schemes. Why is a surge diverter needed across the DC circuit breaker. **07**

OR

- Q.5**
- (a) Classify PWM techniques. **03**
 - (b) What is modular multilevel converter? **04**
 - (c) Explain different aspects to be considered for a parallel operation in MTDC systems. **07**
