

GUJARAT TECHNOLOGICAL UNIVERSITY
BE - SEMESTER-VII (NEW) EXAMINATION – WINTER 2022

Subject Code:3170916**Date:10-01-2023****Subject Name:Advanced Electric Drives****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) Explain PWM control of inverter in brief.	03
	(b) Explain in brief, the control of Current Source Inverter with necessary diagram.	04
	(c) Explain operation of H bridge as a 4-Q drive.	07
Q.2	(a) Describe Selected Harmonic Elimination with necessary figure.	03
	(b) Compare Direct Torque Control and Flux Oriented Control of an Induction Motor drive	04
	(c) Draw and explain operation of open loop V/f control of Induction motor with PWM voltage fed converter.	07
	OR	
	(c) Write a note on reference frame theory.	07
Q.3	(a) In brief, discuss about the Space Vector Modulation with relevant diagrams.	03
	(b) Explain Clarke's transformation for ABC to $\alpha\beta$ conversion.	04
	(c) Write a note on open-loop v/f control of synchronous motor.	07
	OR	
Q.3	(a) Draw the circuit diagram and waveforms for PWM converter as line side rectifier.	03
	(b) Explain Park's transformation for $\alpha\beta$ to dq conversion.	04
	(c) Explain the CSI fed synchronous motor drive.	07
Q.4	(a) Draw block diagram of synchronous motor drive.	03
	(b) List different control techniques of PMSM.	04
	(c) Draw block diagram of speed control of BLDC motor drive.	07
	OR	
Q.4	(a) Compare vector control with direct torque control of synchronous motor drive.	03
	(b) Explain the working of BLDC motor.	04
	(c) Draw block diagram of speed control of PMSM motor drive.	07
Q.5	(a) Draw block diagram for closed loop speed control of SRM.	03
	(b) Discuss PWM module in DSP.	04
	(c) List and explain various topologies for SRM drives.	07
	OR	
Q.5	(a) Draw the inductance profile for 6/4 SRM motor.	03
	(b) List the various DSPs available in market and draw the basic block diagram of DSP controller.	04
	(c) Explain the working of SRM with any-one control topology.	07