

**GUJARAT TECHNOLOGICAL UNIVERSITY**

**BE - SEMESTER-VII (NEW) EXAMINATION – SUMMER 2024**

**Subject Code:3170916**

**Date:22-05-2024**

**Subject Name:Advanced Electric Drives**

**Time:02:30 PM TO 05:00 PM**

**Total Marks:70**

**Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

**MARKS**

- |            |  |           |
|------------|--|-----------|
| <b>Q.1</b> | (a) Describe Selected Harmonic Elimination with necessary figure.  | <b>03</b> |
|            | (b) Explain in brief, the control of Voltage Source Inverter with necessary diagram.                       | <b>04</b> |
|            | (c) Draw and explain the equivalent circuit of a single –phase induction machine.                          | <b>07</b> |
| <b>Q.2</b> | (a) Explain in short 3 level inverter.   | <b>03</b> |
|            | (b) Differentiate between CSI and VSI.   | <b>04</b> |
|            | (c) Explain Direct torque and flux control of induction motor.   | <b>07</b> |
|            | <b>OR</b>  |           |
|            | (c) Explain CSI fed synchronous motor drives.  | <b>07</b> |
| <b>Q.3</b> | (a) State advantages of vector control over scalar control.  | <b>03</b> |
|            | (b) Discuss the points to be considered while selecting carrier frequency for inverter.                    | <b>04</b> |
|            | (c) Draw and explain operation of open loop V/f control of Induction motor with PWM voltage fed converter. | <b>07</b> |
|            | <b>OR</b>  |           |
| <b>Q.3</b> | (a) Why dynamic model Induction motor is required?   | <b>03</b> |
|            | (b) Enlist advantages of V/f control of induction motor  | <b>04</b> |
|            | (c) Write a note on Reference-frame theory, and state commonly used reference frames.                      | <b>07</b> |
| <b>Q.4</b> | (a) Classify permanent magnet motors.  | <b>03</b> |
|            | (b) Draw and explain SRM.  | <b>04</b> |
|            | (c) Explain construction and working of BLDC motor.  | <b>07</b> |
|            | <b>OR</b>  |           |
| <b>Q.4</b> | (a) Enlist various topologies of SRM drives.   | <b>03</b> |
|            | (b) Compare BLDC and PMDC motors.  | <b>04</b> |
|            | (c) Explain construction and working of PMDC motor.  | <b>07</b> |
| <b>Q.5</b> | (a) Discuss the effect of harmonics on induction motor.  | <b>03</b> |
|            | (b) Write a short note on TMSLF2407 with reference to motion control.                                      | <b>04</b> |
|            | (c) Draw and explain operation of open loop V/f control of synchronous motor drive.                        | <b>07</b> |
|            | <b>OR</b>  |           |
| <b>Q.5</b> | (a) Discuss the advantages of uses of DSP in electric drive system.  | <b>03</b> |
|            | (b) Discuss PWM module in DSP.   | <b>04</b> |
|            | (c) Draw and explain block diagram of closed loop speed control of SRM drive.                              | <b>07</b> |

\*\*\*\*\*