

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-VII (NEW) EXAMINATION – SUMMER 2022****Subject Code:3170916****Date:08/06/2022****Subject Name:Advanced Electric Drives****Time:02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

**MARKS**

- |            |  |           |
|------------|--|-----------|
| <b>Q.1</b> | (a) Explain PWM control of inverter in brief.  | <b>03</b> |
|            | (b) Draw the block diagram of Electric drive.  | <b>04</b> |
|            | (c) Draw and explain PWM converter as line side rectifier.   | <b>07</b> |
| <b>Q.2</b> | (a) Describe Selected Harmonic Elimination with necessary figure.  | <b>03</b> |
|            | (b) Discuss the importance of V/f ratio in IM drive.   | <b>04</b> |
|            | (c) Describe the operation of H bridge as a 4-Q drive.   | <b>07</b> |
|            | <b>OR</b>  |           |
|            | (c) Write a note on reference frame theory.  | <b>07</b> |
| <b>Q.3</b> | (a) State advantages of SHE technique.   | <b>03</b> |
|            | (b) Compare vector control and scalar control.   | <b>04</b> |
|            | (c) Discuss speed control in BLDC motors.  | <b>07</b> |
|            | <b>OR</b>  |           |
| <b>Q.3</b> | (a) Describe use of DSP to generate PWM.   | <b>03</b> |
|            | (b) Compare Direct Torque Control and Field Oriented Control.  | <b>04</b> |
|            | (c) Draw and explain operation of open loop V/f control of Induction motor with PWM voltage fed converter. | <b>07</b> |
| <b>Q.4</b> | (a) List different permanent magnet motors.  | <b>03</b> |
|            | (b) Draw block diagram of synchronous motor drive.   | <b>04</b> |
|            | (c) Explain direct torque control of synchronous motor.  | <b>07</b> |
|            | <b>OR</b>  |           |
| <b>Q.4</b> | (a) Draw block diagram for closed loop speed control of SRM.   | <b>03</b> |
|            | (b) List different control techniques of PMSM.   | <b>04</b> |
|            | (c) List and explain various topologies for SRM drives.  | <b>07</b> |
| <b>Q.5</b> | (a) Compare open loop and close loop control of an electric drive.   | <b>03</b> |
|            | (b) Draw equivalent circuit model of Induction motor.  | <b>04</b> |
|            | (c) Explain switching vectors in space vector modulation with a neat labelled diagram.                     | <b>07</b> |
|            | <b>OR</b>  |           |
| <b>Q.5</b> | (a) State advantages and drawbacks of PM motors.   | <b>03</b> |
|            | (b) Draw figure showing construction of outer rotor design type BLDC motor.                                | <b>04</b> |
|            | (c) Draw block diagram for DSP based Brushless Direct Current Motor Drive System.                          | <b>07</b> |