

GUJARAT TECHNOLOGICAL UNIVERSITY**BE- SEMESTER-VII (NEW) EXAMINATION – WINTER 2024****Subject Code:3170906****Date:30-11-2024****Subject Name: Advanced Power Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

MARKS

- | | | |
|------------|---|-----------|
| Q.1 | (a) Explain fly back converter topology with diagram and wave forms. | 03 |
| | (b) Define FACTS. Give classification of FACTS controllers. | 04 |
| | (c) Explain operation of ZVS converter with diagram and wave forms. | 07 |
| Q.2 | (a) Classify the Resonant converter. | 03 |
| | (b) What is the need of Resonant Converter? Compare Series Loaded Resonant (SLR) converter with Parallel loaded resonant (PLR) Converter. | 04 |
| | (c) Derive the expression for duty ratio in continuous and discontinuous mode of operation for Buck -Boost converter with circuit diagram and waveform. | 07 |
| | OR | |
| | (c) Discuss operation of Push pull converter type switched mode dc power supply along with necessary waveforms. | 07 |
| Q.3 | (a) Explain the concept and need of Multi Level inverter. | 03 |
| | (b) Compare the three topologies of multilevel inverter | 04 |
| | (c) Draw circuit diagram and wave forms of five level diode clamped inverter. Explain its working. | 07 |
| | OR | |
| Q.3 | (a) Explain operation of Cascaded H-bridge multilevel inverter | 03 |
| | (b) State advantages and disadvantages of multi-pulse converters. | 04 |
| | (c) Draw the transformer connections for 18 pulse converters.
Explain Y-Z2 transformer connection used for multipulse converter | 07 |
| Q.4 | (a) Explain working principal of SSSC. | 03 |
| | (b) Comparison of SVC & STATCOM. | 04 |
| | (c) Explain operating principle of Unified power flow controller (UPFC). | 07 |
| | OR | |
| Q.4 | (a) Discuss need of phase shifting transformer. | 03 |
| | (b) Explain the working of Fixed Capacitor Thyristor-Controlled Reactor (FC-TCR).
Draw neat diagrams. | 04 |
| | (c) Explain the working principle of TSC-TCR | 07 |
| Q.5 | (a) Explain different type of HVDC link. | 03 |
| | (b) Draw the typical HVDC transmission scheme and explain the equipment's required for HVDC system | 04 |
| | (c) Discuss sine PWM techniques used for multilevel inverter. | 07 |
| | OR | |
| Q.5 | (a) What is the difference between isolated and non-isolated dc power supply? | 03 |
| | (b) What is phase angle compensation in transmission line? | 04 |
| | (c) State the advantages HVDC transmission over EHVAC transmission for bulk power transmission | 07 |
