

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-VII (NEW) EXAMINATION – WINTER 2023****Subject Code:3170906****Date:08-12-2023****Subject Name: Advanced Power Electronics****Time: 10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
<b>Q.1</b>	(a) Compare Linear voltage regulator and Switch mode voltage regulator with the help of block diagram.	<b>03</b>
	(b) With neat circuit diagram and waveform discuss class E resonant inverter.	<b>04</b>
	(c) Discuss operation of Buck converter in continuous and discontinuous conduction mode.	<b>07</b>
<b>Q.2</b>	(a) Draw schematic diagram of Monopolar, Bipolar and Homopolar link for HVDC system.	<b>03</b>
	(b) Draw circuit diagram and waveforms of five level diode clamped inverter.	<b>04</b>
	(c) Figure out the specifications/properties of a good power supply. Explain construction and working of Fly back converter type switched mode dc power supply.	<b>07</b>
	<b>OR</b>	
	(c) Explain the forward converter with waveform. Derive its output voltage expression. Draw its circuit diagram and waveforms.	<b>07</b>
<b>Q.3</b>	(a) Classify resonant pulse converter and discuss applications.	<b>03</b>
	(b) Compare ZCS and ZVS.	<b>04</b>
	(c) Draw circuit diagram and waveforms of five level flying capacitor inverter. Explain its working.	<b>07</b>
	<b>OR</b>	
<b>Q.3</b>	(a) Draw circuit diagram and waveforms of Zero Voltage Switching Converter	<b>03</b>
	(b) Write the advantages of resonance converter as compared to PWM converter	<b>04</b>
	(c) Mention advantages of H bridge multilevel inverter. Explain working of five level H bridge inverter.	<b>07</b>
<b>Q.4</b>	(a) State the types of HVDC systems and explain each in brief.	<b>03</b>
	(b) Explain concept, advantages and limitations of multi-pulse converter.	<b>04</b>
	(c) Explain the working principle of Thyristorised Controlled Reactor (TCR) with neat sketch.	<b>07</b>
	<b>OR</b>	
<b>Q.4</b>	(a) Compare AC and HVDC power transmission systems.	<b>03</b>
	(b) Draw the transformer connections for 18-pulse converter.	<b>04</b>
	(c) Explain the working of three-phase Thyristor Controlled Reactor (TCR) with neat diagrams. How to reduce harmonics introduced by three phase TCR?	<b>07</b>

<b>Q.5</b>	<b>(a)</b>	Define FACTS systems and state its possible benefits in Emerging Transmission Network.	<b>03</b>
	<b>(b)</b>	Explain difference between multi pulse converter and multilevel converter with suitable diagram.	<b>04</b>
	<b>(c)</b>	Discuss principle of shunt compensation. Explain operation of fixed capacitor- thyristors controlled reactor.	<b>07</b>
<b>OR</b>			
<b>Q.5</b>	<b>(a)</b>	State the need of reactive power compensation	<b>03</b>
	<b>(b)</b>	Explain Y-Z2 transformer connection used for multipulse converter.	<b>04</b>
	<b>(c)</b>	Explain the delta connected 3 phase-TCR with necessary diagram and waveforms.	<b>07</b>

\*\*\*\*\*