

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-VII (NEW) EXAMINATION – WINTER 2022****Subject Code:3170906****Date:10-01-2023****Subject Name:Advanced Power Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

**MARKS**

- |            |  |           |
|------------|--|-----------|
| <b>Q.1</b> | (a) Compare Linear voltage regulator and Switch mode voltage regulator with the help of block diagram.   | <b>03</b> |
|            | (b) Explain full bridge converter. State its advantages over half bridge converter.  | <b>04</b> |
|            | (c) Derive output equation for the buck-boost converter with necessary circuit diagram and waveform.   | <b>07</b> |
| <b>Q.2</b> | (a) Explain the working principle of resonant converter.   | <b>03</b> |
|            | (b) Explain fly back converter.  | <b>04</b> |
|            | (c) How the harmonic current are canceled by phase shifting transformer in 12 pulse rectifier? Explain with necessary schematic diagram.               | <b>07</b> |
|            | <b>OR</b>  |           |
|            | (c) Discuss the equipment required for HVDC systems  | <b>07</b> |
| <b>Q.3</b> | (a) Compare HVDC and HVAC transmission systems.  | <b>03</b> |
|            | (b) Draw schematic diagram of Monopolar, Bipolar and Homopolar link.   | <b>04</b> |
|            | (c) Draw the circuit diagram and waveform of five levels cascaded H – Bridge Multilevel Inverter and explain its working.                              | <b>07</b> |
|            | <b>OR</b>  |           |
| <b>Q.3</b> | (a) Give comparison of ZCS & ZVS resonant converter.   | <b>03</b> |
|            | (b) Differentiate between continuous mode of conduction and discontinuous mode of conduction.  | <b>04</b> |
|            | (c) Explain the working of one leg five levels diode clamped multilevel inverter with circuit diagram and waveform. Also mention its salient features. | <b>07</b> |
| <b>Q.4</b> | (a) Why multi pulse converter is better than conventional converter?   | <b>03</b> |
|            | (b) Explain the operation of Class E converter.  | <b>04</b> |
|            | (c) Explain following transformer connection with phasor diagram used in multi pulse converter. (a) Y-Z1 (b) Δ-Z1                                      | <b>07</b> |
|            | <b>OR</b>  |           |
| <b>Q.4</b> | (a) Compare Series Loaded Resonant (SLR) converter with Parallel loaded resonant (PLR) Converter.  | <b>03</b> |
|            | (b) Define Flexible ac Transmission Systems (FACTS) with brief description.  | <b>04</b> |
|            | (c) Explain operating principle of Unified power flow controller (UPFC).   | <b>07</b> |
| <b>Q.5</b> | (a) Discuss static characteristics of STATCOM  | <b>03</b> |
|            | (b) State advantages and limitation of SSSC.   | <b>04</b> |
|            | (c) Explain the working principle of TSC-TCR.  | <b>07</b> |

**OR**

- |            |            |   |           |
|------------|------------|---|-----------|
| <b>Q.5</b> | <b>(a)</b> | Compare SVC and STATCOM.  | <b>03</b> |
|            | <b>(b)</b> | What is series compensation? Discuss working of Thyristor controlled series capacitor (TCSC). | <b>04</b> |
|            | <b>(c)</b> | Explain the working principle of FC-TCR   | <b>07</b> |

\*\*\*\*\*