

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-VII EXAMINATION – SUMMER 2025

Subject Code:3170906

Date:16-05-2025

Subject Name:Advanced Power Electronics

Time:02:30 PM TO 05:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) Define duty cycle and write its importance.	03
	(b) Explain fly back converter.	04
	(c) Illustrate the push pull converter with neat circuit diagram & waveform and derive the equation of output voltage in terms of input voltage & duty cycle.	07
Q.2	(a) Differentiate between continuous mode of conduction and Discontinuous mode of conduction	03
	(b) What is the need of Resonant Converter? Compare Series Loaded Resonant (SLR) converter with Parallel loaded resonant (PLR) Converter	04
	(c) What do you mean by Zero Voltage Switching (ZVS). With neat circuit and waveform explain the operation of ZVS Converter	07
	OR	
	(c) Explain the operation of two transistor forward converter with circuit diagram, waveform and required equation.	07
Q.3	(a) Give Classification of resonant converters.	03
	(b) Classify carrier based PWM technique for multilevel inverter. Discuss any one in detail .	04
	(c) Draw circuit diagram and output voltage phasor diagram of 12-pulse converter.	07
	OR	
Q.3	(a) Compare the three topologies of multilevel inverter.	03
	(b) What are the advantages of cascaded H bridge multi-level inverter over other two topologies?	04
	(c) Explain following transformer connection with phasor diagram used in multi pulse converter. (a) Y-Z1 (b) Δ -Z1	07
Q.4	(a) Explain star/delta phase shifting transformer with phasor diagram	03
	(b) What is phase angle compensation in transmission system?	04

	(c)	Explain TCR with circuit diagram. Draw current and voltage waveforms for different values of α	07
		OR	
Q.4	(a)	Explain different types of HVDC link.	03
	(b)	Draw block diagram of HVDC transmission system. Mention equipment required for HVDC system.	04
	(c)	Explain working of Static Synchronous Series Compensator (SSSC) with neat diagrams	07
Q.5	(a)	State the need of reactive power compensation.	03
	(b)	Discuss the principle of series compensation and state various methods for series compensation	04
	(c)	Explain operating principle of Unified power flow controller (UPFC).	07
		OR	
Q.5	(a)	Give classification and applications of phase shifting transformer	03
	(b)	Discuss static characteristics of STATCOM	04
	(c)	Explain the working principle of TSC-TCR.	07
