

GUJARAT TECHNOLOGICAL UNIVERSITY**BE – SEMESTER- VII EXAMINATION-SUMMER 2023****Subject Code: 3170906****Date: 26/06/2023****Subject Name: Advanced Power Electronics****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) State important advantages, disadvantages and application of SMPS	03
	(b) Explain Flyback converter.	04
	(c) Discuss operation of CUK converter. Derive the relation between duty ratio and i/p voltage.	07
Q.2	(a) Classify the Resonant converter.	03
	(b) What is the need of Resonant Converter? Compare Series Loaded Resonant (SLR) converter with Parallel Loaded Resonant (PLR) converter.	04
	(c) Explain the operation of Zero Voltage Switching resonant converter with circuit diagram, waveform and required equation.	07
	OR	
	(c) Explain operation of Cascaded H-bridge multilevel inverter.	07
Q.3	(a) Explain the concept and need of Multi Level inverter.	03
	Explain difference between multi pulse converter and multilevel converter with suitable diagram.	04
	(b) Draw the transformer connections for 18 pulse converter.	07
	Explain Y-Z2 transformer connection used for multipulse converter.	
	OR	
Q.3	(a) State advantages and disadvantages of Multi-pulse converter.	03
	(b) Compare the three topologies of multilevel inverter	04
	(c) Draw circuit diagram and wave forms of five level diode clamped inverter. Explain its working.	07
Q.4	(a) Explain different type of HVDC link.	03
	(b) Give Comparison of HVAC and HVDC transmission.	04
	(c) Draw and explain bipolar HVDC power transmission system based on 12 pulse converters for each pole.	07
	OR	
Q.4	(a) What is phase angle compensation in transmission line?	03
	(b) Draw the typical HVDC transmission scheme and explain the equipments required for HVDC system.	04
	(c) Discuss importance of reactive power compensation. Discuss phase-shifting transformer with necessary diagram in brief.	07
Q.5	(a) Explain the advantages and limitations of static synchronous series compensator (SSSC).	03
	(b) Define FACTS. Give detail classification of FACTS controller.	04

- (c) Explain the working principle of Thyristorised controlled Reactor (TCR) with neat sketch. **07**

OR

- Q.5** (a) Compare SVC and STATCOM. **03**
(b) What is Synchronous Condenser? **04**
(c) Explain operating principle of Unified Power Flow Controller (UPFC). **07**
