

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-V (NEW) EXAMINATION – WINTER 2023****Subject Code:3151106****Date:07-12-2023****Subject Name:Power Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
 2. Make suitable assumptions wherever necessary.
 3. Figures to the right indicate full marks.
- Simple and non-programmable scientific calculators are allowed.

- Q.1** (a) Describe V-I characteristics of TRIAC briefly. **03**
 (b) Explain in brief about IGBT. **04**
 (c) Discuss firing or triggering of Thyristor in detail. **07**

- Q.2** (a) Write the usage of snubber circuit in power electronics. **03**
 (b) What is the usage of freewheeling diode in controlled rectifiers? **04**
 (c) Draw and explain the circuit of ac phase control using DIAC and TRIAC. **07**

OR

- (c) Draw necessary waveforms and explain working of single phase full controlled bridge rectifier circuit with RLE load. **07**

- Q.3** (a) Explain Step down Chopper briefly. **03**
 (b) Compare class B and class C Chopper **04**
 (c) Explain the principal of Dielectric Heating. Also gives application of Dielectric Heating. **07**

OR

- Q.3** (a) What is commutation circuit for Thyristor? **03**
 (b) Explain displacement factor and harmonic factor of rectifiers. **04**
 (c) Explain in brief the different control strategies for chopper. **07**

- Q.4** (a) Draw the block diagram of UPS. **03**
 (b) Enlist advantages and disadvantages of multiphase chopper? **04**
 (c) Draw and explain the V-I characteristics of UJT. **07**

OR

- Q.4** (a) Design and explain the operation of current source inverter. **03**
 (b) List different driver circuits for MOSFET and IGBT and explain one IC based driver circuit. **04**
 (c) Explain bridge square wave inverter with necessary diagrams. **07**

- Q.5** (a) Compare online and offline UPS. **03**
 (b) What are the applications of an inverter? **04**
 (c) Explain Speed control of Motor. **07**

OR

- Q.5** (a) Enlist advantages of DC chopper drive. **03**
 (b) What is soft switching? Enlist the types of soft switching. **04**
 (c) Explain the construction and working of flyback converter type switched mode DC power supply. **07**

