

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-V (NEW) EXAMINATION – SUMMER 2024****Subject Code: 3151106****Date: 18-05-2024****Subject Name: Power Electronics****Time: 02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) Explain the basic requirements for the successful firing of SCR.	03
	(b) Explain the structure and various triggering modes of operation of TRIAC.	04
	(c) The half wave controlled rectifier has purely resistive load of R and delay angle $\alpha = 60^\circ$ determine. (i) Rectification efficiency (ii) Form factor and (iii) Ripple factor.	07
Q.2	(a) Compare natural and forced commutations of SCR.	03
	(b) Explain the various Turn-On methods of SCR in brief.	04
	(c) Derive the average load voltage and load current equations of single phase half wave controlled rectifier with resistive and inductive load.	07
	OR	
	(c) A dc chopper operates on 300V dc and frequency of 200 Hz, feeds an R-L load. Determine the ON times of the chopper for output voltage of 150V.	07
Q.3	(a) Draw the schematic of step-up chopper and derive an expression for output voltage of chopper.	03
	(b) Compare the Time Ratio control and current limit control strategies of chopper.	04
	(c) With help of neat circuit diagram and waveforms, explain the operation of single phase half bridge voltage source inverter with resistive load.	07
	OR	
Q.3	(a) What are the applications of chopper? Explain the working of class A chopper.	03
	(b) Explain the multiphase chopper.	04
	(c) With help of neat circuit diagram and waveforms, explain the operation of single phase full bridge square wave inverter with resistive load.	07
Q.4	(a) Explain the dv/dt and di/dt ratings of SCR.	03
	(b) What is commutation? Explain class D forced commutation.	04
	(c) Design the basic structure of MCT and explain its turn on and turn off operations.	07
	OR	
Q.4	(a) Explain the internal control pulse width modulation control method of inverter.	03
	(b) Compare IGBT and Power MOSFET.	04
	(c) Design the structure of MOSFET and explain its operation and V-I characteristics.	07

- | | | | |
|------------|------------|---|-----------|
| Q.5 | (a) | Compare General Power supply and SMPS. | 03 |
| | (b) | Explain the working of fly back converter SMPS. | 04 |
| | (c) | With help of block diagram, explain the operation of on line UPS. List the important specifications of on line UPS. | 07 |
| OR | | | |
| Q.5 | (a) | What do you mean by EMI and EMC? | 03 |
| | (b) | Explain the working of induction motor. | 04 |
| | (c) | Write short note on permanent magnet stepper motor drive. | 07 |
