

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-V(NEW) EXAMINATION – SUMMER 2022****Subject Code:3151106****Date:04/06/2022****Subject Name:Power Electronics****Time:02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) Give classification of thyristors family.	03
	(b) Explain advantages of IGBT.	04
	(c) Explain the construction, operation and characteristics of SCR	07
Q.2	(a) Give the classification of inverters.	03
	(b) Explain single phase AC chopper with necessary diagram.	04
	(c) Draw and explain Three Phase Half wave controlled rectifier with required waveforms and equations.	07
	OR	
	(c) Draw and explain the circuit of ac phase control using DIAC and TRIAC.	07
Q.3	(a) Draw and explain Phase Locked Loop Control of DC Drives.	03
	(b) Differentiate between online and offline UPS systems.	04
	(c) What is SMPS? Give the classification of SMPS. Also List out advantages and disadvantages of SMPS.	07
	OR	
Q.3	(a) What is Commutation? Explain briefly the classification of commutation techniques.	03
	(b) Gives comparison between DC and AC Drives.	04
	(c) Explain the principal of Dielectric Heating. Also gives application of Dielectric Heating.	07
Q.4	(a) What is SMPS? Give the classification of SMPS.	03
	(b) A 200 A SCR is to be connected in parallel with 300 A SCR. The on state voltage drops of the SCRs are 2.1 V and 1.75 V respectively. Calculate the series resistance that should be connected with each SCR if the two SCRs have to share the total current 500 A in proportion to their ratings.	04
	(c) Draw and explain the V-I characteristics of UJT.	07
	OR	
Q.4	(a) Why a freewheeling diode is connected in inductive loaded circuit?	03
	(b) What is Pulse Width Modulation? How can it be used to control the output of chopper?	04
	(c) Explain single phase half wave controlled rectifier with RL load with proper waveforms.	07
Q.5	(a) Explain Step down Chopper.	03
	(b) Explain regenerative and dynamic braking of dc motor.	04
	(c) Explain Speed control of Motor	07

OR

- | | | | |
|------------|-----|--|-----------|
| Q.5 | (a) | Write down the basic principle of induction heating. | 03 |
| | (b) | Explain UJT as relaxation oscillator. | 04 |
| | (c) | Write a short note on online UPS system. | 07 |
