

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-V (NEW) EXAMINATION – SUMMER 2024****Subject Code:3151105****Date:23-05-2024****Subject Name:VLSI Design****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

MARKS

- Q.1**
- (a) Compare semicustom and Full custom VLSI design style. **03**
- (b) Discuss following approaches used to reduce complexity of IC design **04**
i) Hierarchy ii) Regularity iii) Modularity iv) Locality
- (c) Draw and explain various fabrication steps for CMOS inverter with proper notations at each fabrication steps. **07**

- Q.2**
- (a) Explain MOSFET capacitance in brief. **03**
- (b) Derive the drain current equation for MOSFET using Gradual Channel Approximation (GCA) **04**
- (c) Find the depletion layer width, depletion region charge and threshold voltage with no substrate bias with the following physical parameters. **07**
Physical parameters
VSB=0, for silicon gate n channel MOS transistor, with the following parameters:
Substrate doping density $N_A = 1.5 \times 10^{16} \text{ cm}^{-3}$,
Gate donor doping $N_D = 10^{18} \text{ cm}^{-3}$,
Gate oxide thickness $t_{ox} = 400 \text{ \AA}$,
 $N_{ss} = 10 \times 10^{10} \text{ cm}^{-3}$.
Consider Boltzmann Constant $= 1.38 \times 10^{-23} \text{ (J/K)}$,
Electron charge $= 1.6 \times 10^{-19} \text{ C}$,
Intrinsic Silicon carrier concentration $n_i = 1.45 \times 10^{10} \text{ cm}^{-3}$,
 $\epsilon_{Si} = 1.035 \times 10^{-12} \text{ F/cm}$
 $\epsilon_0 = 8.85 \times 10^{-14} \text{ F/cm}$,
 $\epsilon_{ox} = 0.345 \times 10^{-12} \text{ F/cm}$.

OR

- (c) For an enhancement type NMOS transistor has its source terminal connected to ground and 3 V connected to the gate. NMOS has $V_T = 2 \text{ V}$, $\lambda = 0.04 \text{ 1/V}$, $\mu_n * C_{ox} = 20 \text{ A/V}^2$, $W = 200 \mu\text{m}$ and $L = 10 \mu\text{m}$, $V_G = 3 \text{ V}$, $V_D = 0.5 \text{ V}$ and 1 V . Calculate Drain Current I_D . **07**

Physical constants :Thermal voltage $= kT/q = 0.026 \text{ volt}$.Energy Gap of silicon (Si) $= E_g = 1.12 \text{ eV}$.Intrinsic Carrier Concentration of silicon $= n_i = 1.45 \times 10^{10} \text{ cm}^{-3}$.Dielectric constant of vacuum $= \epsilon_0 = 8.85 \times 10^{-14} \text{ F/cm}$.Dielectric constant of silicon $= \epsilon_{Si} = 11.7 \times \epsilon_0 \text{ F/cm}$.Dielectric constant of silicon dioxide $= \epsilon_{ox} = 3.97 \times \epsilon_0 \text{ F/cm}$

- Q.3** (a) What is meant by static and dynamic power dissipation? **03**

- (b) Define propagation delay and derive the expression for τ_{pHL} for CMOS inverter. Assume ideal step as an input to CMOS inverter. 04
- (c) Consider a resistive load inverter circuit with $V_{DD}=5\text{ V}$, $K_n'=10\mu\text{A/V}^2$, $V_{TO}=0.8\text{V}$, $R_L=400\text{k}\Omega$ and $W/L=2$. Calculate the critical Voltages (V_{OH} , V_{OL} , V_{IL} and V_{IH}) on the VTC and find the noise margins of the circuit. 07

OR

- Q.3 (a) Draw CMOS inveter. Explain its voltage transfer characteristic. Also explain the NML and NMH noise margins with respect to this transfer characteristic 03

4.4.13

- (b) Draw the inverter circuit with depletion type nMOS load. Mention the operating regions of driver and load transistors for different input voltages. Derive critical voltage points V_{OH} , V_{OL} , V_{IH} and V_{IL} for depletion- load nMOS inverter 04
- (c) Consider a CMOS inverter with the following parameters:
 $V_{DD}=3.3\text{ V}$, $V_{T0,n}=0.6\text{ V}$, $V_{T0,p}=-0.7\text{ V}$, $k_n=200\mu\text{A/V}^2$ and $k_p=160\mu\text{A/V}^2$ 07
 Calculate the noise margins of the circuit. Consider $k_R=2.5\text{ V}$ and $V_{T0,n}\neq|V_{T0,p}|$ as it is not a symmetric CMOS inverter.

- Q.4 (a) What are the limitations of Dynamic circuits? Discuss the effect of charge sharing and charge leakage in dynamic pass transistor logic. 03
- (b) Two nMOS transistors (M1 and M2) connected in series is shown in Figure 1. The power supply is $V_{DD}=3.3\text{ V}$ and the nMOS threshold $V_{TN}=0.55\text{ V}$. Find the output voltage at node b. Consider i) $V_a=2.7\text{ V}$ and ii) $V_a=3\text{V}$. 04

 


Figure 1

- (c) Explain the Euler path approach to find the optimized stick-diagram for any CMOS logic circuit. Draw the optimized stick-diagram for the following Boolean function (CMOS Logic), $F=(A(D+E)+BC)'$. Explain the importance of Euler path approach. 07

OR

- Q.4 (a) What do you mean by stick diagram? Implement the following Boolean function using stick diagram.
 $Y=(A*(D+E)+B*C)'$ 03
- (b) Explain the need of Voltage bootstrapping? Derive the mathematical expression for dynamic Voltage bootstrapping circuit. 04
- (c) For the Exclusive OR function, draw with following realization 07
1. Static CMOS realization
 2. Pseudo nMOS gate
 3. CMOS Transmission Gate(TG)

- Q.5 (a) Compare FinFET and Planar MOSFET 03
- (b) Draw transistor level circuit diagram of NAND based SR latch using CMOS. 04

(c) What is clock-skew? Explain on-chip clock generation and distribution. **07**

OR

Q.5 (a) Draw and discuss three stage ring oscillator **03**

(b) Implement and Describe CMOS clocked SR flip-flop **04**

(c) What is need of Design of Testability (DFT) in VLSI IC design and explain Built in Self Test (BIST) techniques of DFT **07**
